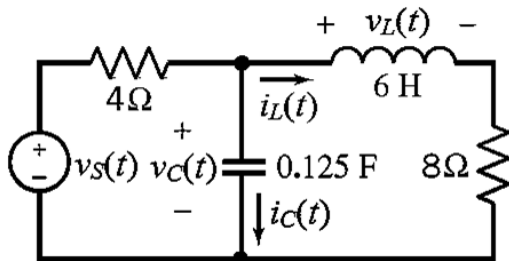



## HOMEWORK #6: Laplace Transform Network Analysis

### 1. Sketching $s$ -Domain Equivalents of Time-Domain Networks

Consider the second order network shown below with  $v_s(t) = 24 - 36u(t)$ .




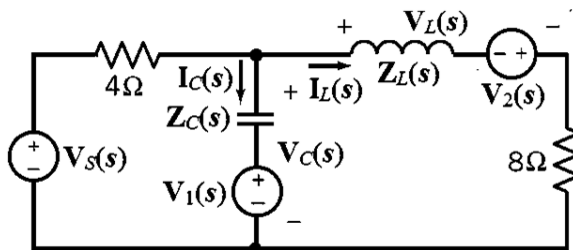- (a) The network below depicts the  $s$ -Domain equivalent of the 2<sup>nd</sup> order network with each energy storage element replaced by its Thevenin model.




Compute the following:

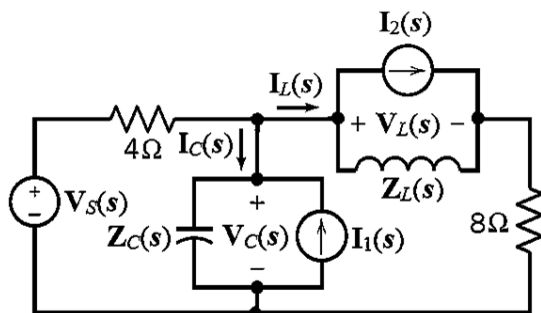- i.  $V_s(s)$
  - ii.  $Z_C(s)$  and  $Z_L(s)$
  - iii.  $V_1(s)$  and  $V_2(s)$
- (b) The network shown depicts the  $s$ -Domain model of the 2<sup>nd</sup> network with each energy storage element replaced by its Norton model. Compute  $I_1(s)$  and  $I_2(s)$ .




## 2. $s$ -Domain Analysis of Networks with Initial Conditions

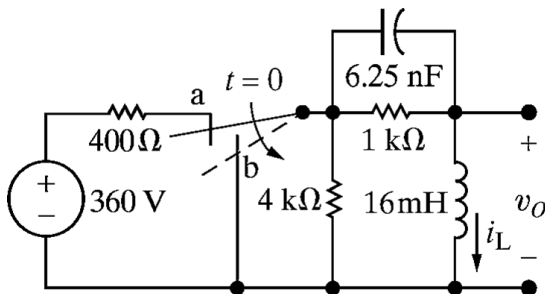- (a) Consider the second order network below. The switch moves to position (b) at  $t = 0$  after being at position (a) for a long time.




- Draw the  $s$ -Domain equivalent network valid for  $t > 0^-$ .
  - Compute  $\mathbf{V}_o(s)$ , the Laplace Transform of the complete response voltage  $v_o(t)$  for  $t > 0^-$ .
  - Compute  $\mathbf{I}_L(s)$ , the Laplace Transform of the complete response current  $i_L(t)$  for  $t > 0^-$ .
  - Compute the complete response voltage  $v_o(t)$  for  $t > 0^-$ . Identify the transient response portion  $v_{o,TR}(t)$  and steady state response portion  $v_{o,SS}(t)$  of  $v_o(t)$ . Is the transient response un-damped, under-damped, critically-damped, or over-damped?
  - Compute the complete response current  $i_L(t)$  for  $t > 0^-$ . Identify the transient response portion  $i_{L,TR}(t)$  and steady state response portion  $i_{L,SS}(t)$  of  $i_L(t)$ . Is the transient response un-damped, under-damped, critically-damped, or over-damped?
- (b) Consider the second order network below. The switch moves to position (b) at  $t = 0$  after being in position (a) for a long time.

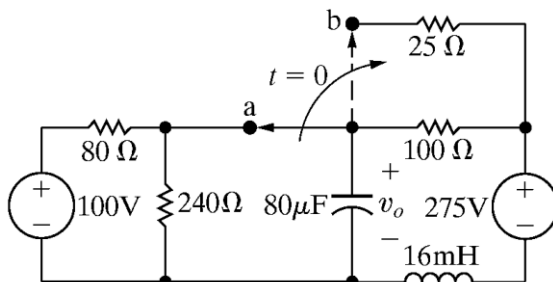


- Draw the  $s$ -Domain equivalent network valid for  $t > 0^-$ .
- Compute  $\mathbf{V}_o(s)$ , the Laplace Transform of the complete response voltage  $v_o(t)$  for  $t > 0^-$ .
- Compute the complete response voltage  $v_o(t)$  for  $t > 0^-$ . Identify the transient response portion  $v_{o,TR}(t)$  and steady state response portion  $v_{o,SS}(t)$  of  $v_o(t)$ . Is the transient response un-damped, under-damped, critically-damped, or over-damped?

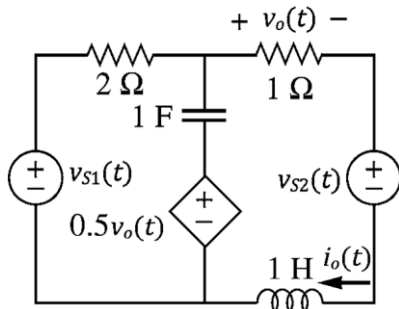- (c) Consider the second order network shown below. The independent voltage sources have expressions  $v_{s1}(t) = 5e^{-2t}u(t)V$  and  $v_{s2}(t) = 3u(-t)V$ . Compute the complete response current  $i_o(t)$  for  $t > 0^-$ .




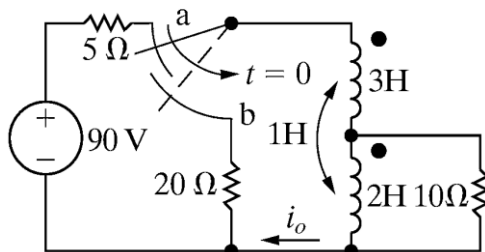- (d) Consider the magnetically coupled network shown below. The “make-before-break” switch moves to position (b) after being in position (a) for a long time. Compute the complete response current  $i_o(t)$  for  $t > 0^-$ .




### 3. s-Domain Analysis of Relaxed Networks

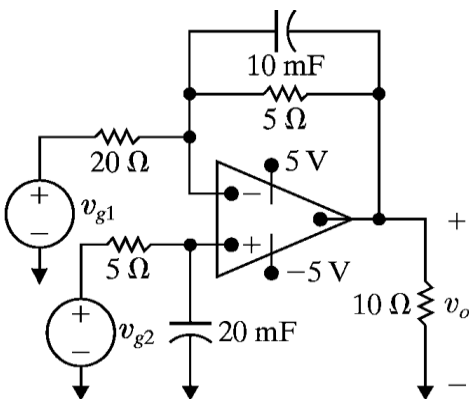- (a) Consider the second order relaxed ideal op-amp network with voltage source expressions  $v_{g1}(t) = 40u(t)V$  and  $v_{g2}(t) = 16u(t)V$ .




- Compute the complete response voltage  $v_o(t)$  for  $t > 0^-$ . Identify the transient response portion  $v_{o,TR}(t)$  and steady state response portion  $v_{o,SS}(t)$  of  $v_o(t)$ . Is the transient response un-damped, under-damped, critically-damped, or over-damped?
- Will the output voltage saturate? If so, at what time?

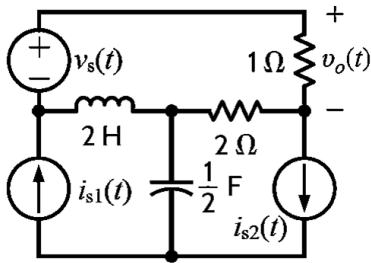
- (b) Consider the second order relaxed network shown with source expressions  $v_s(t) = 4u(t)V$ ,  $i_{s1}(t) = e^{-2t}u(t)A$ , and  $i_{s2}(t) = 2u(t)A$ . Apply Thevenin's Theorem to compute the complete response voltage  $v_o(t)$  for  $t > 0^-$ . Assume the  $1\Omega$  resistor is the load network.



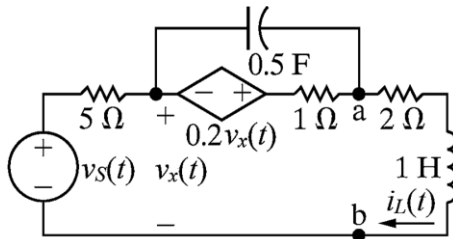
- (c) Consider the second order relaxed network shown with  $v_s(t) = 20u(t)V$ .



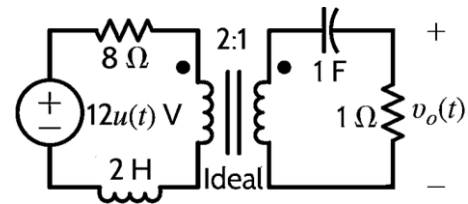- Compute the  $s$ -Domain Thevenin impedance  $\mathbf{Z}_{TH}(s)$  and Thevenin voltage  $\mathbf{V}_{TH}(s)$ .
  - Use the  $s$ -Domain Thevenin equivalent network found in part (i) to compute the  $s$ -Domain load current  $\mathbf{I}_L(s)$ . Do not take the inverse Laplace transform of  $\mathbf{I}_L(s)$ .
- (d) Consider the second order relaxed ideal transformer network shown.



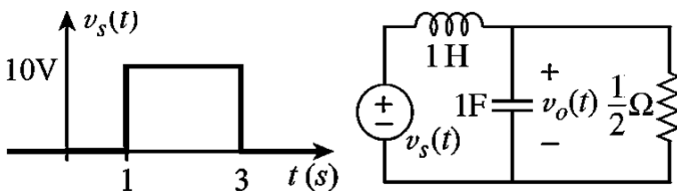- Reflect the primary  $s$ -Domain equivalent network to the secondary of the transformer and compute  $\mathbf{V}_o(s)$ , the Laplace Transform of the complete response voltage  $v_o(t)$  for  $t > 0^-$ .
  - Compute the complete response voltage  $v_o(t)$  for  $t > 0^-$ .
- (e) Consider the 2<sup>nd</sup> order relaxed network shown below with  $v_s(t)$  depicted by the plot.



- Compute  $\mathbf{V}_s(s)$ , the Laplace Transform of the source voltage  $v_s(t)$ .
- Compute  $\mathbf{V}_o(s)$ , the Laplace Transform of the complete voltage response  $v_o(t)$ .
- Compute the complete voltage response  $v_o(t)$  for  $t > 0^-$ . Identify the transient response portion  $v_{o,TR}(t)$  and steady state response portion  $v_{o,SS}(t)$  of  $v_o(t)$ . Is the transient response un-damped, under-damped, critically-damped, or over-damped?