




Lecture #1(a): Poly-Phase Networks

Theory

ECE 20200: Linear Circuit Analysis II
Steve Naumov (Instructor)

Overview

- ▶ **Balanced poly-phase networks:** A network comprising a **balanced poly-phase source** and a **balanced poly-phase load**
- ▶ **Balanced Poly-phase source:** A voltage source that generates k sinusoidal voltage waveforms with these characteristics:
 - ▶ Each waveform's **operating frequency is the same**
 - ▶ Each waveform's **magnitude is the same**
 - ▶ **Consecutive waveform pairs** are **$(360/k)$ degrees apart.**
- ▶ **Balanced Poly-phase load:** A load that draws the same power from each voltage waveform
- ▶ Most common poly-phase network is a **three-phase network**

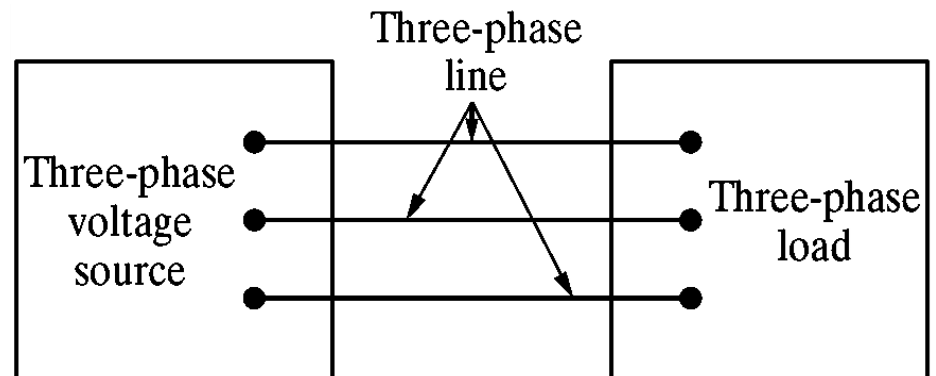

Overview (cont'd)

- ▶ Why study balanced poly-phase networks?
 - ▶ Nearly all electric power is generated and distributed using balanced poly-phase networks.
 - ▶ Instantaneous power is constant (not pulsating) and results in uniform power transmission and less vibration in the poly-phase generators.
 - ▶ For the same amount of power, a poly-phase network is more economical than a single-phase counterpart.


Lecture #1(a) Poly-Phase Networks

Theory

Balanced 3-Phase Voltage Sources

Balanced 3-Phase Voltages

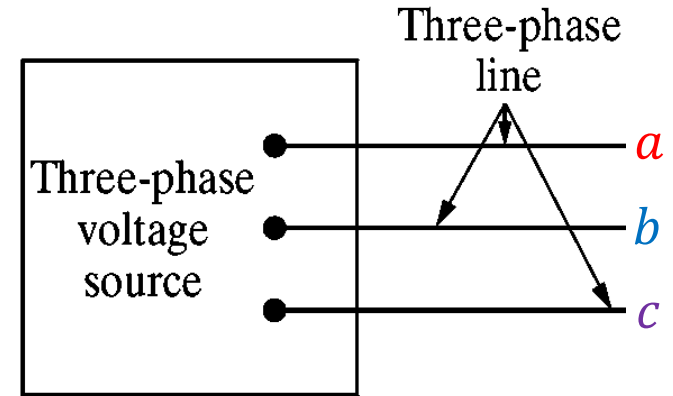- ▶ A **balanced 3-phase source** generates 3 sinusoidal voltages:
 - ▶ Each voltage's magnitude and **frequency is V_ϕ volts and f_ϕ Hz**
 - ▶ Consecutive pairs of voltages are **$360^\circ/3 = 120^\circ$** apart.



- ▶ Each voltage is referred to as **V_a** (a-phase voltage), **V_b** (b-phase voltage), and **V_c** (c-phase voltage)
- ▶ **V_b** and **V_c** relate to **V_a** with respect to phase in one of two ways:
 - ▶ **Positive Phase Sequence (a-b-c)**
 - ▶ $V_a = V_\phi e^{j\theta_{\phi_V}}$ $V_b = (e^{-j120^\circ})V_a$ $V_c = (e^{+j120^\circ})V_a$
 - ▶ **Negative Phase Sequence (a-c-b)**
 - ▶ $V_a = V_\phi e^{j\theta_{\phi_V}}$ $V_b = (e^{+j120^\circ})V_a$ $V_c = (e^{-j120^\circ})V_a$

▶

Balanced 3-Phase Voltages(cont'd)

- Independent of the phase sequence, an important characteristic of balanced 3-phase voltages is that:

$$\mathbf{V}_a + \mathbf{V}_b + \mathbf{V}_c = 0V$$

- Proof (a-b-c sequence)

$$\mathbf{V}_\phi e^{j\theta\phi_V} + \mathbf{V}_\phi e^{j(\theta\phi_V - 120^\circ)} + \mathbf{V}_\phi e^{j(\theta\phi_V + 120^\circ)} = 0V$$

$$(1 + e^{-j120^\circ} + e^{+j120^\circ})\mathbf{V}_a = 0V$$


$$(0)\mathbf{V}_a = 0V$$

- Proof (a-c-b sequence)

$$\mathbf{V}_\phi e^{j\theta\phi_V} + \mathbf{V}_\phi e^{j(\theta\phi_V + 120^\circ)} + \mathbf{V}_\phi e^{j(\theta\phi_V - 120^\circ)} = 0V$$

$$(1 + e^{+j120^\circ} + e^{-j120^\circ})\mathbf{V}_a = 0V$$

$$(0)\mathbf{V}_a = 0V$$

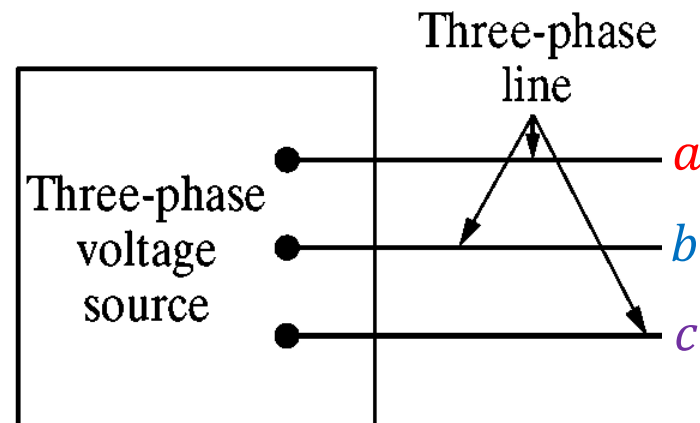


Balanced 3-phase Voltages

Source Topologies

- Two ideal 3-phase voltage source topologies exist


{Wye-(Y), Tee-(T), Star-(*)} Topology

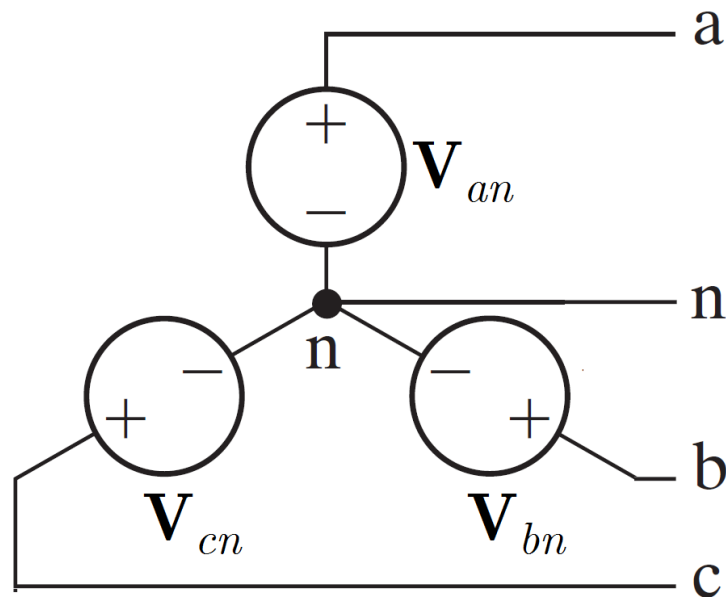

$\{V_{an}, V_{bn}, V_{cn}\}$ called {phase, line-to-neutral} voltages

$$V_{an} + V_{bn} + V_{cn} = 0V$$

{Delta-(Δ), Pie-(π)} Topology

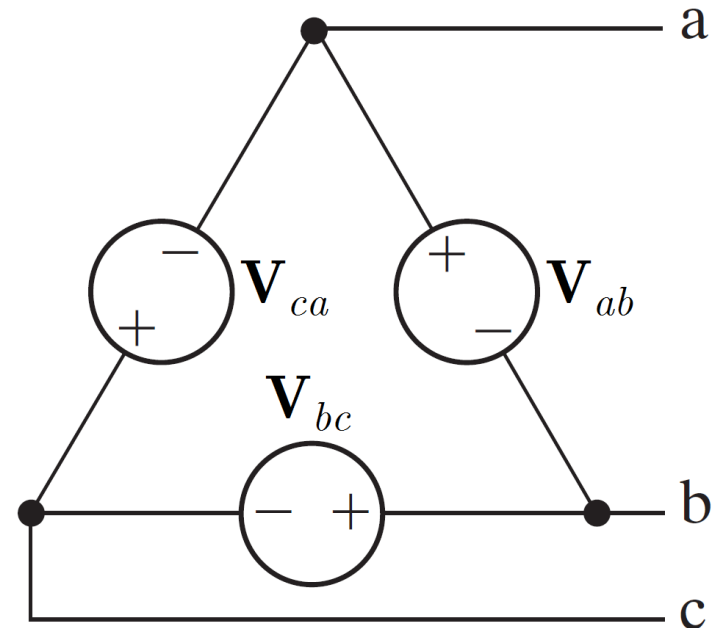

$\{V_{ab}, V_{bc}, V_{ca}\}$ called {line, line-to-line} voltages

$$V_{ab} + V_{bc} + V_{ca} = 0V$$

Transforming 3-Phase Voltages

Wye-(Y) → Delta-(Δ) Transformations

- Given a **a-b-c phase sequence**, balanced 3-phase phase voltages \mathbf{V}_{an} , \mathbf{V}_{bn} , and \mathbf{V}_{cn} , the line-to-line voltage \mathbf{V}_{ab} can be computed as follows:

Applying KVL:


$$\mathbf{V}_{ab} = \mathbf{V}_{an} - \mathbf{V}_{bn}$$

$$\mathbf{V}_{ab} = V_{\phi} e^{j\theta_{\phi_V}} - V_{\phi} e^{j(\theta_{\phi_V} - 120^\circ)}$$

$$\mathbf{V}_{ab} = V_{\phi} e^{j\theta_{\phi_V}} - V_{\phi} e^{j\theta_{\phi_V}} e^{-j120^\circ}$$

$$\mathbf{V}_{ab} = (1 - e^{-j120^\circ}) V_{\phi} e^{j\theta_{\phi_V}}$$
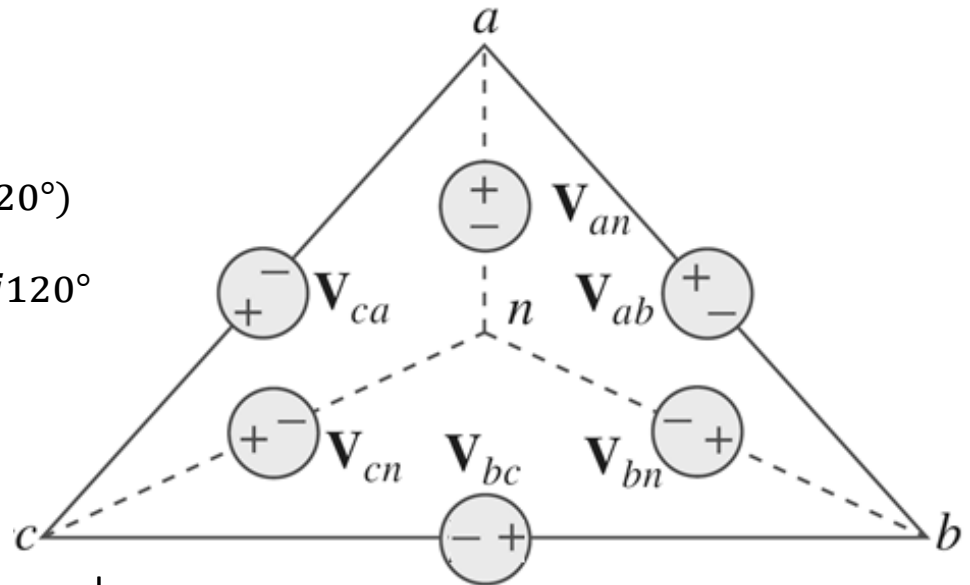
$$\boxed{\mathbf{V}_{ab} = (\sqrt{3} e^{+j30^\circ}) \mathbf{V}_{an}}$$



- Since line-to-line voltages \mathbf{V}_{bc} and \mathbf{V}_{ca} are balanced, we can compute them in terms of \mathbf{V}_{ab} :

$$\boxed{\mathbf{V}_{bc} = (e^{-j120^\circ}) \mathbf{V}_{ab}}$$

$$\boxed{\mathbf{V}_{ca} = (e^{+j120^\circ}) \mathbf{V}_{ab}}$$

How do equations on this slide change for a negative phase sequence Y source?

Transforming 3-Phase Voltages

Delta-(Δ) \rightarrow Wye-(Y) Transformations

- Given an **a-b-c sequence**, balanced 3-phase line-to-line voltages \mathbf{V}_{ab} , \mathbf{V}_{bc} , and \mathbf{V}_{ca} , the a-phase voltage \mathbf{V}_{an} can be computed as follows:


$$\mathbf{V}_{an} = \mathbf{V}_{ab} / \left(\sqrt{3} e^{+j30^\circ} \right) = V_\phi e^{j\theta_{\phi_V}}$$

$$\mathbf{V}_{an} = \mathbf{V}_{ab} \left[\left(\sqrt{3}/3 \right) e^{-j30^\circ} \right] = V_\phi e^{j\theta_{\phi_V}}$$

- Since the phase voltages \mathbf{V}_{bn} and \mathbf{V}_{cn} are balanced, we can compute them in terms of a-phase voltage \mathbf{V}_{ab} :

$$\mathbf{V}_{bc} = \left(e^{-j120^\circ} \right) \mathbf{V}_{ab}$$
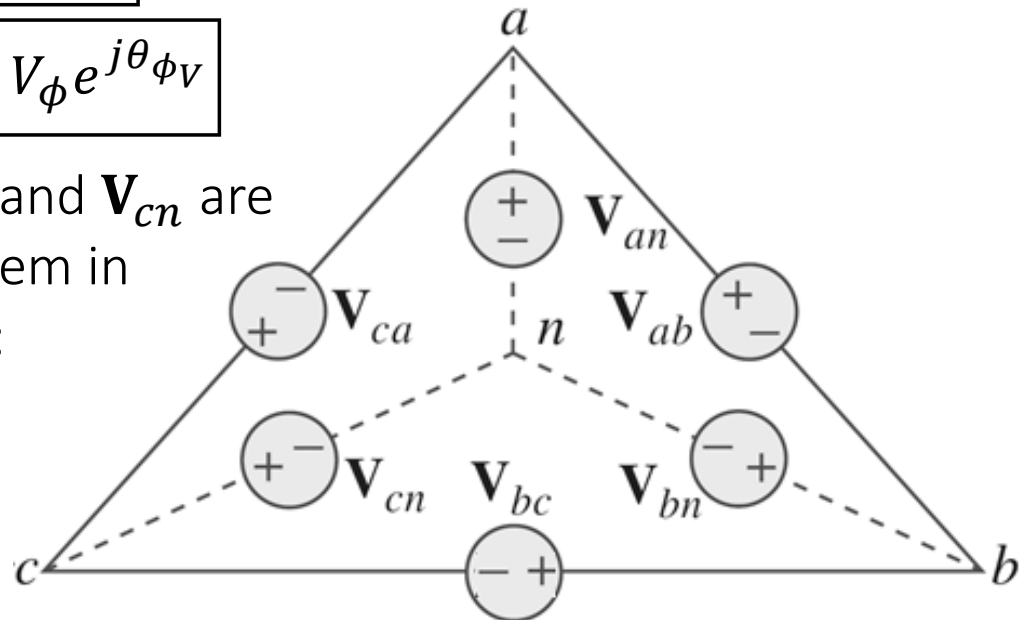
$$\mathbf{V}_{ca} = \left(e^{+j120^\circ} \right) \mathbf{V}_{ab}$$



How do equations on this slide change
for a negative phase sequence Y source?

Lecture #1(a) Poly-Phase Networks


Theory

Delta (Pie) and Wye (Tee) Impedance Networks


Wye-(Y) and Delta-(Δ) Impedance Networks

- There are two important load types for poly-phase networks

{Wye-(Y), Tee-(T), Star-(*)} Topology

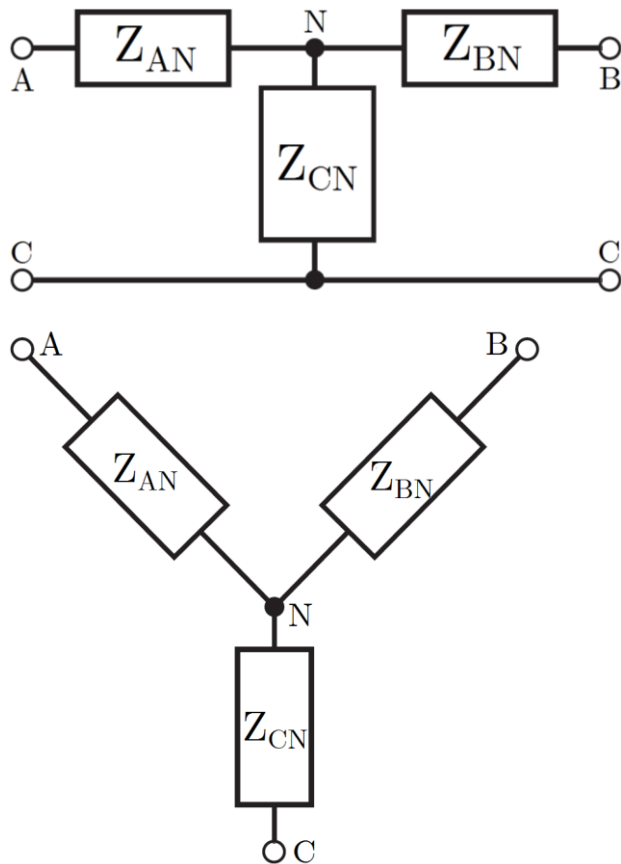

Delta-(Δ) or Pie-(π) Topology

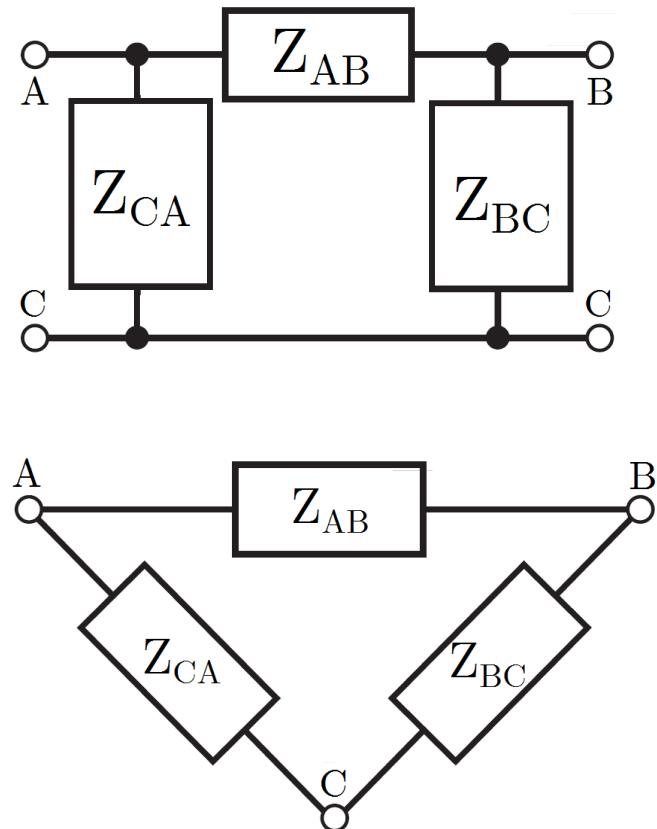

Wye-(Y) and Delta-(Δ) Impedance Networks


Transforming Impedances of Unbalanced Loads

- ▶ Transforming Wye-Y \rightarrow Delta- Δ Impedances

$$\begin{aligned} Z_{AB} &= \frac{Z_{AN}Z_{BN} + Z_{BN}Z_{CN} + Z_{CN}Z_{AN}}{Z_{CN}} \\ Z_{BC} &= \frac{Z_{AN}Z_{BN} + Z_{BN}Z_{CN} + Z_{CN}Z_{AN}}{Z_{AN}} \\ Z_{CA} &= \frac{Z_{AN}Z_{BN} + Z_{BN}Z_{CN} + Z_{CN}Z_{AN}}{Z_{BN}} \end{aligned}$$

- ▶ Transforming Delta- $\Delta \rightarrow$ Wye-Y Impedances

$$\begin{aligned} Z_{AN} &= \frac{Z_{AB}Z_{CA}}{Z_{AB} + Z_{BC} + Z_{CA}} \\ Z_{BN} &= \frac{Z_{BC}Z_{AB}}{Z_{AB} + Z_{BC} + Z_{CA}} \\ Z_{CN} &= \frac{Z_{CA}Z_{BC}}{Z_{AB} + Z_{BC} + Z_{CA}} \end{aligned}$$

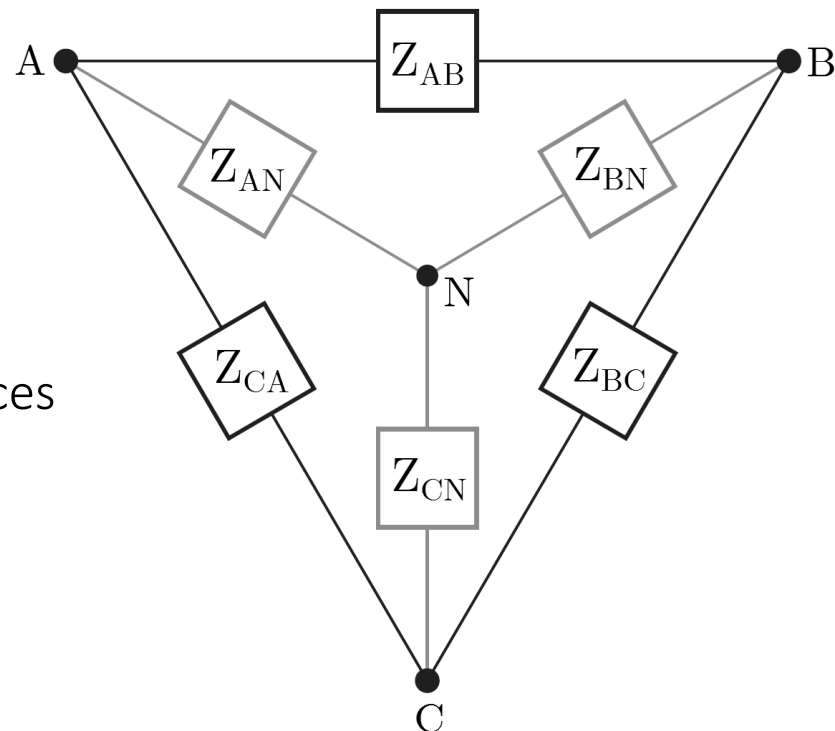

Balanced 3-Phase Loads

Voltage and Current Transformations

- ▶ **Balanced Poly-phase load:** Load draws same power from each phase
 - ▶ To meet requirement, the each load impedance must be equal!
 - ▶ A Wye-Y load is balanced when $Z_{AN} = Z_{BN} = Z_{CN} = Z_Y$
 - ▶ A Delta- Δ load is balanced when $Z_{AB} = Z_{BC} = Z_{CA} = Z_{\Delta}$

- ▶ **Transforming Balanced Loads**

- ▶ Wye-Y \rightarrow Delta- Δ


$$Z_{\Delta} = \frac{Z_Y Z_Y + Z_Y Z_Y + Z_Y Z_Y}{Z_Y}$$

$$\boxed{Z_{\Delta} = 3Z_Y}$$

- ▶ Delta- $\Delta \rightarrow$ Wye-Y Loads


$$Z_Y = \frac{Z_{\Delta} Z_{\Delta}}{Z_{\Delta} + Z_{\Delta} + Z_{\Delta}}$$

$$\boxed{Z_Y = Z_{\Delta}/3}$$

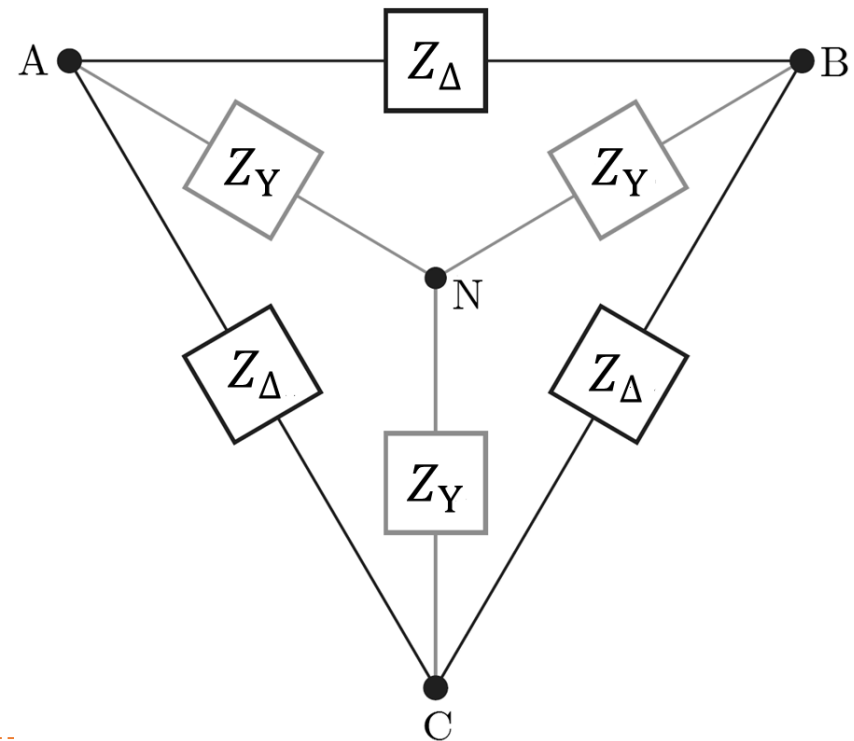

Overview of 3-Phase Networks

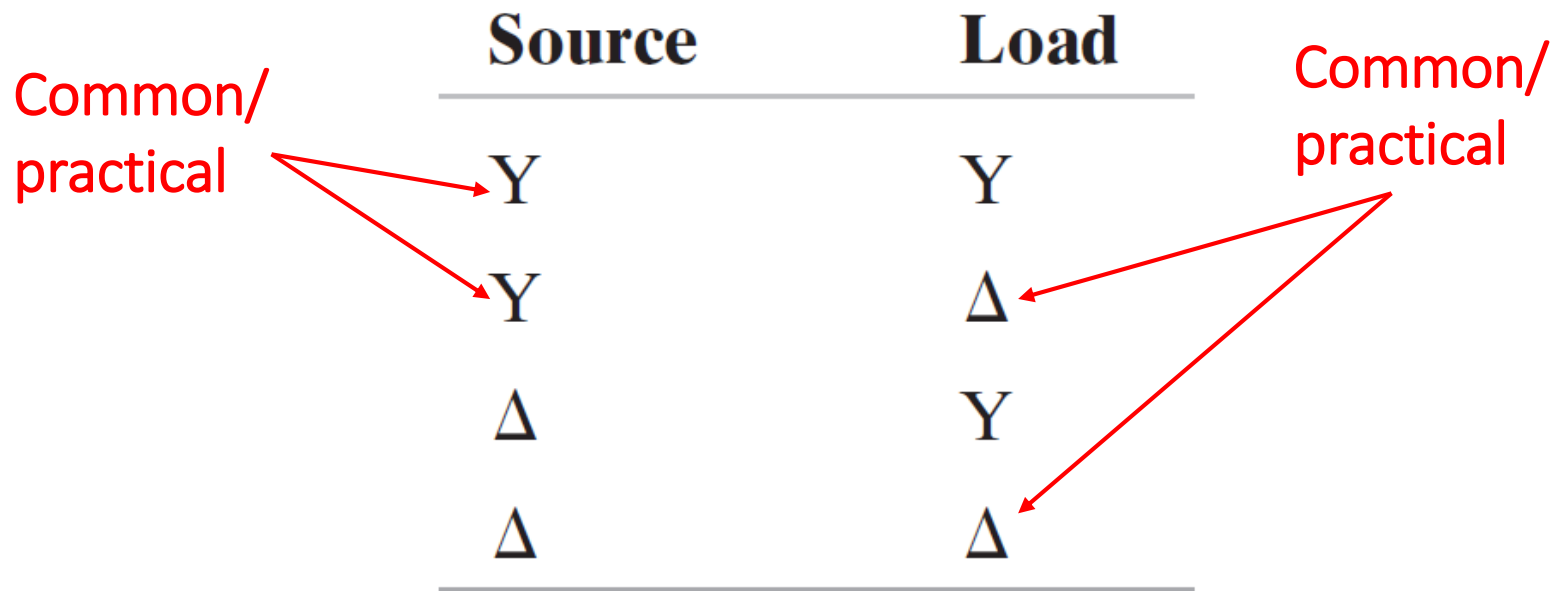- ▶ Since 3-phase sources and loads can each have either a Wye-Y or Delta-D topology, four combinations of sources and loads exist
- ▶ Configurations of 3-phase networks




Lecture #1(a) Poly-Phase Networks

Theory

The Balanced Y-Y Network

The General 3-Phase Y-Y Network

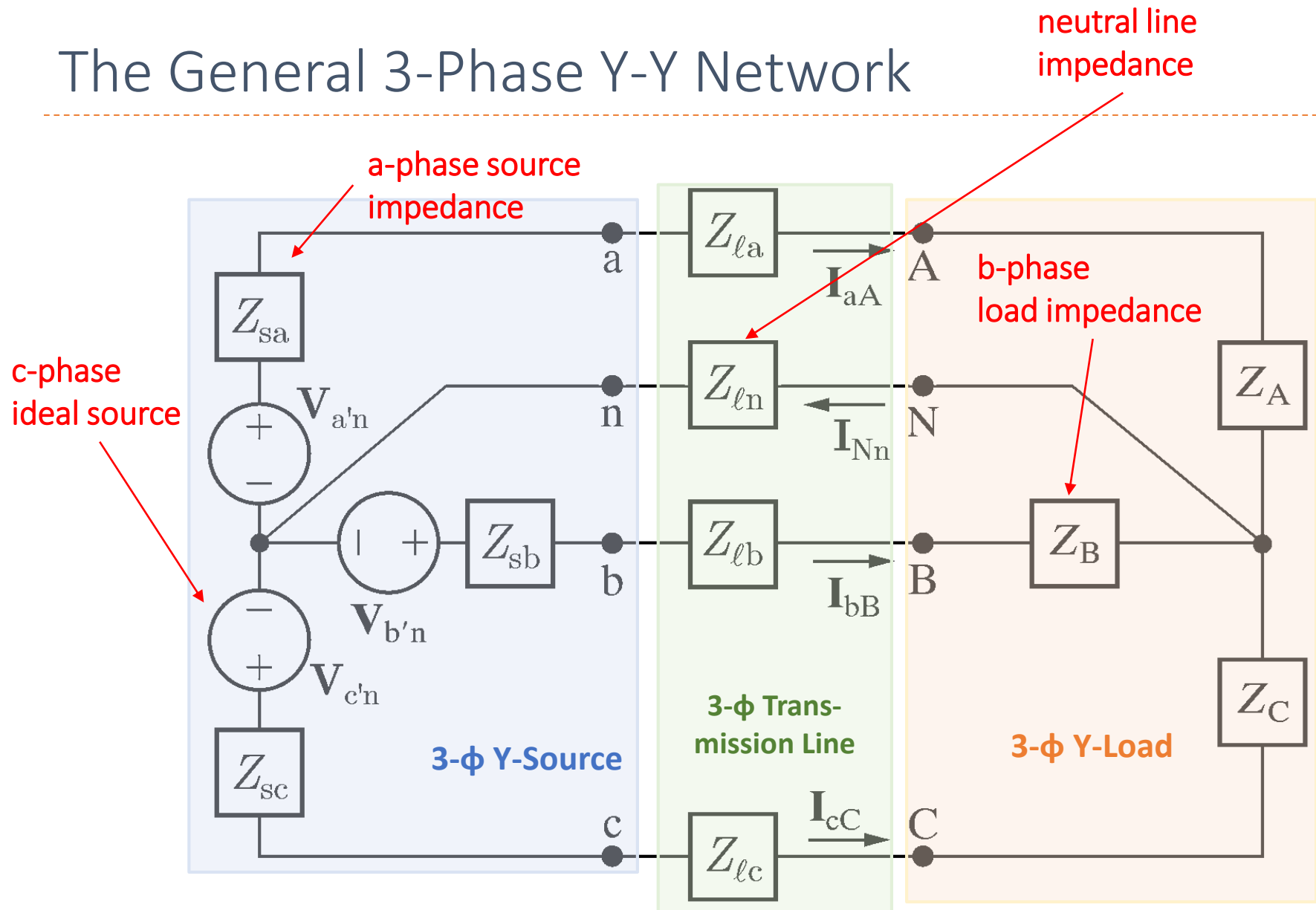

A Balanced Y-Y 3-phase Network: Analysis

- Perform nodal analysis @ at node N:

$$\frac{\mathbf{V}_N - \mathbf{V}_{a'n}}{Z_S + Z_\ell + Z_Y} + \frac{\mathbf{V}_N - \mathbf{V}_{b'n}}{Z_S + Z_\ell + Z_Y} + \frac{\mathbf{V}_N - \mathbf{V}_{c'n}}{Z_S + Z_\ell + Z_Y} + \frac{\mathbf{V}_N - 0V}{Z_{\ell n}} = 0A$$

$$\mathbf{V}_N \left[\frac{3}{Z_\phi} + \frac{1}{Z_{\ell n}} \right] = \frac{1}{Z_\phi} [\mathbf{V}_{a'n} + \mathbf{V}_{b'n} + \mathbf{V}_{c'n}] \rightarrow \mathbf{V}_N \left[\frac{3}{Z_\phi} + \frac{1}{Z_{\ell n}} \right] = \frac{1}{Z_\phi} [0V]$$

$$\boxed{\mathbf{V}_N = 0V}$$


- Major conclusions:

$$\boxed{\mathbf{V}_{Nn} = 0V}$$

$$\boxed{\mathbf{I}_{Nn} = 0A = \mathbf{I}_{aA} + \mathbf{I}_{bB} + \mathbf{I}_{cC}}$$

- Consequence:

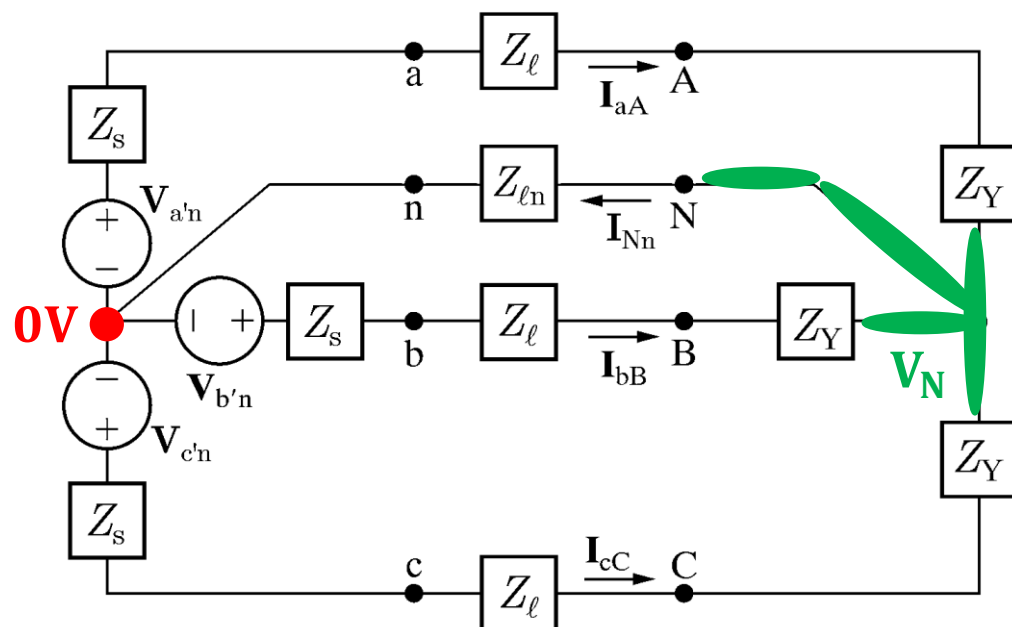- Can remove neutral line from this configuration or can replace neutral line with a short between nodes {n,N}




A Balanced Y-Y 3-phase Network

Preferred Analysis Method: Single-phase equivalent network

▶ Single-phase equivalent network:

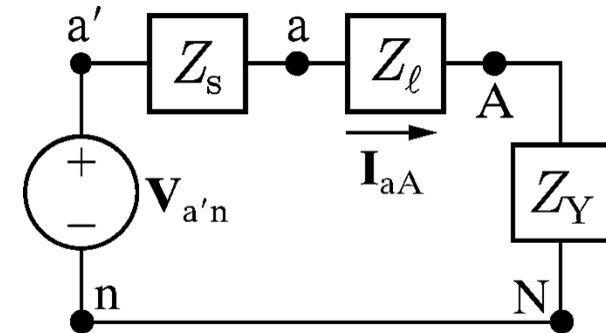- ▶ An equivalent network for a single phase (e.g. a-phase) that gives same V-I values on previous slide.



- ▶ The a-phase line current \mathbf{I}_{aA} : $\mathbf{I}_{aA} = \mathbf{V}_{a'n}/Z_\phi$
- ▶ The a-phase load voltage \mathbf{V}_{AN} : $\mathbf{V}_{AN} = \mathbf{I}_{aA}Z_Y$
- ▶ The a-phase terminal source voltage \mathbf{V}_{an} :

$$\mathbf{V}_{an} = V_{a'n} - \mathbf{I}_{aA}Z_s = \mathbf{I}_{aA}(Z_\ell + Z_Y) = (\mathbf{V}_{a'n}/Z_\phi)(Z_\ell + Z_Y)$$

- ▶ Line-to-line load voltages (\mathbf{V}_{AB} , \mathbf{V}_{BC} , \mathbf{V}_{CA}) and the line-to-line terminal source voltages (\mathbf{V}_{ab} , \mathbf{V}_{bc} , \mathbf{V}_{ca}) can be derived using conversion factor ($\sqrt{3}e^{\pm j30^\circ}$) and the source's phase sequence
- ▶ For example (assuming a-b-c sequence):

$$\mathbf{V}_{AB} = (\sqrt{3}e^{j30^\circ})\mathbf{V}_{AN}$$

$$\mathbf{V}_{ab} = (\sqrt{3}e^{j30^\circ})\mathbf{V}_{an}$$

Lecture #1(a) Poly-Phase Networks

Theory

Analysis of Balanced 3-Phase Sources

Balanced 3-Phase Networks

Y-Connected Sources

- ▶ Ideal a-Phase Source Voltage: $\mathbf{V}_{a'n}$
- ▶ Transmission Line Current: \mathbf{I}_{aA}
- ▶ Other values are computed as follows:

- ▶ a-Phase Current ($\mathbf{I}_{na'}$):

$$\boxed{\mathbf{I}_{na'} = \mathbf{I}_{aA}}$$

- ▶ a-Phase Terminal Voltage (\mathbf{V}_{an}):


$$\boxed{\mathbf{V}_{an} = \mathbf{V}_{a'n} - \mathbf{I}_{aA}Z_s}$$

- ▶ a-to-b Line-to-Line Voltage (\mathbf{V}_{ab}): Using KVL...

$$\mathbf{V}_{ab} = \mathbf{V}_{an} - \mathbf{V}_{bn} = \mathbf{V}_{an} - \mathbf{V}_{an}e^{\mp j120^\circ} = (1 - e^{\mp j120^\circ})\mathbf{V}_{an}$$

$$\boxed{\mathbf{V}_{ab} = (\sqrt{3}e^{j\pm 30^\circ})\mathbf{V}_{an} = (\sqrt{3}e^{\pm j30^\circ})(\mathbf{V}_{a'n} - \mathbf{I}_{aA}Z_s)}$$

- ▶ a-to-b Line-to-Line Current (\mathbf{I}_{ab}): N/A

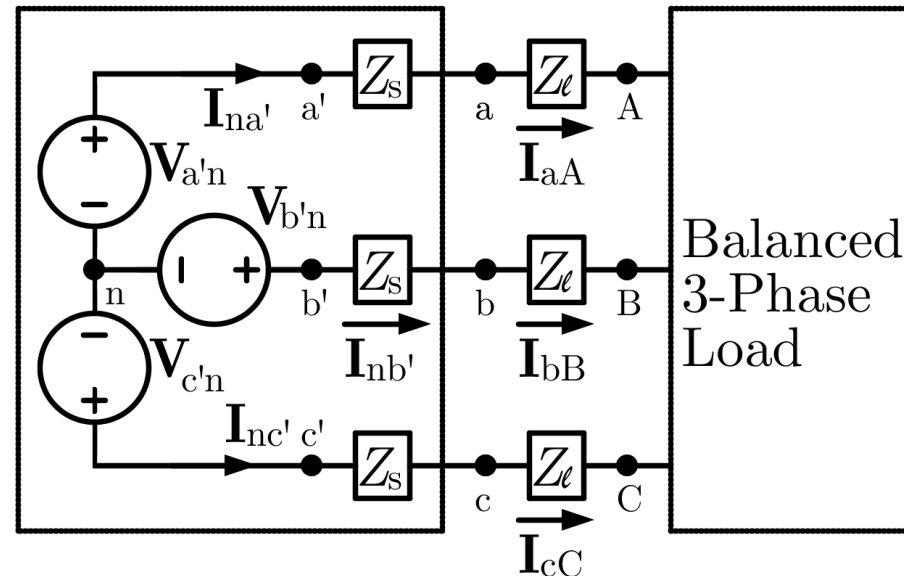

Balanced 3-Phase Networks

Δ -Connected Sources

- ▶ Ideal a-Phase Source Voltage: $\mathbf{V}_{a'b}$
- ▶ Transmission Line Current: \mathbf{I}_{aA}
- ▶ Other values are computed as follows

- ▶ a-to-b Terminal Line-to-Line Voltage (\mathbf{V}_{ab}):

$$\mathbf{V}_{ab} = \mathbf{V}_{a'b} - \mathbf{I}_{ba}Z_s = (\sqrt{3}e^{\pm j30^\circ})\mathbf{V}_{an}$$

- ▶ a-Phase Voltage (\mathbf{V}_{ab}):


$$\mathbf{V}_{ab} = \mathbf{V}_{a'b} - \mathbf{I}_{ba}Z_s = (\sqrt{3}e^{\pm j30^\circ})\mathbf{V}_{an}$$

- ▶ a-Phase Current (\mathbf{I}_{ba}): Use KCL @ (a)

$$\mathbf{I}_{aA} = \mathbf{I}_{ba} - \mathbf{I}_{ac} = \mathbf{I}_{ba} - \mathbf{I}_{ba}e^{\pm j120^\circ} = (1 - e^{\pm j120^\circ})\mathbf{I}_{ba} = (\sqrt{3}e^{\mp j30^\circ})\mathbf{I}_{ba}$$

$$\mathbf{I}_{ba} = \mathbf{I}_{aA}/(\sqrt{3}e^{\mp j30^\circ})$$

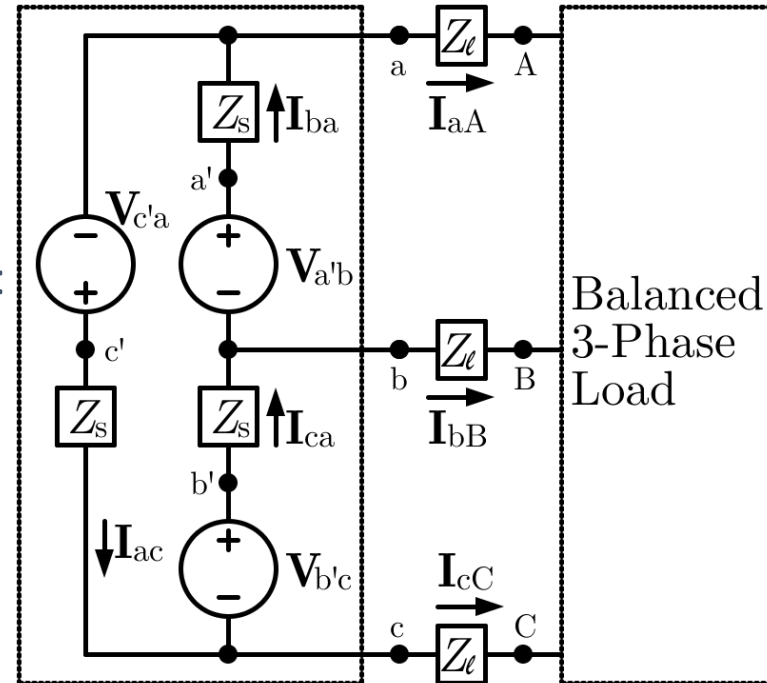- ▶ b-to-a Line-to-Line Current (\mathbf{I}_{ba}): $\mathbf{I}_{ba} = (\mathbf{V}_{a'b} - \mathbf{V}_{ab})/Z_s = \mathbf{I}_{aA}/(\sqrt{3}e^{\mp j30^\circ})$



Lecture #1(a) Poly-Phase Networks

Theory

Analysis of Balanced 3-Phase Loads

Balanced 3-Phase Networks

Y-Connected Loads

- ▶ Transmission Line Current: \mathbf{I}_{aA}
- ▶ Other related values can be computed as follows

- ▶ A-Phase Current (\mathbf{I}_{AN}):

$$\boxed{\mathbf{I}_{AN} = \mathbf{I}_{aA}}$$

- ▶ A-Phase Voltage (\mathbf{V}_{AN}):


$$\boxed{\mathbf{V}_{AN} = \mathbf{I}_{AN} Z_Y = \mathbf{I}_{aA} Z_Y}$$

- ▶ A-to-B Line-to-Line Voltage \mathbf{V}_{AB} : Using KVL...

$$\mathbf{V}_{AB} = \mathbf{V}_{AN} - \mathbf{V}_{BN} = \mathbf{V}_{AN} - \mathbf{V}_{AN} e^{\mp j120^\circ} = (1 - e^{\mp j120^\circ}) \mathbf{V}_{AN}$$

$$\boxed{\mathbf{V}_{AB} = (\sqrt{3} e^{\pm j30^\circ}) \mathbf{V}_{AN}}$$

- ▶ A-to-B Line-to-Line Current: $\mathbf{I}_{AB} \rightarrow N/A$

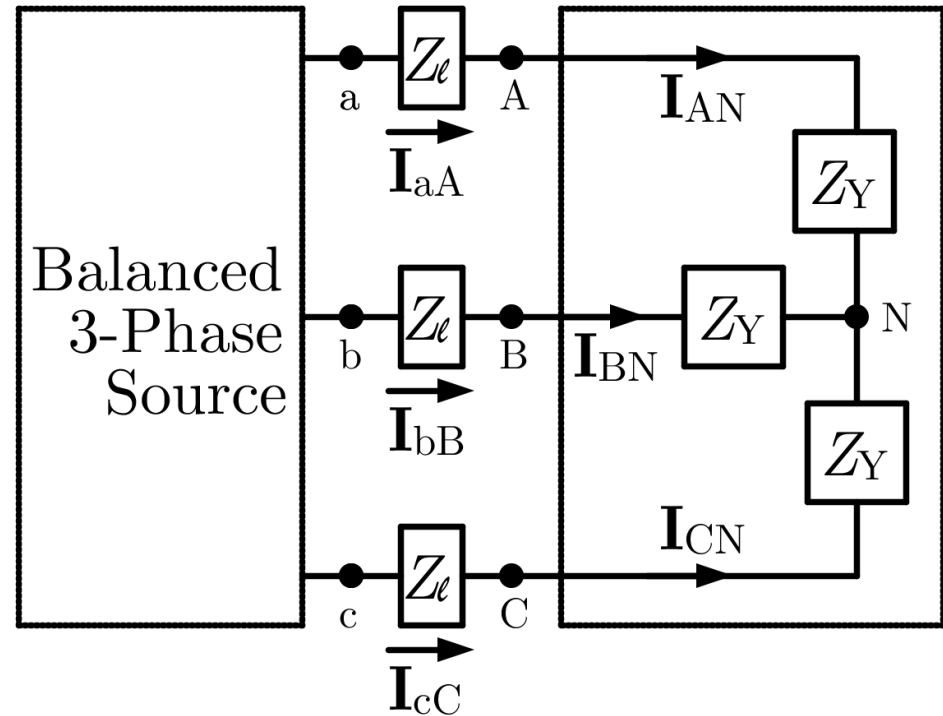

Balanced 3-Phase Networks

Δ -Connected Loads

- ▶ Transmission line current: \mathbf{I}_{aA}
- ▶ Other related values can be computed as follows

- ▶ A-Phase Voltage (\mathbf{V}_{AB}):

$$\mathbf{V}_{AB} = (\sqrt{3}e^{\pm j30^\circ})\mathbf{V}_{AN}$$

- ▶ A-to-B Line-to-Line Voltage (\mathbf{V}_{AB}):

$$\mathbf{V}_{AB} = (\sqrt{3}e^{\pm j30^\circ})\mathbf{I}_{aA}(Z_\Delta/3)$$

- ▶ A-Phase Current (\mathbf{I}_{AB}): Use KCL @ (A)

$$\mathbf{I}_{aA} = \mathbf{I}_{AB} - \mathbf{I}_{CA} = \mathbf{I}_{AB} - \mathbf{I}_{AB}e^{\pm j120^\circ} = (1 - e^{\pm j120^\circ})\mathbf{I}_{AB} = (\sqrt{3}e^{\mp j30^\circ})\mathbf{I}_{AB}$$

$$\mathbf{I}_{AB} = \mathbf{V}_{AB}/Z_\Delta = \mathbf{I}_{aA}/(\sqrt{3}e^{\mp j30^\circ})$$

- ▶ A-to-B Line-to-Line Current (\mathbf{I}_{AB}): $\mathbf{I}_{AB} = \mathbf{V}_{AB}/Z_\Delta = \mathbf{I}_{aA}/(\sqrt{3}e^{\mp j30^\circ})$

