



Lecture #2(a): Magnetically Coupled Networks *Theory*

ECE 20200: Linear Circuit Analysis II
Steve Naumov (Instructor)

Lecture Overview

- ▶ This set of slides presented the following
 - ▶ Mutual Inductance
 - ▶ Defining Mutual Conductance
 - ▶ Dotted Sign Convention
 - ▶ Energy Considerations
 - ▶ Analysis of Magnetically Coupled Networks
 - ▶ The Linear Transformer
 - ▶ SSS Analysis
 - ▶ Reflected Impedances
 - ▶ The Ideal Transformer
 - ▶ Element Constraints
 - ▶ Dot Convention
 - ▶ SSS Analysis
 - ▶ Reflecting Elements

Lecture #2(a): Magnetically Coupled Networks *Theory*

Mutual Inductance

Inductance Review

- ▶ When a current $i_L(t)$ passes through a coiled wire having N turns, a magnetic flux $\phi(t)$ is produced in a direction determined by the RHL
- ▶ The current $i_L(t)$ is related to the magnetic flux $\phi(t)$ as follows


$$\phi(t) = \mathcal{P}Ni_L(t)$$

- ▶ $i_L(t)$: Current through coil measured in Amperes
- ▶ $\phi(t)$: Magnetic flux measured in Webbers
- ▶ N : Number of turns of the coil
- ▶ \mathcal{P} : Permeance of space occupied by ϕ . Depends on magnetic properties of space.
- ▶ The flux $\phi(t)$ intercepts/links the N turns. This effect is represented by flux linkage $\lambda(t)$ as

$$\lambda(t) = N\phi(t) \text{ (Webber-Turns)}$$

- ▶ Substituting $\phi(t)$ in the above relation yields
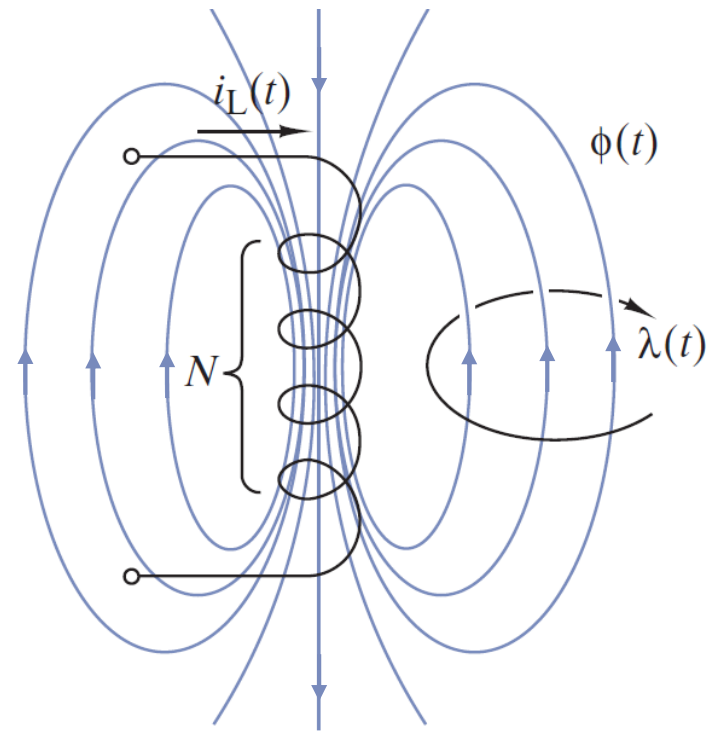
$$\lambda(t) = N\phi(t) = N\mathcal{P}Ni_L(t) = \mathcal{P}N^2i_L(t)$$



Inductance Review (cont'd)

- ▶ The flux linkage $\lambda(t)$ is proportional to the current $i_L(t)$ through the coil

$$\lambda(t) = \mathcal{P}N^2 i_L(t)$$

- ▶ The proportionality constant $L = \mathcal{P}N^2$ is known as the **self-inductance L** of the coil (measured in Henry's). Therefore,


$$\lambda(t) = Li_L(t)$$

- ▶ By Faraday's Law, the voltage across the N turns of the coil can be expressed as follows

$$v_L(t) = \frac{d\lambda(t)}{dt}$$

- ▶ Therefore, the v - i relation of a coil having a constant inductance $L = \mathcal{P}N^2$ is given by
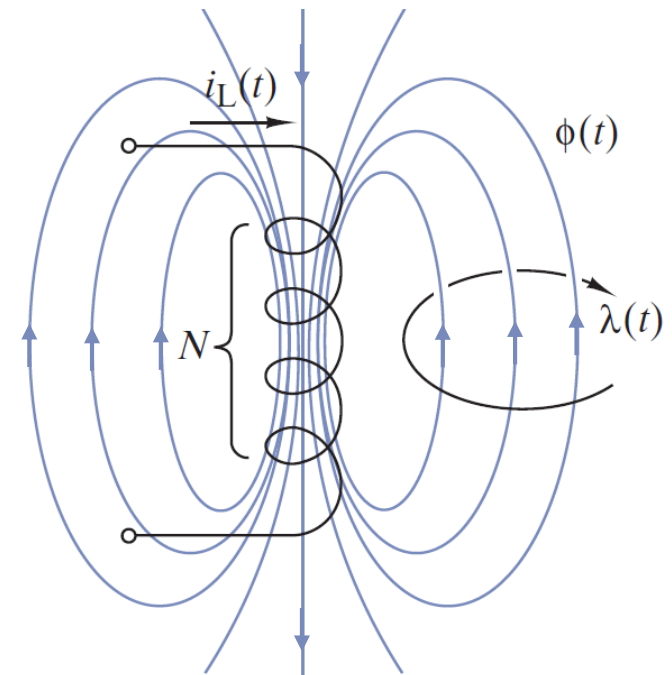
$$v_L(t) = \frac{d\lambda(t)}{dt} = L \frac{di_L(t)}{dt}$$



Decoupled (Non-Neighboring) Coils

▶ Coil with N_1 Turns

- ▶ Current $i_1(t)$ passes through the coil having N_1 turns and produces a magnetic flux $\phi_1(t)$

$$\phi_1(t) = \mathcal{P}_1 N_1 i_1(t)$$

- ▶ Flux $\phi_1(t)$ intercepts or links the N_1 . The flux linkage $\lambda_1(t)$ is given by
$$\lambda_1(t) = N_1 \phi_1(t)$$


- ▶ By Faraday's Law, voltage $v_1(t)$ and flux linkage $\lambda_1(t)$ relate as follows

$$v_1(t) = \frac{d\lambda_1(t)}{dt} = N_1 \frac{d\phi_1(t)}{dt} = [\mathcal{P}_1 N_1 N_1] \frac{di_1(t)}{dt} = [\mathcal{P}_1 N_1^2] \frac{di_1(t)}{dt} = L_1 \frac{di_1(t)}{dt}$$

▶ Coil with N_2 Turns

- ▶ Similar equations can be developed

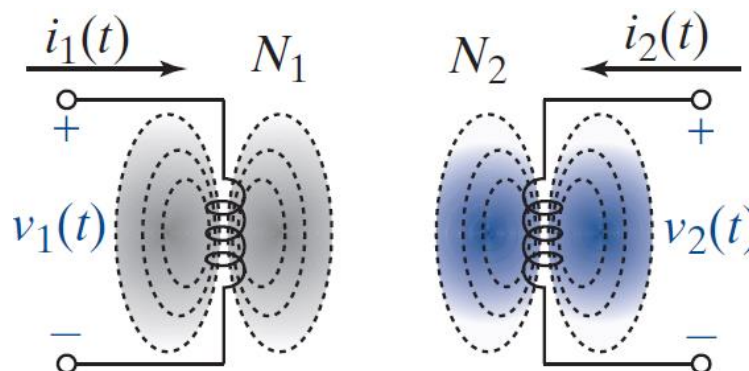- ▶ Since the two coils are not in close proximity, their fluxes do not interact



Magnetically Coupled (Neighboring) Coils

- ▶ The total magnetic flux for each for each coupled coil is given below

Coil With Inductance L_1

$$\phi_1 = \phi_{1 \rightarrow 1} + \phi_{2 \rightarrow 1} = \mathcal{P}_1 N_1 i_1 \text{ (total flux)}$$

$$\phi_{1 \rightarrow 1} = \mathcal{P}_{1 \rightarrow 1} N_1 i_1 \text{ (self term)}$$

$$\phi_{2 \rightarrow 1} = \mathcal{P}_{2 \rightarrow 1} N_2 i_2 \text{ (coupling term)}$$


Coil With Inductance L_2

$$\phi_2 = \phi_{2 \rightarrow 2} + \phi_{1 \rightarrow 2} = \mathcal{P}_2 N_2 i_2 \text{ (total flux)}$$

$$\phi_{2 \rightarrow 2} = \mathcal{P}_{2 \rightarrow 2} N_2 i_2 \text{ (self term)}$$

$$\phi_{1 \rightarrow 2} = \mathcal{P}_{1 \rightarrow 2} N_1 i_1 \text{ (coupling term)}$$

- ▶ $\phi_{1 \rightarrow 1}$: Portion of total flux ϕ_1 caused by i_1 linking only the N_1 turns of L_1
- ▶ $\phi_{2 \rightarrow 1}$: Portion of total flux ϕ_1 caused by i_2 linking N_2 turns of L_2 to N_1 turns of L_1
- ▶ $\phi_{2 \rightarrow 2}$: Portion of total flux ϕ_2 caused by i_2 linking only the N_2 turns of L_2
- ▶ $\phi_{1 \rightarrow 2}$: Portion of total flux ϕ_2 caused by i_1 linking N_1 turns of L_1 to N_2 turns of L_2

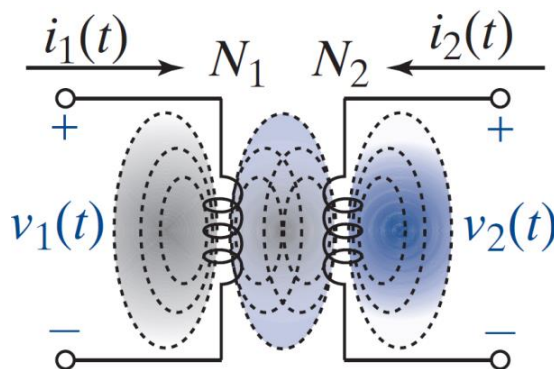

Magnetically Coupled (Neighboring) Coils (cont'd)

- ▶ The flux linkage for each coupled coil is given below

Coil With Inductance L_1

$$\lambda_1 = \lambda_{1 \rightarrow 1} + \lambda_{2 \rightarrow 1} = N_1 \phi_1 \text{ (total link)}$$

$$\lambda_{1 \rightarrow 1} = N_1 \phi_{1 \rightarrow 1} \text{ (self term)}$$

$$\lambda_{2 \rightarrow 1} = N_1 \phi_{2 \rightarrow 1} \text{ (coupling term)}$$


Coil With Inductance L_2

$$\lambda_2 = \lambda_{2 \rightarrow 2} + \lambda_{1 \rightarrow 2} = N_2 \phi_2 \text{ (total link)}$$

$$\lambda_{2 \rightarrow 2} = N_2 \phi_{2 \rightarrow 2} \text{ (self term)}$$

$$\lambda_{1 \rightarrow 2} = N_2 \phi_{1 \rightarrow 2} \text{ (coupling term)}$$

- ▶ $\lambda_{1 \rightarrow 1}$: Portion of total linkage λ_1 caused by $\phi_{1 \rightarrow 1}$ linking only the N_1 turns of L_1
- ▶ $\lambda_{2 \rightarrow 1}$: Portion of total linkage λ_1 caused by $\phi_{2 \rightarrow 1}$ linking the N_1 turns of L_1
- ▶ $\lambda_{2 \rightarrow 2}$: Portion of total linkage λ_2 caused by $\phi_{2 \rightarrow 2}$ linking only the N_2 turns of L_2
- ▶ $\lambda_{1 \rightarrow 2}$: Portion of total linkage λ_2 caused by $\phi_{1 \rightarrow 2}$ linking the N_2 turns of L_2

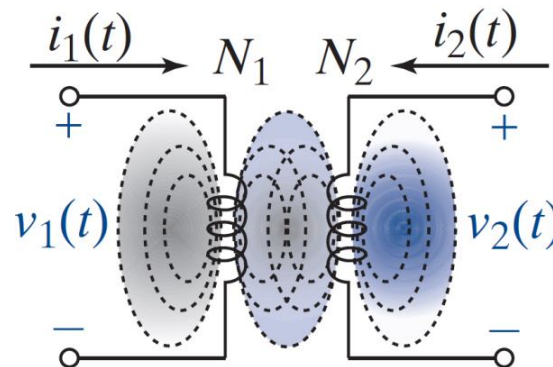

Magnetically Coupled (Neighboring) Coils (cont'd)

- By Faraday's Law, the voltage across each coil is as follows

Coil With Inductance L_1

$$v_1 = v_{1 \rightarrow 1} + v_{2 \rightarrow 1} \text{ (total voltage)}$$

$$v_{1 \rightarrow 1} = N_1 \phi'_{1 \rightarrow 1} = [\mathcal{P}_{1 \rightarrow 1} N_1^2] i'_1$$

$$v_{2 \rightarrow 1} = N_1 \phi'_{2 \rightarrow 1} = [N_1 \mathcal{P}_{2 \rightarrow 1} N_2] i'_2$$


Coil With Inductance L_2

$$v_2 = v_{2 \rightarrow 2} + v_{1 \rightarrow 2} \text{ (total voltage)}$$

$$v_{2 \rightarrow 2} = N_2 \phi'_{2 \rightarrow 2} = [\mathcal{P}_{2 \rightarrow 2} N_2^2] i'_2$$

$$v_{1 \rightarrow 2} = N_2 \phi'_{1 \rightarrow 2} = [N_2 \mathcal{P}_{1 \rightarrow 2} N_1] i'_1$$

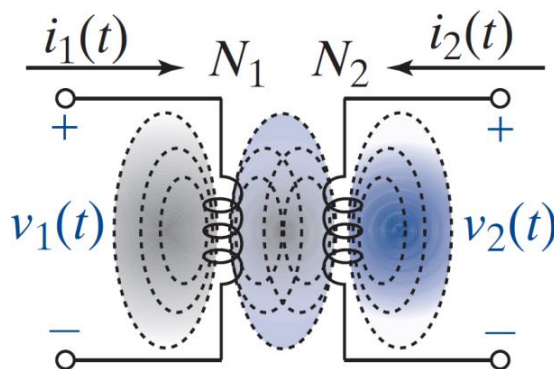- $v_{1 \rightarrow 1}$: Self-induced voltage across L_1 by time-varying current i_1 in L_1
- $v_{2 \rightarrow 1}$: Voltage induced across L_1 by time-varying i_2 in L_2
- $v_{2 \rightarrow 2}$: Self-induced voltage across L_2 by time-varying current i_2 in L_2
- $v_{1 \rightarrow 2}$: Voltage induced across L_2 by time-varying current i_1 in L_1



Magnetically Coupled (Neighboring) Coils (cont'd)

- ▶ A total of four inductance parameters exist

Coil With Inductance L_1

$$v_1 = v_{1 \rightarrow 1} + v_{2 \rightarrow 1} \text{ (total voltage)}$$

$$v_{1 \rightarrow 1} = [\mathcal{P}_{1 \rightarrow 1} N_1^2] i'_1 = L_1 i'_1$$

$$v_{2 \rightarrow 1} = [\mathcal{P}_{2 \rightarrow 1} N_2 N_1] i'_2 = M_{2 \rightarrow 1} i'_2$$


Coil With Inductance L_2

$$v_2 = v_{2 \rightarrow 2} + v_{1 \rightarrow 2} \text{ (total voltage)}$$

$$v_{2 \rightarrow 2} = [\mathcal{P}_{2 \rightarrow 2} N_2^2] i'_2 = L_2 i'_2$$

$$v_{1 \rightarrow 2} = [\mathcal{P}_{1 \rightarrow 2} N_2 N_1] i'_1 = M_{1 \rightarrow 2} i'_1$$

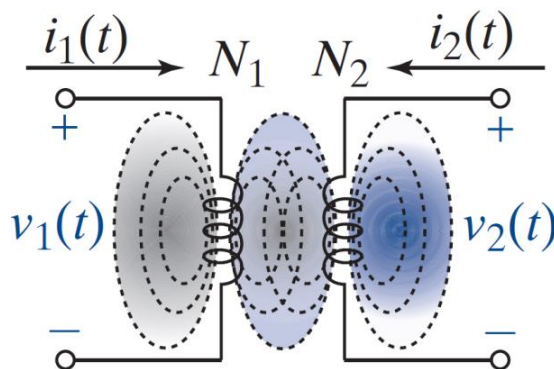- ▶ L_1 : Self-inductance of the first coil measured in Henry's
- ▶ $M_{2 \rightarrow 1}$: Mutual Inductance of coil #1 due to coil #2 measured in Henry's
- ▶ L_2 : Self-inductance of the second coil measured in Henry's
- ▶ $M_{1 \rightarrow 2}$: Mutual Inductance of coil #2 due to coil #1 measured in Henry's



Magnetically Coupled (Neighboring) Coils (cont'd)

- ▶ To summary, the total voltage across each coil is given by

$$v_1(t) = v_{1 \rightarrow 1}(t) + v_{2 \rightarrow 1}(t) = L_1 \frac{di_1(t)}{dt} + M_{2 \rightarrow 1} \frac{di_2(t)}{dt}$$

$$v_2(t) = v_{2 \rightarrow 2}(t) + v_{1 \rightarrow 2}(t) = L_2 \frac{di_2(t)}{dt} + M_{1 \rightarrow 2} \frac{di_1(t)}{dt}$$


- ▶ If the magnetic properties of the space surrounding the flux are linear,

$$\mathcal{P}_{2 \rightarrow 1} = \mathcal{P}_{1 \rightarrow 2} = \mathcal{P}_M \quad M = M_{2 \rightarrow 1} = M_{1 \rightarrow 2} = N_1 N_2 \mathcal{P}_M$$

- ▶ Incorporating the above equalities simplifies the voltage equations as follows

$$v_1(t) = v_{1 \rightarrow 1}(t) + v_{2 \rightarrow 1}(t) = L_1 \frac{di_1(t)}{dt} + M \frac{di_2(t)}{dt}$$
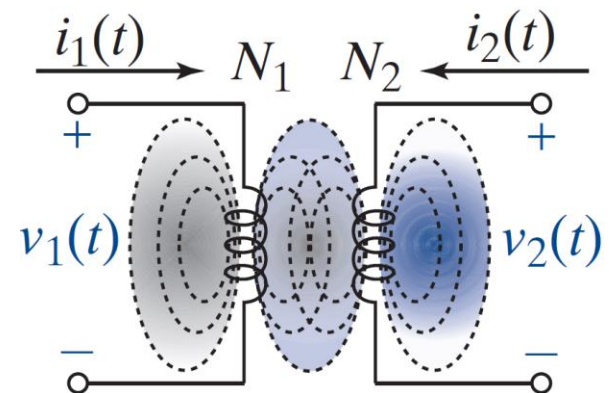
$$v_2(t) = v_{2 \rightarrow 2}(t) + v_{1 \rightarrow 2}(t) = L_2 \frac{di_2(t)}{dt} + M \frac{di_1(t)}{dt}$$



Magnetically Coupled (Neighboring) Coils (cont'd)

- ▶ Although $M, L_1, L_2 \geq 0$ H, voltages $Mi_1'(t)$ and $Mi_2'(t)$ may be positive or negative depending on the rate of change of the respective current
- ▶ To account for the signs, we must adjust the voltage equations as follows


$$v_1(t) = v_{1 \rightarrow 1}(t) \pm v_{2 \rightarrow 1}(t) = L_1 \frac{di_1(t)}{dt} \pm M \frac{di_2(t)}{dt}$$
$$v_2(t) = v_{2 \rightarrow 2}(t) \pm v_{1 \rightarrow 2}(t) = L_2 \frac{di_2(t)}{dt} \pm M \frac{di_1(t)}{dt}$$

- ▶ How do we find the sign of the self-induced voltages $v_{1 \rightarrow 1}(t)$ and $v_{2 \rightarrow 2}(t)$?

Passive Sign Convention (PSC)



- ▶ How do we find the sign of the mutually-induced voltages $v_{2 \rightarrow 1}(t)$ and $v_{1 \rightarrow 2}(t)$?

Dotted Sign Convention (DSC)

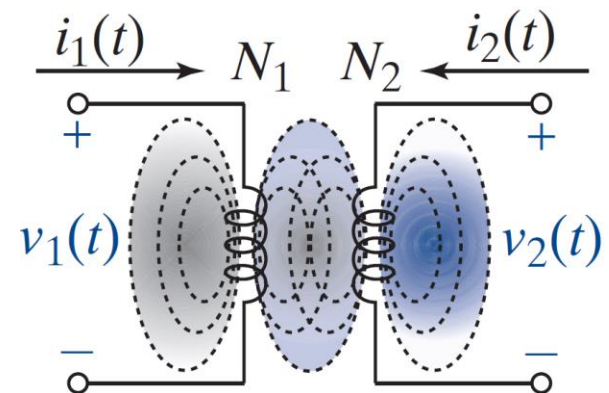

Dotted Sign Convention (DSC)



- ▶ The sign of voltages $Mi_1'(t)$ and $Mi_2'(t)$ depends on two factors:
 - ▶ Spatial orientation of the windings (i.e. how the coils are wound)
 - ▶ The voltage/current references assigned at the terminals of each coil
- ▶ **Additive Coupling:** Current reference directions are such that flux created by each current is oriented in the same direction. For this scenario, the signs of $Mi_1'(t)$ and $Mi_2'(t)$ are both positive.

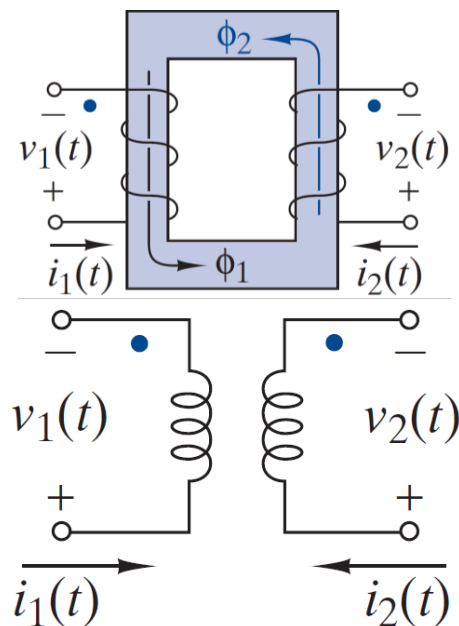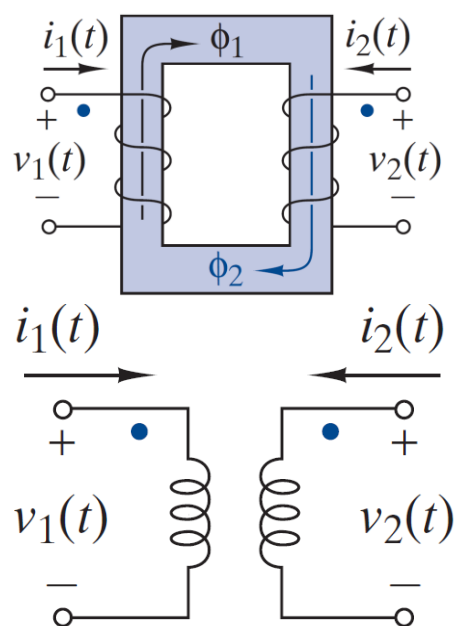

$$\begin{aligned} v_1(t) &= L_1 \frac{di_1(t)}{dt} + M \frac{di_2(t)}{dt} \\ v_2(t) &= L_2 \frac{di_2(t)}{dt} + M \frac{di_1(t)}{dt} \end{aligned}$$

Dotted Sign Convention (DSC) (cont'd)

- ▶ The sign of voltages $Mi_1'(t)$ and $Mi_2'(t)$ depends on two factors:
 - ▶ Spatial orientation of the windings (i.e. how the coils are wound)
 - ▶ The voltage/current references assigned at the terminals of each coil
- ▶ **Subtractive Coupling:** Current reference directions are such that the flux created by each current is oriented in the **opposite direction**. For this scenario, the signs of $Mi_1'(t)$ and $Mi_2'(t)$ are both **negative**.

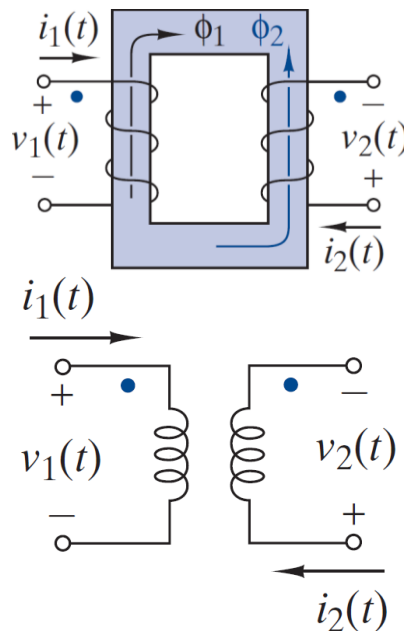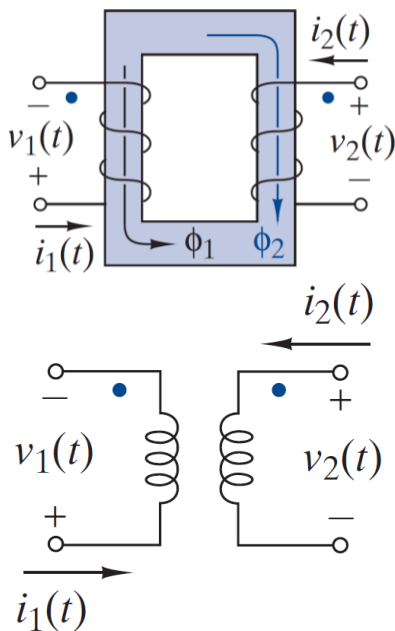


$$\begin{aligned} v_1(t) &= L_1 \frac{di_1(t)}{dt} - M \frac{di_2(t)}{dt} \\ v_2(t) &= L_2 \frac{di_2(t)}{dt} - M \frac{di_1(t)}{dt} \end{aligned}$$


Dotted Sign Convention (DSC) – Summary

- ▶ Current reference directions through the coils and reference polarities of voltages across the coils is chosen according to the passive sign convention.
- ▶ The dotted terminal of each coil indicates physical attributes (i.e. the spatial orientation) of the coil windings and **are fixed**.
- ▶ **The Dot Convention Summarized**

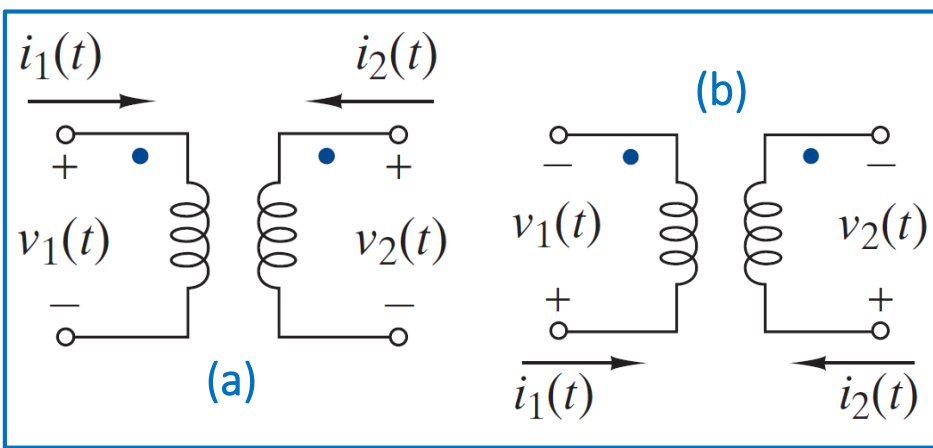Mutual inductance is **additive** when the current reference directions both enter or both leave the dotted nodes, otherwise, the mutual inductance is **subtractive**.



Additive

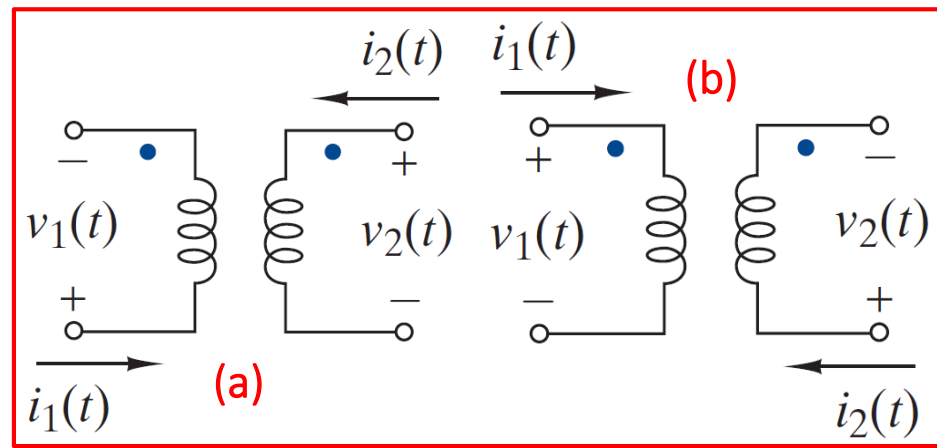

Subtractive

Phasor Representation of Voltages

- ▶ The total voltage across each coil in the time domain was found to be

$$v_1(t) = v_{1 \rightarrow 1}(t) \pm v_{2 \rightarrow 1}(t) = L_1 \frac{di_1(t)}{dt} \pm M \frac{di_2(t)}{dt}$$
$$v_2(t) = v_{2 \rightarrow 2}(t) \pm v_{1 \rightarrow 2}(t) = L_2 \frac{di_2(t)}{dt} \pm M \frac{di_1(t)}{dt}$$

- ▶ If the mutually coupled coils operate in the sinusoidal steady state (SSS) at a radian frequency ω , the total voltage across each coil in the phasor (frequency) domain is as follows

$$\mathbf{V}_1 = \mathbf{V}_{1 \rightarrow 1} \pm \mathbf{V}_{2 \rightarrow 1} = j\omega L_1 \mathbf{I}_1 \pm j\omega M \mathbf{I}_2$$

$$\mathbf{V}_2 = \mathbf{V}_{2 \rightarrow 2} \pm \mathbf{V}_{1 \rightarrow 2} = j\omega L_2 \mathbf{I}_2 \pm j\omega M \mathbf{I}_1$$

Lecture #2(a): Magnetically Coupled Networks *Theory*

Power, Energy, and Coupling Coefficient

Power for Magnetically Coupled Coils

- ▶ The instantaneous power absorbed by each coil is given as

$$p_1(t) = v_1(t)i_1(t) = L_1 i_1(t) \frac{di_1(t)}{dt} \pm M i_1(t) \frac{di_2(t)}{dt}$$

$$p_2(t) = v_2(t)i_2(t) = L_2 i_2(t) \frac{di_2(t)}{dt} \pm M i_2(t) \frac{di_1(t)}{dt}$$

- ▶ The total instantaneous power $p(t)$ absorbed by both coils is

$$p(t) = p_1(t) + p_2(t)$$

$$p(t) = L_1 \left[i_1(t) \frac{di_1(t)}{dt} \right] + L_2 \left[i_2(t) \frac{di_2(t)}{dt} \right] \pm M \left[i_1(t) \frac{di_2(t)}{dt} + i_2(t) \frac{di_1(t)}{dt} \right]$$

- ▶ Each bracketed term above is a perfect derivative. So, $p(t)$ can be written as

$$p(t) = L_1 \left[\frac{1}{2} \frac{di_1^2(t)}{dt} \right] + L_2 \left[\frac{1}{2} \frac{di_2^2(t)}{dt} \right] \pm M \left[\frac{d[i_1(t)i_2(t)]}{dt} \right]$$

$$p(t) = \frac{d}{dt} \left[\frac{1}{2} L_1 i_1^2(t) + \frac{1}{2} L_2 i_2^2(t) \pm M i_1(t) i_2(t) \right]$$

Energy for Magnetically Coupled Coils

- ▶ The total instantaneous power and energy can be related as follows

$$p(t) = \frac{d}{dt} w(t) = \frac{d}{dt} \left[\frac{1}{2} L_1 i_1^2(t) + \frac{1}{2} L_2 i_2^2(t) \pm M i_1(t) i_2(t) \right] \Rightarrow$$

$$\boxed{w(t) = 0.5 L_1 i_1^2(t) + 0.5 L_2 i_2^2(t) \pm M i_1(t) i_2(t)}$$

- ▶ Since each coil is a passive element, $w(t) \geq 0$ for all t . The energy $w(t)$ may become negative only when the mutual term is negative.

$$w(t) = 0.5 L_1 i_1^2(t) + 0.5 L_2 i_2^2(t) - M i_1(t) i_2(t) \geq 0$$

- ▶ Completing the square gives

$$w(t) = 0.5 L_1 i_1^2 - \sqrt{L_1 L_2} i_1 i_2 + 0.5 L_2 i_2^2 + \sqrt{L_1 L_2} i_1 i_2 - M i_1 i_2 \geq 0$$

$$w(t) = 0.5 \left(\sqrt{L_1} i_1 - \sqrt{L_2} i_2 \right)^2 + i_1 i_2 \left(\sqrt{L_1 L_2} - M \right) \geq 0$$

- ▶ From above, when will $w(t) \geq 0$?

Mutual Coupling Coefficient \mathbf{k}

$$w(t) = \frac{1}{2} \left(\sqrt{L_1} i_1(t) - \sqrt{L_2} i_2(t) \right)^2 + i_1(t) i_2(t) \left(\sqrt{L_1 L_2} - M \right) \geq 0$$

- ▶ From the above inequality, the energy is non-negative provided

$$0 \text{ H} \leq M \leq \sqrt{L_1 L_2} \text{ H}$$

- ▶ The above establishes that the mutual inductance magnitude cannot be larger than the geometric mean of the self-inductances of the two coils.
- ▶ **Mutual Coupling Coefficient \mathbf{k}** : Indicates the degree in which $M \rightarrow \sqrt{L_1 L_2}$. **For larger \mathbf{k} , more flux from one coil couples with the other coil, and vice versa.**

$$k = M / \sqrt{L_1 L_2} \rightarrow 0 \leq k \leq 1$$


- ▶ Coils are decoupled when $\mathbf{k} = 0$
- ▶ Coils are tightly coupled when $\mathbf{k} > 0.5$
- ▶ Coils are loosely coupled when $\mathbf{k} \leq 0.5$
- ▶ Coils are perfectly coupled when $\mathbf{k} = 1$ (physically impossible)

Lecture #2(a): Magnetically Coupled Networks *Theory*

Linear Transformer

Linear Transformer

- ▶ **Transformer:** A four-terminal (i.e. 2-port) circuit element that models a magnetic device that leverages the mutual inductance phenomenon of two coils in close spatial proximity.
 - ▶ **Primary Coil/Winding:** Coil connected to the source side having resistance R_1 and self-inductance L_1 Henry's
 - ▶ **Secondary Coil/Winding:** Coil connected to the load side having resistance R_2 and self-inductance L_2 Henry's
- ▶ **Linear Transformer:** A transformer whose coils are wound around a magnetically linear material and whose coupling coefficient $k \neq 1$
 - ▶ e.g. air, plastic, wood, etc.
 - ▶ Usually k is a few tenths, but not always.
 - ▶ Uses include radios, TVs, and other high frequency communication applications.

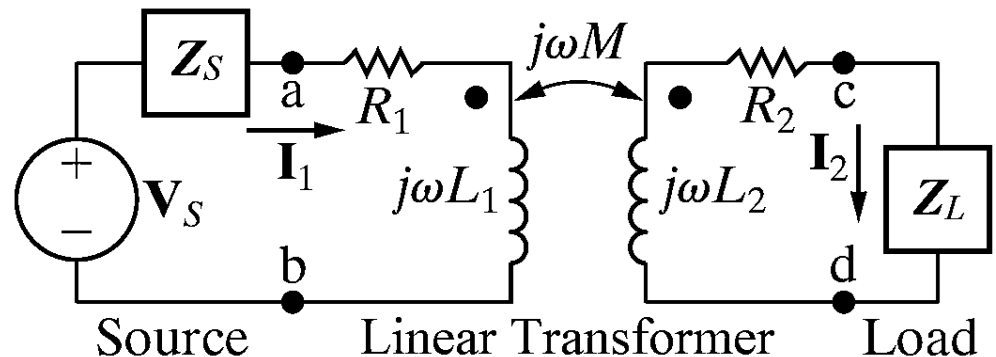

Linear Transformer – SSS Analysis

- ▶ Often, transformers operate in the SSS at a particular frequency ω
- ▶ Mesh analysis of the “Typical Linear Transformer Network” in SSS gives

- ▶ Mesh @ Primary Network

$$\begin{aligned} \mathbf{V}_S &= \mathbf{I}_1(\mathbf{Z}_S + R_1 + j\omega L_1) - j\omega M \mathbf{I}_2 \\ \mathbf{V}_S &= \mathbf{I}_1 \mathbf{Z}_{11} - j\omega M \mathbf{I}_2 \end{aligned}$$

\mathbf{Z}_{11} : Total self-impedance of the mesh network coupled to the primary coil


- ▶ Mesh @ Secondary Network

$$\begin{aligned} \mathbf{I}_2(R_2 + j\omega L_2 + \mathbf{Z}_L) - j\omega M \mathbf{I}_1 &= 0V \\ -j\omega M \mathbf{I}_1 + \mathbf{I}_2 \mathbf{Z}_{22} &= 0V \end{aligned}$$

\mathbf{Z}_{22} : Total self-impedance of the mesh network coupled to the secondary coil

- ▶ Matrix equation governing the electrical behavior of the linear transformer network is given as
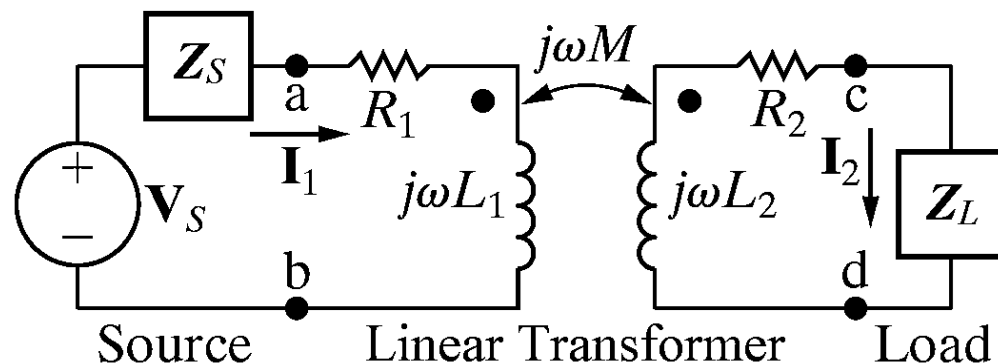
$$\begin{bmatrix} \mathbf{Z}_{11} & -j\omega M \\ -j\omega M & \mathbf{Z}_{22} \end{bmatrix} \begin{bmatrix} \mathbf{I}_1 \\ \mathbf{I}_2 \end{bmatrix} = \begin{bmatrix} \mathbf{V}_s \\ 0 \end{bmatrix}$$



Linear Transformer – Equivalent Primary Network

- ▶ Equivalent network on primary side can be established for analysis purposes

- ▶ Solve secondary mesh equation for I_2

$$I_2 = (j\omega M / Z_{22}) I_1$$

- ▶ Substitute I_2 into primary mesh equation

$$V_S = I_1 Z_{11} - j\omega M (j\omega M / Z_{22}) I_1$$

- ▶ Simplify primary mesh equation

$$V_S = (Z_{11} + [(\omega M)^2 / Z_{22}]) I_1$$

- ▶ Input Impedance

$$Z_{IN} = V_S / I_1 = Z_{11} + [(\omega M)^2 / Z_{22}] = Z_{11} + [(\omega M / |Z_{22}|)^2] Z_{22}^* = Z_{11} + Z_{r2 \rightarrow 1}$$

- ▶ **Reflected Impedance** $Z_{r2 \rightarrow 1}$: Additional impedance “seen” by V_S due to non-zero magnetic coupling among coils (as $M, \omega \rightarrow 0$, $Z_{r2 \rightarrow 1} \rightarrow 0$)

- ▶ Transformer reverses sign of $\text{Im}(Z_{22})$ and scales Z_{22} by a factor $(\omega M / |Z_{22}|)^2$
- ▶ Sign is independent of dot markings on the coils


- ▶ Current through Primary

$$I_1 = V_S / Z_{IN}$$

- ▶ Voltage across Primary

$$V_1 = (Z_{IN} - Z_S) I_1$$

Equivalent primary network

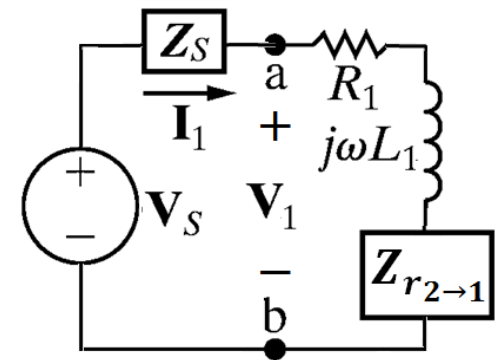

Linear Transformer – Equivalent Secondary Network

- ▶ Equivalent network on secondary side can be established for analysis purposes

- ▶ Solve primary mesh equation for I_1

$$I_1 = (V_S + j\omega M I_2) / Z_{11}$$

- ▶ Substitute I_1 into secondary mesh equation

$$-j\omega M[(V_S + j\omega M I_2) / Z_{11}] + I_2 Z_{22} = 0V$$

- ▶ Simplify secondary mesh equation

$$(j\omega M / Z_{11}) V_S = (Z_{22} + [(\omega M)^2 / Z_{11}]) I_2$$

- ▶ Impedance Seen by Load

$$Z_{TH} = Z_{22} - Z_L + [(\omega M)^2 / Z_{11}] = Z_{22} - Z_L + [(\omega M / |Z_{11}|)^2] Z_{11}^* = Z_{22} - Z_L + Z_{r1 \rightarrow 2}$$

- ▶ **Reflected Impedance** $Z_{r1 \rightarrow 2}$: Additional impedance “seen” by Z_L due to non-zero magnetic coupling among coils (as $M, \omega \rightarrow 0$, $Z_{r1 \rightarrow 2} \rightarrow 0$)

- ▶ Transformer reverses sign of $\text{Im}(Z_{11})$ and scales Z_{11} by a factor $(\omega M / |Z_{11}|)^2$
- ▶ Sign is independent of dot markings on the coils

- ▶ Current through Secondary

$$I_2 = V_{TH} / (Z_{TH} + Z_L)$$


- ▶ Voltage across Secondary

$$V_2 = Z_L I_2$$

- ▶ OC Voltage at Port c-d

$$V_{OC} = (j\omega M / Z_{11}) V_S$$

Equivalent Secondary Network

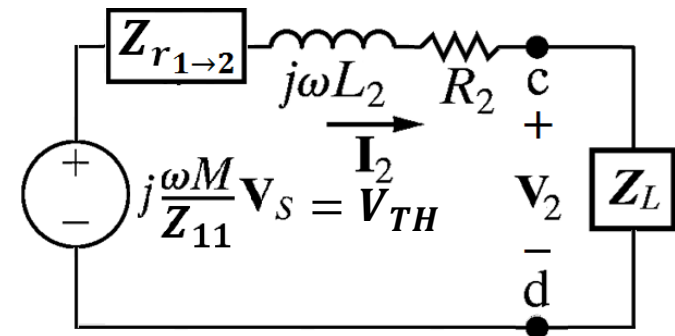


Lecture #2(a): Magnetically Coupled Networks *Theory*

Ideal Transformer

Ideal Transformer

- ▶ **Ideal Transformer:** A transformer that is designed to come as close as possible to the following ideal properties
 - ▶ Coils are wound on a linear magnetic material of high permeability (e.g. iron-based material), so coupling coefficient $\kappa = 1$ (i.e. perfect coupling)
 - ▶ Coils have “large” number of turns ($N_1, N_2 \rightarrow \infty$)
 - ▶ Coils have “large” self inductance ($L_1, L_2, M \rightarrow \infty$)
 - ▶ Each coil exhibits zero (average) power losses (i.e. $R_1 = R_2 = 0$)
- ▶ Ideal transformers are
 - ▶ Typically referred to as iron-core transformers
 - ▶ Used primarily in power-based applications, including power supply design

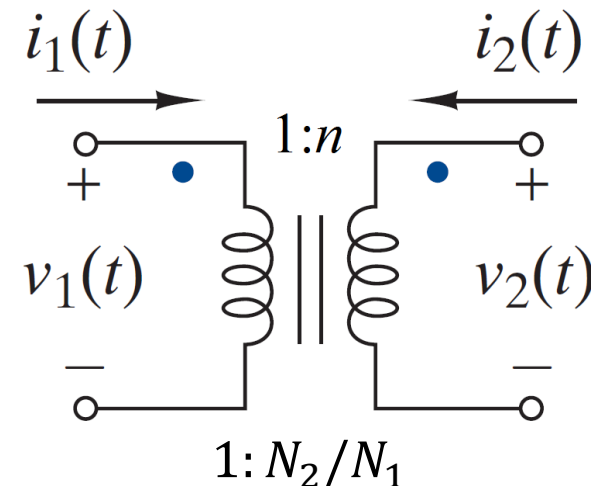

Ideal Transformers – Perfect Coupling

- ▶ Perfect magnetic coupling (i.e. $k = 1$) means all flux from coil #1 links coil #2.
- ▶ Recall, the total flux in each winding is

Flux for Coil #1

$$\phi_1 = \phi_{1 \rightarrow 1} + \phi_{2 \rightarrow 1} = \mathcal{P}_1 N_1 i_1 \text{ (total flux)}$$

$$\phi_{1 \rightarrow 1} = \mathcal{P}_{1 \rightarrow 1} N_1 i_1 \text{ (self term)}$$

$$\phi_{2 \rightarrow 1} = \mathcal{P}_{2 \rightarrow 1} N_2 i_2 \text{ (coupling term)}$$

Flux for Coil #2

$$\phi_2 = \phi_{2 \rightarrow 2} + \phi_{1 \rightarrow 2} = \mathcal{P}_2 N_2 i_2 \text{ (total flux)}$$

$$\phi_{2 \rightarrow 2} = \mathcal{P}_{2 \rightarrow 2} N_2 i_2 \text{ (self term)}$$

$$\phi_{1 \rightarrow 2} = \mathcal{P}_{1 \rightarrow 2} N_1 i_1 \text{ (coupling term)}$$

- ▶ When the windings are perfectly coupled

Flux for Coil #1


$$\phi_{2 \rightarrow 1} = \phi_2 = \mathcal{P}_{2 \rightarrow 1} N_2 i_2 = \mathcal{P}_2 N_2 i_2$$

Flux for Coil #2

$$\phi_{1 \rightarrow 2} = \phi_1 = \mathcal{P}_{2 \rightarrow 1} N_1 i_1 = \mathcal{P}_1 N_1 i_1$$

- ▶ The above equalities imply that
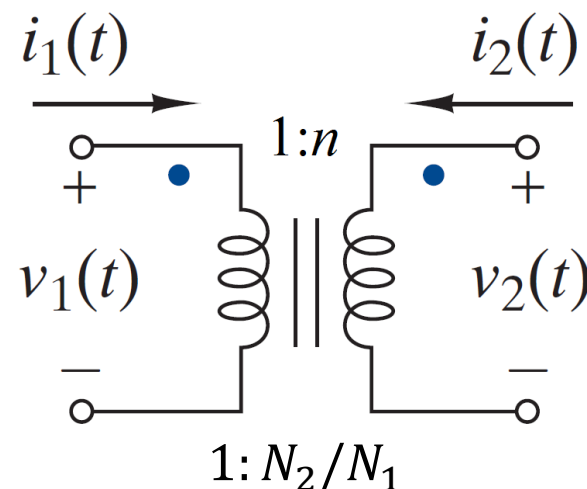
$$\mathcal{P}_{2 \rightarrow 1} = \mathcal{P}_2 = \mathcal{P}_{1 \rightarrow 2} = \mathcal{P}_1 = \mathcal{P}_M$$



Ideal Transformers – Perfect Coupling (cont'd)

- Substitute a single \mathcal{P}_M into the voltage equations gives

Voltage Across Coil #1

$$v_1 = [\mathcal{P}_M N_1^2] i_1' \pm [\mathcal{P}_M N_1 N_2] i_2'$$

- Factor an N_1 out of v_1 and an $\pm N_2$ out of v_2 yields

Voltage Across Coil #1

$$v_1 = N_1 ([\mathcal{P}_M N_1] i_1' \pm [\mathcal{P}_M N_2] i_2')$$

- Divide v_2 by v_1 to yield

$$\frac{v_2}{v_1} = \frac{\pm N_2 (\pm [\mathcal{P}_M N_2] i_2' + [\mathcal{P}_M N_1] i_1')}{N_1 ([\mathcal{P}_M N_1] i_1' \pm [\mathcal{P}_M N_2] i_2')}$$

- Therefore, perfect magnetic coupling ($k = 1$) implies


$$\boxed{\frac{v_2(t)}{v_1(t)} = \pm \frac{N_2}{N_1}} \rightarrow \boxed{\frac{v_1}{v_2} = \pm \frac{N_1}{N_2}}$$

Voltage Across Coil #2

$$v_2 = [\mathcal{P}_M N_2^2] i_2' \pm [\mathcal{P}_M N_1 N_2] i_1'$$

Voltage Across Coil #2
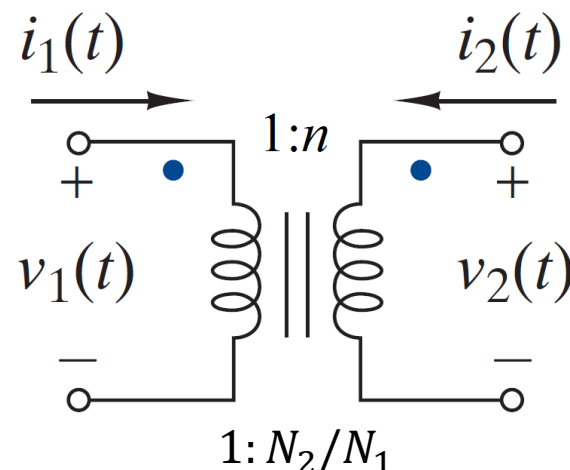
$$v_2 = \pm N_2 (\pm [\mathcal{P}_M N_2] i_2' + [\mathcal{P}_M N_1] i_1')$$



Ideal Transformers – Zero Power Losses

- ▶ Ideal transformers consume zero instantaneous power. According to PSC, instantaneous power of both coils must be zero.

$$p(t) = p_1(t) + p_2(t) = v_1(t)i_1(t) + v_2(t)i_2(t) = 0W$$


- ▶ Above implies coils neither consume nor store energy.
- ▶ Rearranging above yields

$$-v_2(t)i_2(t) = v_1(t)i_1(t) \Rightarrow \boxed{\frac{v_2(t)}{v_1(t)} = -\frac{i_1(t)}{i_2(t)}} \rightarrow \boxed{\frac{v_1(t)}{v_2(t)} = -\frac{i_2(t)}{i_1(t)}}$$

- ▶ Combine the zero power loss assumption and the perfect coupling assumption to yield

$$\boxed{\frac{v_2(t)}{v_1(t)} = \pm \frac{N_2}{N_1} = -\frac{i_1(t)}{i_2(t)}}$$
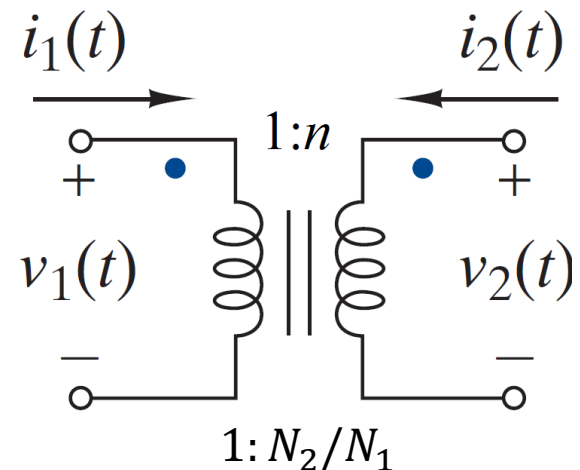
$$\boxed{\frac{v_1(t)}{v_2(t)} = \pm \frac{N_1}{N_2} = -\frac{i_2(t)}{i_1(t)}}$$



Ideal Transformers: i - v Characteristics


▶ Ideal Transformer i - v Constraint (additive)

$$\frac{v_2(t)}{v_1(t)} = \pm \frac{N_2}{N_1} = n$$

$$\frac{i_1(t)}{i_2(t)} = -\frac{N_2}{N_1} = -n$$

▶ Some Transformer Terminology


- ▶ **Turns Ratio** $n = N_2/N_1$: The ratio of the number of turns in the secondary coil to the number of turns in the primary coil
- ▶ **Step-up Transformer**: Ideal transformer with $n > 1$ such that it provides a secondary voltage $|v_2(t)|$ greater than the primary voltage $|v_1(t)|$
- ▶ **Step-down Transformer**: Ideal transformer with $n < 1$ such that it provides a secondary voltage $|v_2(t)|$ less than the primary voltage $|v_1(t)|$
- ▶ **Isolation Transformer**: Ideal transformer with $n = 1$ such that it provides a secondary voltage $|v_2(t)|$ that is the same as the primary voltage $|v_1(t)|$

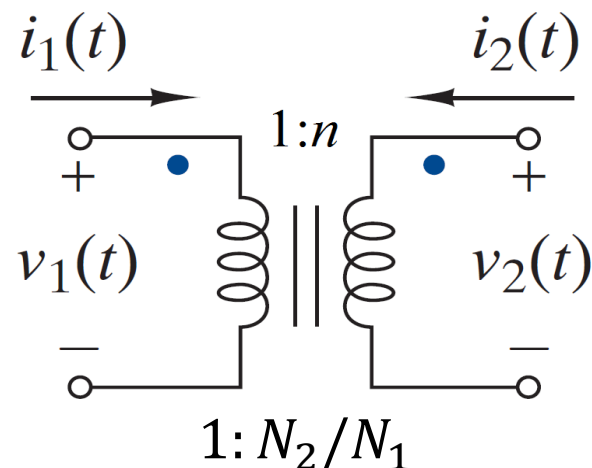

Ideal Transformers – Dot Convention (Viewpoint #1)


- ▶ The preceding characteristics were found assuming additive coupling. Generally, the sign of the constraints are found by using the dot convention.
- ▶ Dot Convention for Ideal Transformer (Assuming Passive Sign Convention)

- ▶ Additive Mutual Coupling

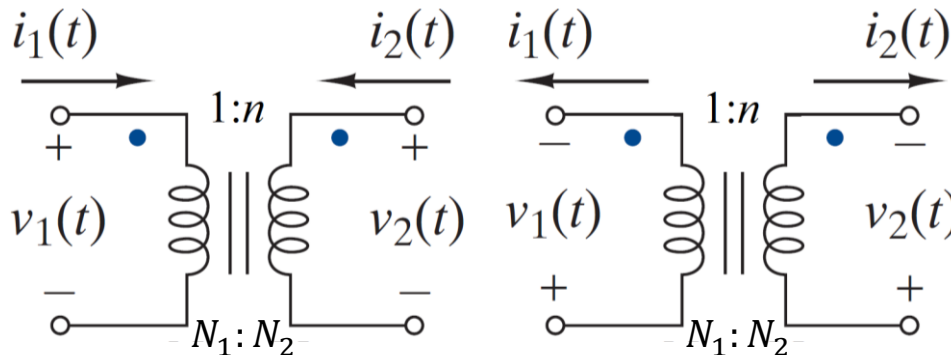

$$\frac{v_2(t)}{v_1(t)} = +\frac{N_2}{N_1} = +n$$
$$\frac{i_1(t)}{i_2(t)} = -\frac{N_2}{N_1} = -n$$

- ▶ Subtractive Mutual Coupling

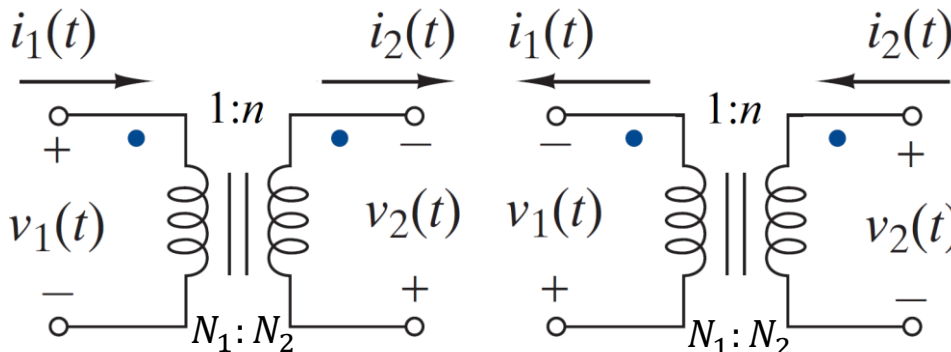


$$\frac{v_2(t)}{v_1(t)} = -\frac{N_2}{N_1} = -n$$
$$\frac{i_1(t)}{i_2(t)} = +\frac{N_2}{N_1} = +n$$

Ideal Transformers – Dot Convention (Viewpoint #2)

▶ Dotted Sign Convention for Ideal Transformer (Independent of PSC)


▶ Voltage References

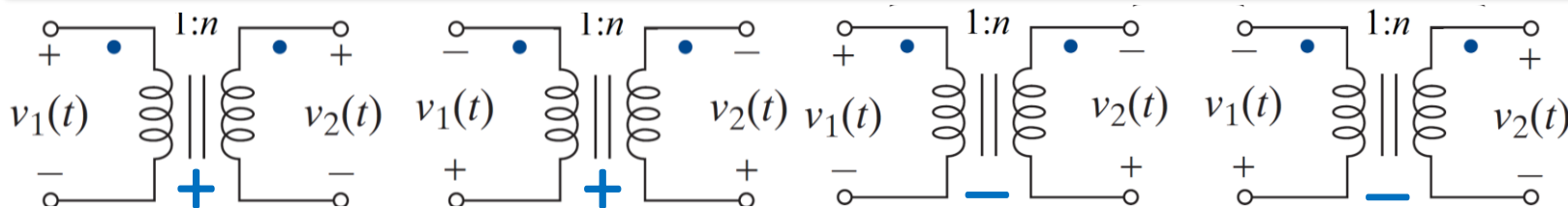Use $+n = +N_2/N_1$ if the ideal transformer voltages are referenced as both positive or both negative at the dotted terminals, otherwise, use $-n = -N_2/N_1$



▶ Current References

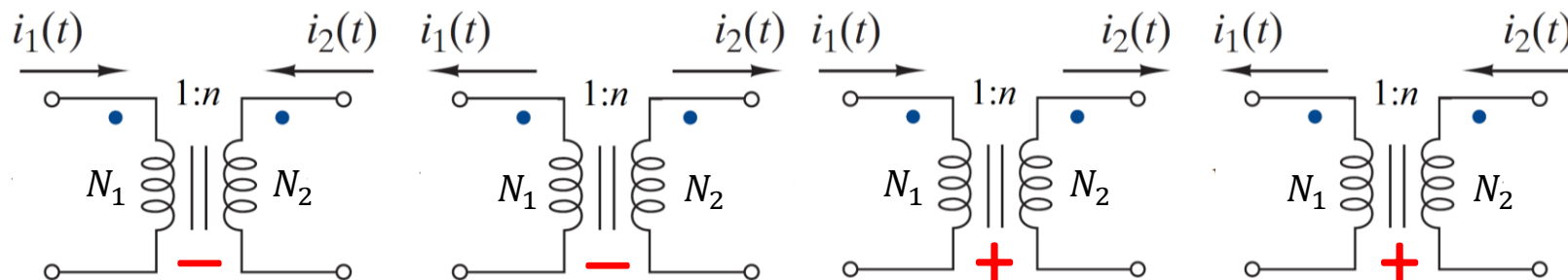Use $-n = -N_2/N_1$ if the ideal transformer currents are referenced as both entering or both leaving the dotted terminals, otherwise, use $+n = N_2/N_1$



Ideal Transformer – SSS Analysis

- ▶ KCL analysis of “Typical Ideal Transformer Network” in the SSS

- ▶ KCL @ Node (a) (Primary)

$$-I_{s1} + (V_1 - V_{s1})/Z_1 + I_1 = 0A$$

- KCL @ Node (c) (Secondary)

$$-I_{s2} + (V_2 - V_{s2})/Z_2 + I_2 = 0A$$

- ▶ Ideal Transformer Voltage Constraint

$$0I_1 + 0I_2 - (N_2/N_1)V_1 + V_2 = 0V$$

- Ideal Transformer Current Constraint


$$I_1 + (N_2/N_1)I_2 + 0V_1 + 0V_2 = 0A$$

- ▶ Matrix equation governing behavior of typical ideal transformer network

$$\begin{bmatrix} 1 & 0 & Z_1^{-1} & 0 \\ 0 & 1 & 0 & Z_2^{-1} \\ 0 & 0 & -N_2/N_1 & 1 \\ 1 & N_2/N_1 & 0 & 0 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} I_{s1} + V_{s1}/Z_1 \\ I_{s2} + V_{s2}/Z_2 \\ 0 \\ 0 \end{bmatrix}$$

$$V_2/V_1 = N_2/N_1$$

$$I_1/I_2 = -N_2/N_1$$

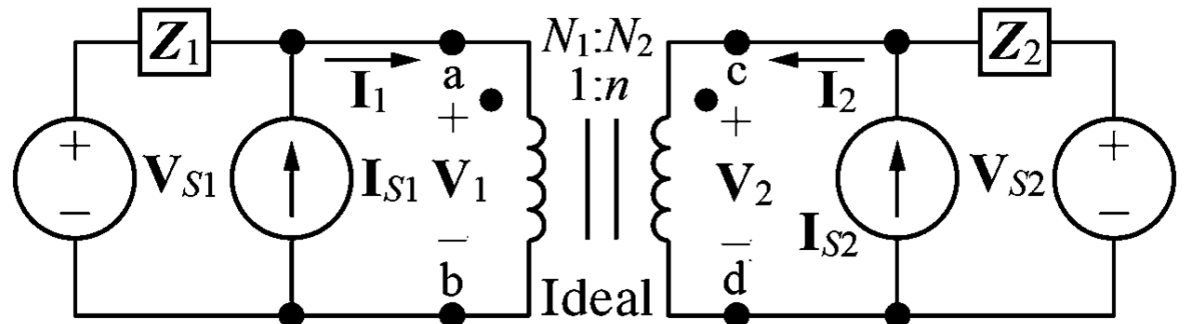

Ideal Transformer – Equivalent Primary Network

- ▶ Equivalent network on primary side can be established for analysis purposes

- ▶ Sub. for I_2 and V_2 into secondary EQ.

$$-I_{s2} + [(N_2/N_1)V_1 - V_{s2}]/Z_2 - (N_1/N_2)I_1 = 0A$$

- ▶ Solve above for I_1

$$-(N_2/N_1)I_{s2} + (N_2/N_1)[(N_2/N_1)V_1 - V_{s2}]/Z_2 = I_1$$

- ▶ Substitute I_1 expression into primary equation

$$-I_{s1} + (V_1 - V_{s1})/Z_1 - (N_2/N_1)I_{s2} + (N_2/N_1)[(N_2/N_1)V_1 - V_{s2}]/Z_2 = 0A$$

- ▶ Simplify above equation

$$-I_{s1} + (V_1 - V_{s1})/Z_1 - (N_2/N_1)I_{s2} + [V_1 - (N_1/N_2)V_{s2}]/[(N_1/N_2)^2 Z_2] = 0A$$


$$-I_{s1} + (V_1 - V_{s1})/Z_1 - I_{r2 \rightarrow 1} + (V_1 - V_{r2 \rightarrow 1})/Z_{r2 \rightarrow 1} = 0A$$

- ▶ **Reflected Elements:** Elements “appearing” on opposite side of transformer due to ideal transformer operation

- ▶ **Impedance** $Z_{r2 \rightarrow 1} = (N_1/N_2)^2 Z_2$: Secondary impedance seen by primary

- ▶ **Current Source** $I_{r2 \rightarrow 1} = (N_2/N_1)I_{s2}$: Secondary current source seen by primary

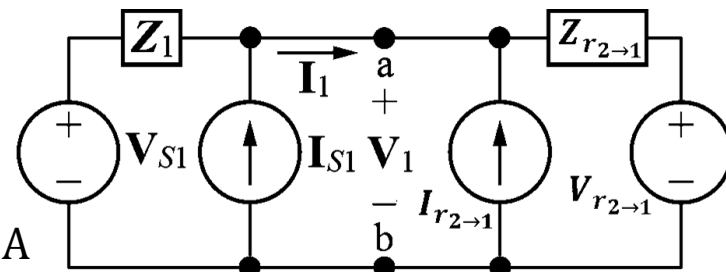
- ▶ **Voltage Source** $V_{r2 \rightarrow 1} = (N_1/N_2)V_{s2}$: Secondary voltage source seen by primary



Equivalent Primary Network

Ideal Transformer – Equivalent Secondary Network

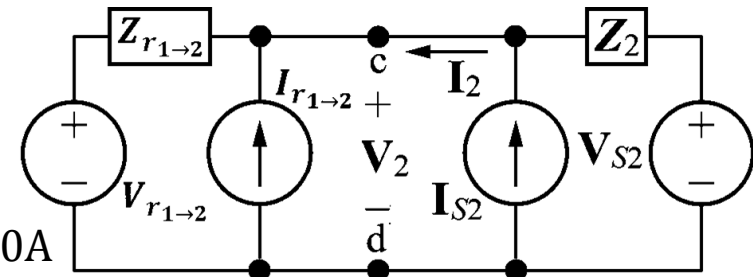- ▶ Equivalent network on secondary side can be established for analysis purposes



Equivalent Secondary Network

- ▶ Sub. for I_1 and V_1 into primary EQ.

$$-I_{s1} + [(N_1/N_2)V_2 - V_{s1}]/Z_1 - (N_2/N_1)I_2 = 0A$$

- ▶ Solve above for I_2

$$-(N_1/N_2)I_{s1} + (N_1/N_2)[(N_1/N_2)V_2 - V_{s1}]/Z_1 = I_2$$

- ▶ Substitute I_2 expression into secondary equation

$$-I_{s2} + (V_2 - V_{s2})/Z_2 - (N_1/N_2)I_{s1} + (N_1/N_2)[(N_1/N_2)V_2 - V_{s1}]/Z_1$$

- ▶ Simplify above equation

$$-I_{s2} + (V_2 - V_{s2})/Z_2 - (N_1/N_2)I_{s1} + [V_2 - (N_2/N_1)V_{s1}]/[(N_2/N_1)^2 Z_1] = 0A$$

$$-I_{s2} + (V_2 - V_{s2})/Z_1 - I_{r1→2} + (V_2 - V_{r1→2})/Z_{r1→2} = 0A$$

- ▶ **Reflected Elements:** Elements “appearing” on opposite side of transformer due to ideal transformer operation

- ▶ **Impedance** $Z_{r1→2} = (N_2/N_1)^2 Z_1$: Primary impedance seen by secondary

- ▶ **Current Source** $I_{r1→2} = (N_1/N_2)I_{s1}$: Primary current source seen by secondary

- ▶ **Voltage Source** $V_{r1→2} = (N_2/N_1)V_{s1}$: Primary voltage source seen by secondary

Ideal Transformer – SSS Analysis

- ▶ KCL analysis of “Typical Ideal Transformer Network” in the SSS

- ▶ KCL @ Node (a) (Primary)

$$-I_{s1} + (V_1 - V_{s1})/Z_1 + I_1 = 0A$$

- KCL @ Node (c) (Secondary)

$$-I_{s2} + (V_2 - V_{s2})/Z_2 + I_2 = 0A$$

- ▶ Ideal Transformer Voltage Constraint

$$0I_1 + 0I_2 + (N_2/N_1)V_1 + V_2 = 0V$$

- Ideal Transformer Current Constraint


$$I_1 - (N_2/N_1)I_2 + 0V_1 + 0V_2 = 0A$$

- ▶ Matrix equation governing behavior of typical ideal transformer network

$$\begin{bmatrix} 1 & 0 & Z_1^{-1} & 0 \\ 0 & 1 & 0 & Z_2^{-1} \\ 0 & 0 & N_2/N_1 & 1 \\ 1 & -N_2/N_1 & 0 & 0 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} I_{s1} + V_{s1}/Z_1 \\ I_{s2} + V_{s2}/Z_2 \\ 0 \\ 0 \end{bmatrix}$$

$$V_2/V_1 = -N_2/N_1$$

$$I_1/I_2 = N_2/N_1$$

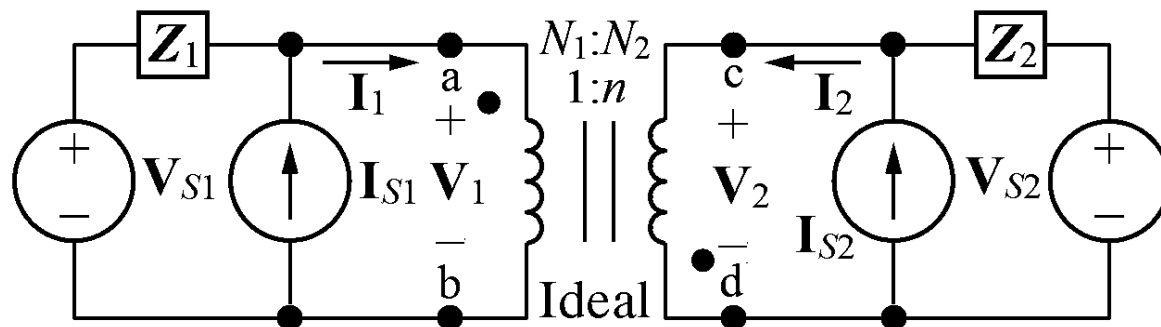

Ideal Transformer – Equivalent Primary Network

- ▶ Equivalent network on primary side can be established for analysis purposes

- ▶ Sub. for I_2 and V_2 into secondary EQ.

$$-I_{s2} + [-(N_2/N_1)V_1 - V_{s2}]/Z_2 + (N_1/N_2)I_1 = 0A$$

- ▶ Solve above for I_1

$$(N_2/N_1)I_{s2} + (N_2/N_1)[(N_2/N_1)V_1 + V_{s2}]/Z_2 = I_1$$

- ▶ Substitute I_1 expression into primary equation

$$-I_{s1} + (V_1 - V_{s1})/Z_1 + (N_2/N_1)I_{s2} + (N_2/N_1)[(N_2/N_1)V_1 + V_{s2}]/Z_2 = 0A$$


- ▶ Simplify above equation

$$-I_{s1} + (V_1 - V_{s1})/Z_1 + (N_2/N_1)I_{s2} + [V_1 + (N_1/N_2)V_{s2}]/[(N_1/N_2)^2 Z_2] = 0A$$

$$-I_{s1} + (V_1 - V_{s1})/Z_1 \boxed{+} I_{r_{2 \rightarrow 1}} + (V_1 \boxed{+} V_{r_{2 \rightarrow 1}})/Z_{r_{2 \rightarrow 1}} = 0A$$

- ▶ **Reflected Elements:** Elements “appearing” on opposite side of transformer due to ideal transformer operation

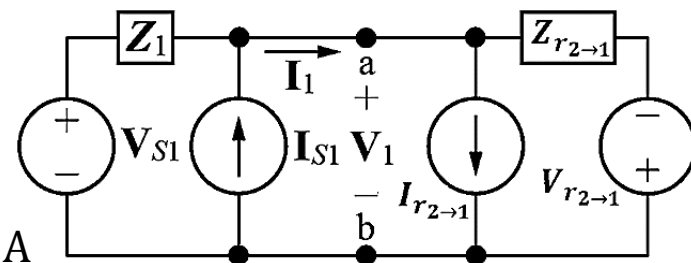
- ▶ **Impedance** $Z_{r_{2 \rightarrow 1}} = (N_1/N_2)^2 Z_2$: Secondary impedance seen on primary
- ▶ **Current Source** $I_{r_{2 \rightarrow 1}} = -(N_2/N_1)I_{s2}$: Secondary current source seen on primary
- ▶ **Voltage Source** $V_{r_{2 \rightarrow 1}} = -(N_1/N_2)V_{s2}$: Secondary voltage source seen on primary



Equivalent Primary Network

Ideal Transformer – Equivalent Secondary Network

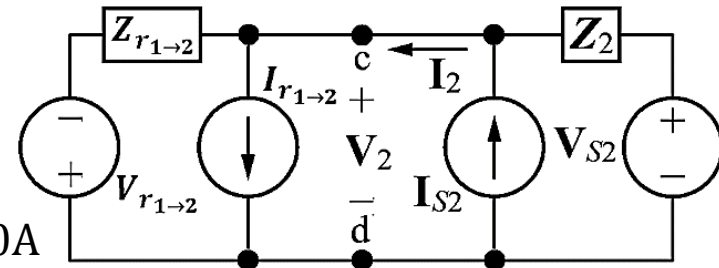- ▶ Equivalent network on secondary side can be established for analysis purposes



Equivalent Secondary Network

- ▶ Sub. for I_1 and V_1 into primary EQ.

$$-I_{s1} + [-(N_1/N_2)V_2 - V_{s1}]/Z_1 + (N_2/N_1)I_2 = 0A$$

- ▶ Solve above for I_2

$$(N_1/N_2)I_{s1} - (N_1/N_2)[-(N_1/N_2)V_2 - V_{s1}]/Z_1 = I_2$$

- ▶ Substitute I_2 expression into secondary equation

$$-I_{s2} + (V_2 - V_{s2})/Z_2 + (N_1/N_2)I_{s1} + (N_1/N_2)[(N_1/N_2)V_2 + V_{s1}]/Z_1$$

- ▶ Simplify above equation

$$-I_{s2} + (V_2 - V_{s2})/Z_2 + (N_1/N_2)I_{s1} + [V_2 + (N_2/N_1)V_{s1}]/[(N_2/N_1)^2 Z_1] = 0A$$

$$-I_{s2} + (V_2 - V_{s2})/Z_1 \boxed{+} I_{r1→2} + (V_2 \boxed{+} V_{r1→2})/Z_{r1→2} = 0A$$

- ▶ **Reflected Elements:** Elements “appearing” on opposite side of transformer due to ideal transformer operation


- ▶ **Impedance** $Z_{r1→2} = (N_2/N_1)^2 Z_1$: Primary impedance seen by secondary

- ▶ **Current Source** $I_{r1→2} = -(N_1/N_2)I_{s1}$: Primary current source by secondary

- ▶ **Voltage Source** $V_{r1→2} = -(N_2/N_1)V_{s1}$: Primary voltage source seen by secondary

Reflecting Elements – Summary (1/2)

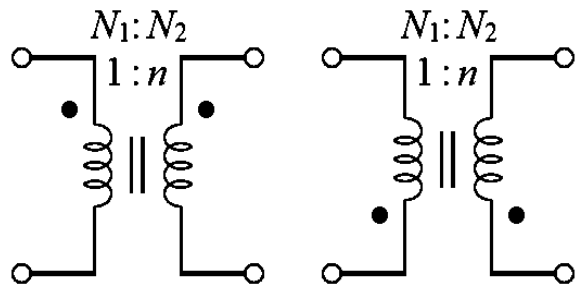► Rules for Reflecting Elements to Primary Side



Rule for Impedances


$$\mathbf{Z}_{r2 \rightarrow 1} = \mathbf{Z}_2 (N_1/N_2)^2 = \mathbf{Z}_2 / n^2$$

Rule for Voltage Sources

$$\mathbf{V}_{r2 \rightarrow 1} = \mathbf{V}_{s2} (N_1/N_2) = \mathbf{V}_{s2} / n$$

Rule for Current Sources
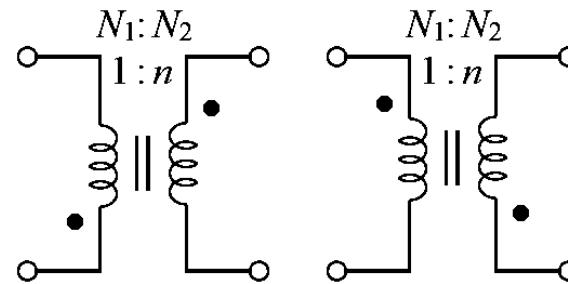
$$\mathbf{I}_{r2 \rightarrow 1} = \mathbf{I}_{s2} (N_2/N_1) = n \mathbf{I}_{s2}$$



Rule for Impedances

$$\mathbf{Z}_{r2 \rightarrow 1} = \mathbf{Z}_2 (N_1/N_2)^2 = \mathbf{Z}_2 / n^2$$

Rule for Voltage Sources

$$\mathbf{V}_{r2 \rightarrow 1} = -\mathbf{V}_{s2} (N_1/N_2) = -\mathbf{V}_{s2} / n$$

Rule for Current Sources


$$\mathbf{I}_{r2 \rightarrow 1} = -\mathbf{I}_{s2} (N_2/N_1) = -n \mathbf{I}_{s2}$$

► Notes About Reflection

- Order of elements must be preserved when reflecting
- Reflection rules also apply to dependent sources
- **Cannot be applied** if primary and secondary is **electrically coupled**!

Reflecting Elements – Summary (2/2)

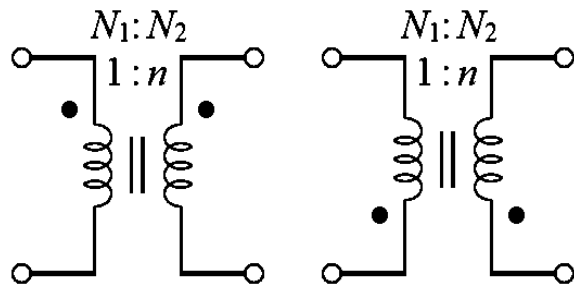► Rules for Reflecting Elements to Secondary Side



Rule for Impedances


$$\mathbf{Z}_{r1 \rightarrow 2} = \mathbf{Z}_1 (N_2/N_1)^2 = n^2 \mathbf{Z}_1$$

Rule for Voltage Sources

$$\mathbf{V}_{r1 \rightarrow 2} = \mathbf{V}_{s1} (N_2/N_1) = n \mathbf{V}_{s1}$$

Rule for Current Sources
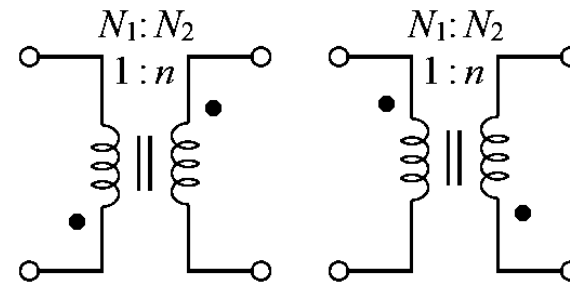
$$\mathbf{I}_{r1 \rightarrow 2} = \mathbf{I}_{s1} (N_1/N_2) = \mathbf{I}_{s1}/n$$



Rule for Impedances

$$\mathbf{Z}_{r1 \rightarrow 2} = \mathbf{Z}_1 (N_2/N_1)^2 = n^2 \mathbf{Z}_1$$

Rule for Voltage Sources

$$\mathbf{V}_{r1 \rightarrow 2} = -\mathbf{V}_{s1} (N_2/N_1) = -n \mathbf{V}_{s1}$$

Rule for Current Sources

$$\mathbf{I}_{r1 \rightarrow 2} = -\mathbf{I}_{s1} (N_1/N_2) = -\mathbf{I}_{s1}/n$$

► Notes About Reflection

- Order of elements must be preserved when reflecting
- Reflection rules also apply to dependent sources
- **Cannot be applied** if primary and secondary is electrically coupled!

Lecture Summary

- ▶ This set of slides presented the following
 - ▶ Mutual Inductance
 - ▶ Defining Mutual Conductance
 - ▶ Dotted Sign Convention
 - ▶ Energy Considerations
 - ▶ Analysis of Magnetically Coupled Networks
 - ▶ The Linear Transformer
 - ▶ SSS Analysis
 - ▶ Reflected Impedances
 - ▶ The Ideal Transformer
 - ▶ Element Constraints
 - ▶ Dot Convention
 - ▶ SSS Analysis
 - ▶ Reflecting Elements