



Lecture #1(b) Poly-Phase Networks

Examples

ECE 20200: Linear Circuit Analysis II
Steve Naumov (Instructor)


Lecture #1(b) Poly-Phase Networks

Examples

Y and Δ Impedance Networks

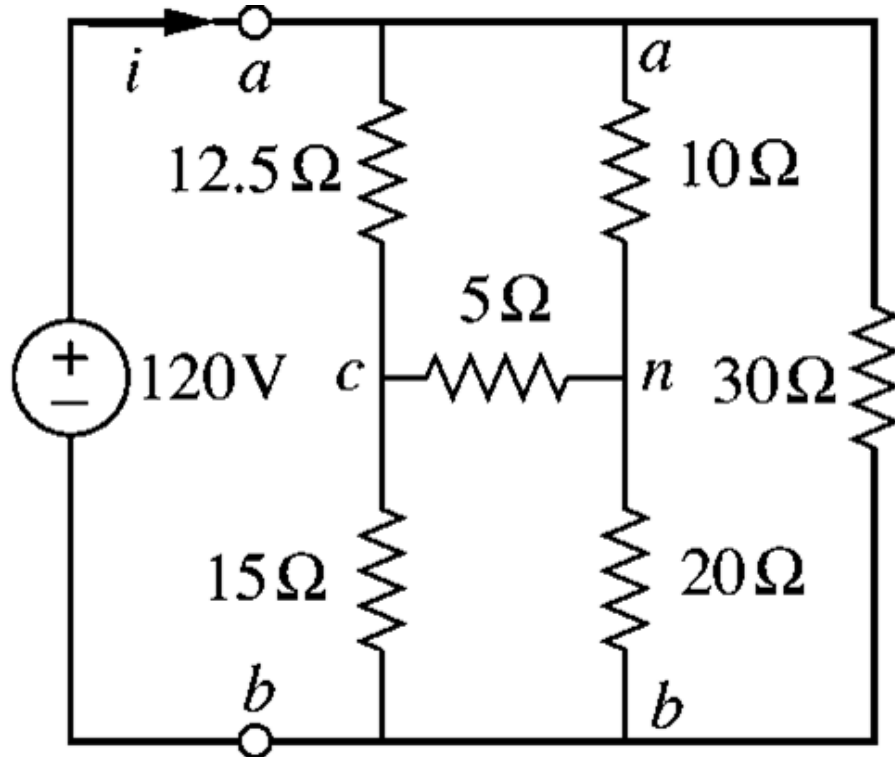Example #1

- ▶ Assume the resistive network operates in the DC steady state.
 - ▶ Determine the equivalent resistance R_{ab} seen by the source
 - ▶ Compute current i using the equivalent resistance R_{ab}



Example #1 (SOLUTION)

- ▶ Determine R_{ab} seen by the source
 - ▶ The 3 red-enclosed resistors are in a Y config.
 $R_{an} = 10\Omega$, $R_{bn} = 20\Omega$, and $R_{cn} = 5\Omega$
 - ▶ Transform the three resistors into a delta config

$$R_{\Delta} = R_{an}R_{bn} + R_{bn}R_{cn} + R_{cn}R_{an}$$

$$R_{\Delta} = (10\Omega)(20\Omega) + (20\Omega)(5\Omega) + (5\Omega)(10\Omega)$$



$$R_{\Delta} = 350\Omega^2$$

$$R_{ab} = R_{\Delta}/R_{cn} = 350/5 \rightarrow R_{ab} = 70\Omega$$

$$R_{bc} = R_{\Delta}/R_{an} = 350/10 \rightarrow R_{bc} = 35\Omega$$

$$R_{ca} = R_{\Delta}/R_{bn} = 350/20 \rightarrow R_{ca} = 17.5\Omega$$

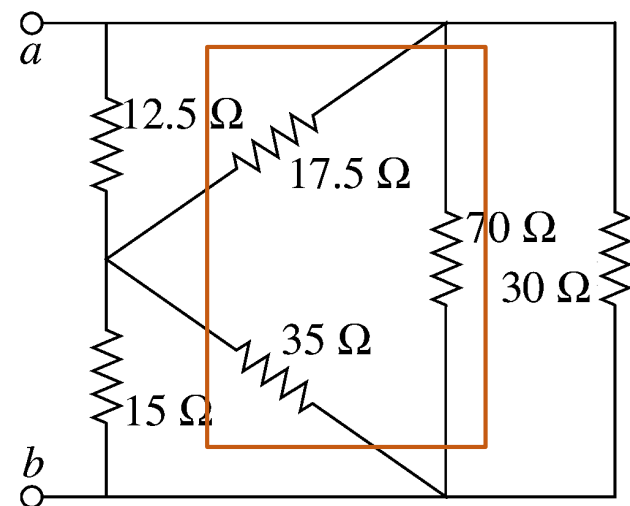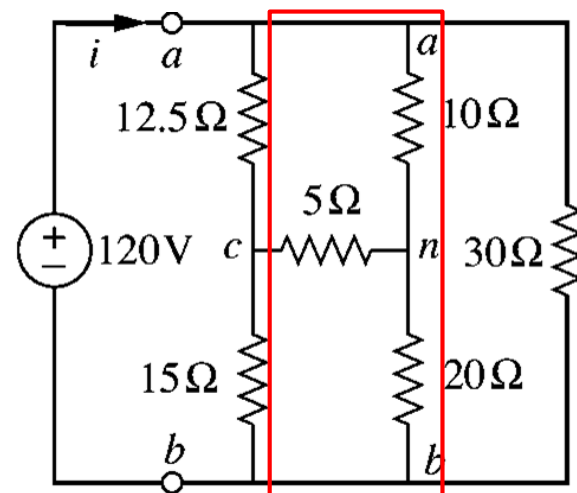- ▶ The new equivalent resistance network is shown here



Example #1 (SOLUTION cont'd)

- ▶ Determine R_{ab} seen by the source
 - ▶ Now, there are three pairs of resistors in parallel with each other

$$R_1 = (12.5\Omega) \parallel (17.5\Omega) \rightarrow \boxed{R_1 = 7.292\Omega}$$

$$R_2 = (15\Omega) \parallel (35\Omega) \rightarrow \boxed{R_2 = 10.5\Omega}$$

$$R_3 = (70\Omega) \parallel (30\Omega) \rightarrow \boxed{R_3 = 21\Omega}$$



- ▶ The reduced equivalent network is shown. Finally, R_{ab} can be computed as

$$R_{ab} = (R_x + R_y) \parallel R_z = (7.292\Omega + 10.5\Omega) \parallel (21\Omega)$$

$$R_{ab} = (17.792\Omega) \parallel (21\Omega) \rightarrow \boxed{R_{ab} = 9.632\Omega}$$


- ▶ Compute current i using the equivalent resistance R_{ab}
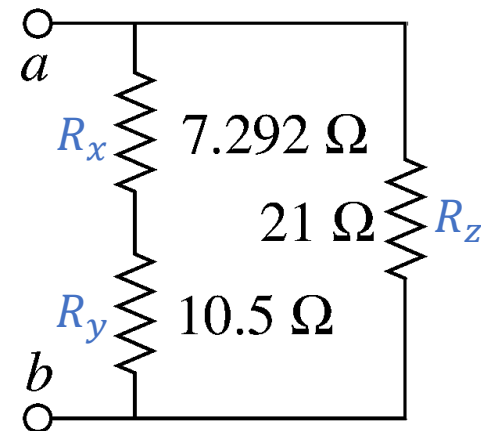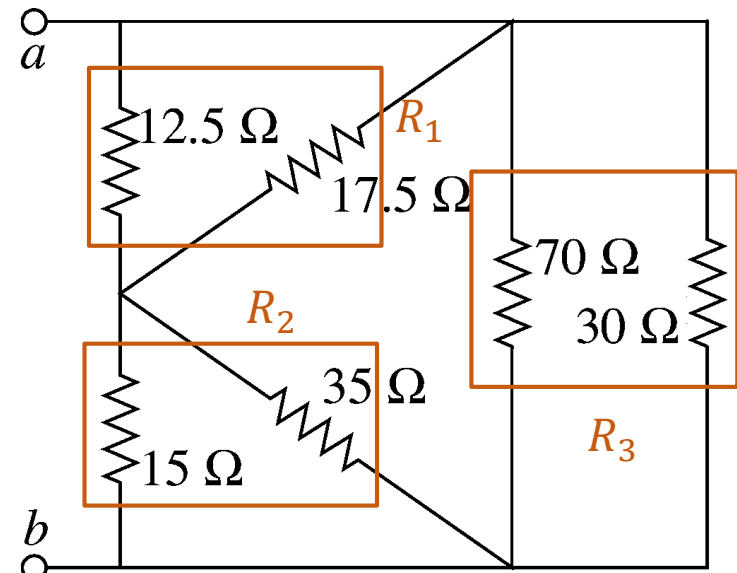
$$i = \frac{V_{src}}{R_{ab}} = \frac{120V}{9.632\Omega} \rightarrow \boxed{i = 12.458A}$$



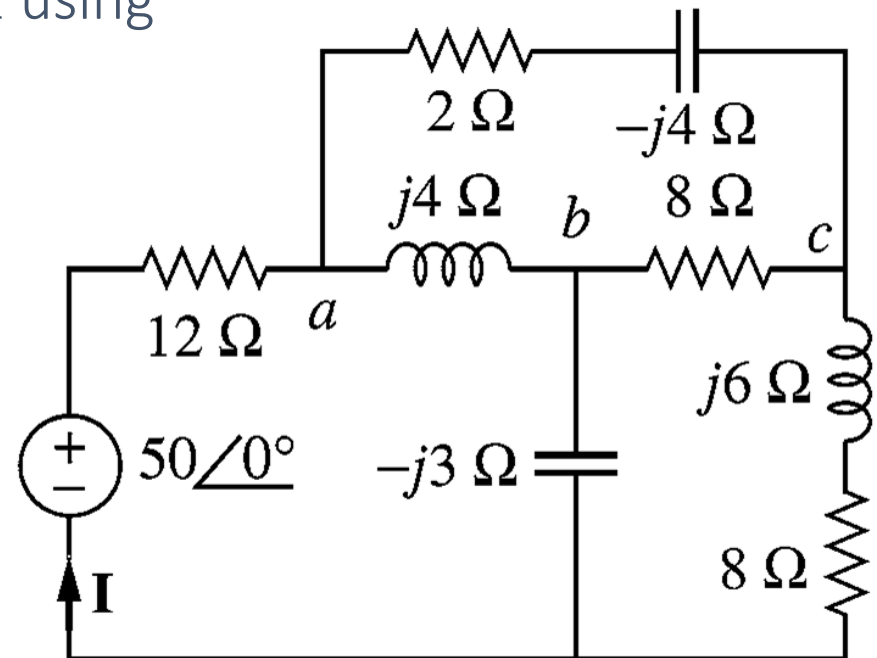Example #2

- ▶ Assume the network is operating in the sinusoidal steady state (SSS). Compute the following
 - ▶ Use Δ -to- Y transformations, Y -to- Δ transformations, or both to compute the equivalent impedance seen by the load
 - ▶ Compute the phasor current \mathbf{I} using the equivalent impedance



Example #2 (SOLUTION)

- ▶ Use Δ -to-Y transformations, Y-to- Δ transformations, or both to compute the equivalent impedance seen by the load

- ▶ Red-enclosed impedances form a Δ config.

$$Z_{ab} = j4\Omega, Z_{bc} = 8\Omega, \text{ and } Z_{ca} = 2 - j4\Omega$$

- ▶ Transform the 3 impedances to a Y-config


$$Z_y = Z_{ab} + Z_{bc} + Z_{ca} \text{ (denominator)}$$

$$Z_y = j4\Omega + 8\Omega + 2\Omega - j4\Omega \rightarrow \boxed{Z_y = 10\Omega}$$

$$Z_{an} = Z_{ab}Z_{ca}/Z_y = [(j4)(2 - j4)]/10 \rightarrow \boxed{Z_{an} = 1.6 + j0.8\Omega}$$

$$Z_{bn} = (Z_{ab}Z_{bc})/Z_y = [(j4)(8)]/10 \rightarrow \boxed{Z_{bn} = j3.2\Omega}$$
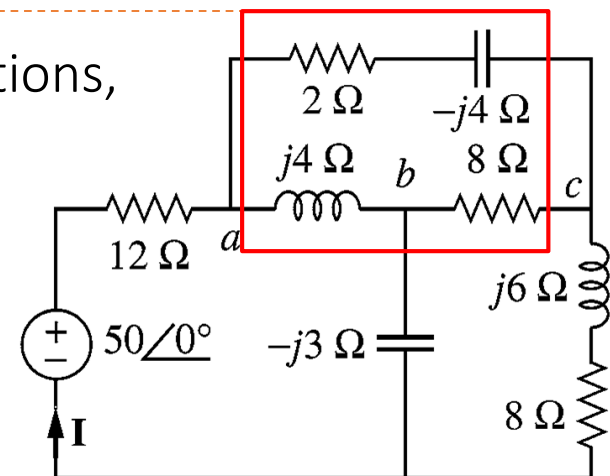
$$Z_{cn} = (Z_{bc}Z_{ca})/Z_y = [(8)(2 - j4)]/10 \rightarrow \boxed{Z_{cn} = 1.6 - j3.2\Omega}$$



Example #2 (SOLUTION cont'd)

- ▶ Use Δ -to-Y transformations, Y-to- Δ transformations, or both to compute the equivalent impedance seen by the load
- ▶ The equivalent schematic after the transformation is shown below
- ▶ Now, Z_{eq} seen by the source can now be computed

$$Z_{eq} = (Z_{cn} + 8\Omega + j6\Omega) || (Z_{bn} - j3\Omega) + (Z_{an} + 12\Omega)$$


$$Z_{eq} = (1.6\Omega - j3.2\Omega + 8\Omega + j6\Omega) || (j3.2\Omega - j3\Omega) + (1.6\Omega + j0.8\Omega + 12\Omega)$$

$$Z_{eq} = 13.6\Omega + j1\Omega = 13.64e^{j4.2^\circ}\Omega$$

- ▶ Compute the phasor current \mathbf{I} using the equivalent impedance

$$\mathbf{I} = \frac{\mathbf{V}_{src}}{Z_{eq}} = \frac{50e^{j0^\circ}\text{V}}{13.64e^{j4.2^\circ}\Omega}$$
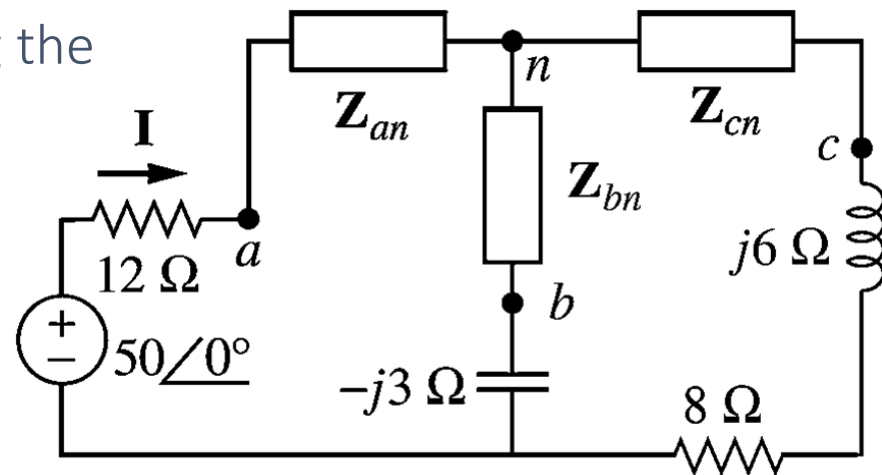
$$\mathbf{I} = 3.66 - j0.269\text{A} = 3.67e^{-j4.2^\circ}\text{A}$$



Lecture #1(b) Poly-Phase Networks

Examples

Balanced 3-Phase Networks

Example #1

- ▶ A balanced 3-phase Y source with a-b-c sequence has an impedance of $Z_s = 0.2 + j0.5 \Omega/\phi$ (Ohm's per phase) and an voltage of $\mathbf{V}_{a'n} = 120e^{j0^\circ} \text{ V (rms)}$. The source drives a balanced 3-phase Y load with an impedance of $Z_Y = 39 + j28 \Omega/\phi$. The line impedance connecting source to the load is $Z_\ell = 0.8 + j1.5 \Omega/\phi$. Use a-phase internal source voltage as the reference.
 - ▶ Draw the a-phase equivalent network of the Y-Y system
 - ▶ Calculate the transmission line currents for each phase
 - ▶ Calculate the phase voltages at the load
 - ▶ Calculate the line-to-line voltages at the load's terminals
 - ▶ Calculate the phase voltages at the source's terminals
 - ▶ Calculate the line-to-line voltages at the source's terminals
 - ▶ Calculate the total complex power, average power, and reactive power absorbed by the load
 - ▶ Calculate the total complex power, average power, and reactive power lost in the three transmission lines
 - ▶ Calculate the total complex power, average power, and reactive power lost in the 3-phase source

Example #1 (SOLUTION)

- ▶ Draw the a-phase equivalent network of the Y-Y system
- ▶ Calculate transmission line currents currents for each phase

- ▶ First compute the a-phase equivalent impedance Z_ϕ

$$Z_\phi = Z_s + Z_\ell + Z_Y$$

$$Z_\phi = (0.2 + 0.8 + 39) + j(0.5 + 1.5 + 28) \rightarrow \boxed{Z_\phi = 40 + j30 \Omega}$$


- ▶ Next compute the a-phase transmission line current

$$\mathbf{I}_{aA} = \mathbf{V}_{a'n} / Z_\phi = [120e^{j0^\circ} \text{V}(\text{rms})] / (40 + j30 \Omega) \rightarrow \boxed{\mathbf{I}_{aA} \approx 2.4e^{-j36.89^\circ} \text{A}(\text{rms})}$$

- ▶ Finally, compute the b- and c-phase line currents (a-b-c) sequence

$$\mathbf{I}_{bB} = (e^{-j120^\circ}) \mathbf{I}_{aA} \rightarrow \boxed{\mathbf{I}_{bB} \approx 2.4e^{-j156.89^\circ} \text{A}(\text{rms})}$$
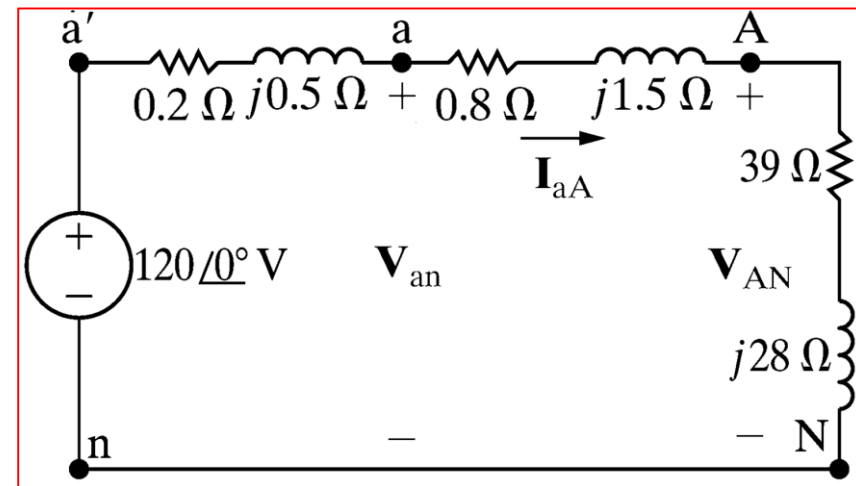
$$\mathbf{I}_{cC} = (e^{+j120^\circ}) \mathbf{I}_{aA} \rightarrow \boxed{\mathbf{I}_{cC} \approx 2.4e^{+j83.11^\circ} \text{A}(\text{rms})}$$



Example #1 (SOLUTION cont'd)

- ▶ Calculate the phase voltages at the load

- ▶ First, compute the A-phase load voltage

$$\mathbf{V}_{AN} = I_{aA} Z_Y \approx [2.4e^{-j36.89^\circ} \text{A}_{(rms)}](39 + j28\Omega)$$

$$\mathbf{V}_{AN} \approx 115.23e^{-j1.19^\circ} \text{V}_{(rms)}$$

- ▶ Now, compute B- and C-phase load voltages

$$\mathbf{V}_{BN} = (e^{-j120^\circ})\mathbf{V}_{AN} \rightarrow \mathbf{V}_{BN} \approx 115.23e^{-j121.19^\circ} \text{V}_{(rms)}$$

$$\mathbf{V}_{CN} = (e^{+j120^\circ})\mathbf{V}_{AN} \rightarrow \mathbf{V}_{CN} \approx 115.23e^{+j118.81^\circ} \text{V}_{(rms)}$$

- ▶ Calculate the line-to-line voltages at the load's terminals (A-B-C sequence)


- ▶ Use factor $(\sqrt{3}e^{j30^\circ})$ to compute the A-to-B line-to-line load voltage

$$\mathbf{V}_{AB} = (\sqrt{3}e^{j30^\circ})\mathbf{V}_{AN} \rightarrow \mathbf{V}_{AB} \approx 199.58e^{j28.81^\circ} \text{V}_{(rms)}$$

- ▶ Next, compute the B-C and C-A load voltages (A-B-C sequence)

$$\mathbf{V}_{BC} = (e^{-j120^\circ})\mathbf{V}_{AB} \rightarrow \mathbf{V}_{BC} \approx 199.58e^{-j91.19^\circ} \text{V}_{(rms)}$$
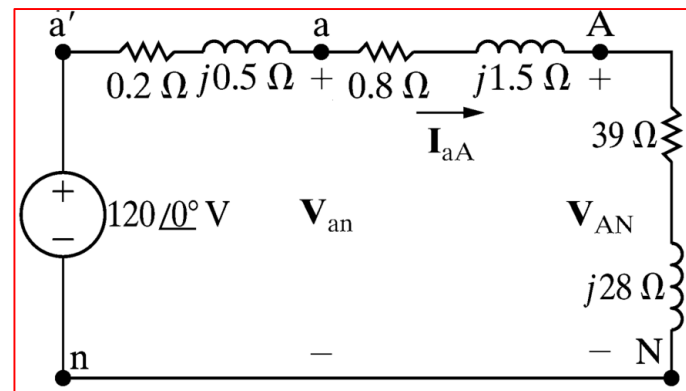
$$\mathbf{V}_{CA} = (e^{+j120^\circ})\mathbf{V}_{AB} \rightarrow \mathbf{V}_{CA} \approx 199.58e^{+j148.81^\circ} \text{V}_{(rms)}$$



Example #1 (SOLUTION cont'd)

- ▶ Calculate phase voltages at source's terminals

- ▶ First, compute the a-phase voltage at the source terminal

$$\mathbf{V}_{an} = \mathbf{V}_{a'n} - \mathbf{I}_{aA}Z_S$$

$$\mathbf{V}_{an} \approx 120e^{j0^\circ}\text{V} - [2.4e^{-j36.89^\circ}\text{A}](0.2 + j0.5\Omega)$$

$$\mathbf{V}_{an} \approx 118.90e^{-j0.32^\circ}\text{V}(rms)$$

- ▶ Now, compute b- and c-phase voltages at source's terminals (a-b-c seq.)

$$\mathbf{V}_{bn} = (e^{-j120^\circ})\mathbf{V}_{an} \rightarrow \mathbf{V}_{bn} \approx 118.90e^{-j120.32^\circ}\text{V}(rms)$$

$$\mathbf{V}_{cn} = (e^{+j120^\circ})\mathbf{V}_{an} \rightarrow \mathbf{V}_{cn} \approx 118.90e^{j119.68^\circ}\text{V}(rms)$$

- ▶ Calculate the line-to-line voltages and at the source's terminals


- ▶ First compute a-b line source terminal voltage (a-b-c sequence)

$$\mathbf{V}_{ab} = (\sqrt{3}e^{j30^\circ})\mathbf{V}_{an} \rightarrow \mathbf{V}_{ab} \approx 205.94e^{j29.68^\circ}\text{V}(rms)$$

- ▶ Next, compute the b-c and c-a load voltages (a-b-c sequence)

$$\mathbf{V}_{bc} = (e^{-j120^\circ})\mathbf{V}_{ab} \rightarrow \mathbf{V}_{bc} \approx 205.94e^{-j90.32^\circ}\text{V}(rms)$$
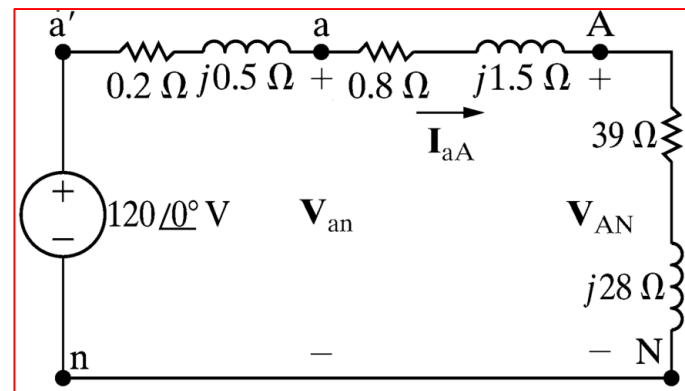
$$\mathbf{V}_{ca} = (e^{+j120^\circ})\mathbf{V}_{ab} \rightarrow \mathbf{V}_{ca} \approx 205.94e^{+j149.68^\circ}\text{V}(rms)$$



Example #1 (SOLUTION cont'd)

- ▶ Calculate the total complex power, average power, and reactive power absorbed by the load

- ▶ First, calculate load's a-phase complex power

$$\mathbf{S}_{AN} = \mathbf{V}_{AN} \mathbf{I}_{aA}^* = |\mathbf{I}_{aA}|^2 Z_Y^* = |\mathbf{V}_{AN}|^2 / Z_Y^*$$

$$\mathbf{S}_{AN} = (115.23 e^{-j1.19^\circ} \text{V}_{\text{rms}})(2.4 e^{-j36.89^\circ} \text{A}_{\text{rms}})^*$$

$$\mathbf{S}_{AN} = 224.58 + j161.38 \text{ VA} = 276.55 e^{j35.7^\circ} \text{ VA}$$

- ▶ Next, compute the total complex power absorbed by the load


$$\mathbf{S}_{tot,load} = 3\mathbf{S}_{AN} = 3(224.58 + j161.38 \text{ VA}) = 3(276.55 e^{j35.7^\circ} \text{ VA})$$

$$\mathbf{S}_{tot,load} = 673.75 + j484.14 \text{ VA} = 829.66 e^{j35.7^\circ} \text{ VA}$$

- ▶ Finally, compute the total average and reactive power of the load

$$P_{tot,load} = \text{Re}(\mathbf{S}_{tot,load}) \rightarrow P_{tot,load} = 673.75 \text{ W}$$
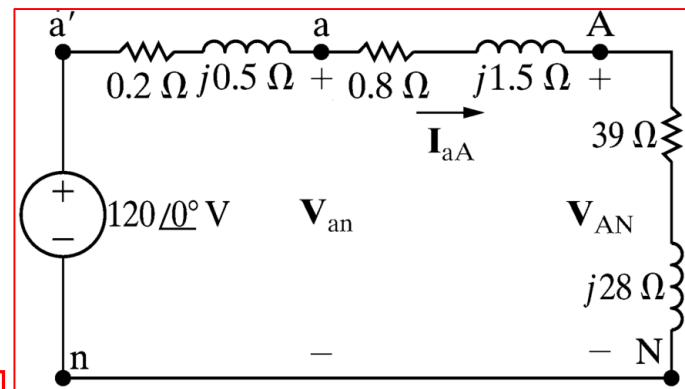
$$Q_{tot,load} = \text{Im}(\mathbf{S}_{tot,load}) \rightarrow Q_{tot,load} = 484.14 \text{ VARs}$$



Example #1 (SOLUTION cont'd)

- ▶ Calculate the total complex power, average power, and reactive power lost in the three transmission lines

- ▶ First, calculate a-phase line's complex power

$$\mathbf{S}_{aA} = (\mathbf{V}_{an} - \mathbf{V}_{AN}) \mathbf{I}_{aA}^* = |\mathbf{I}_{aA}|^2 Z_\ell = \frac{|\mathbf{V}_{an} - \mathbf{V}_{AN}|^2}{Z_\ell^*}$$

$$\mathbf{S}_{aA} = |2.4e^{-j36.89^\circ} \text{A}_{\text{rms}}|^2 (0.8 + j1.5 \Omega)$$

$$\mathbf{S}_{aA} = 4.61 + j8.64 \text{ VA} = 9.79e^{j61.93^\circ} \text{ VA}$$

- ▶ Next, compute the total complex power lost in the three lines


$$\mathbf{S}_{\text{tot,line}} = 3\mathbf{S}_{aA} = 3(4.61 + j8.64 \text{ VA}) = 3(9.79e^{j61.93^\circ} \text{ VA})$$

$$\mathbf{S}_{\text{tot,line}} = 13.82 + j25.92 \text{ VA} = 29.38e^{j61.93^\circ} \text{ VA}$$

- ▶ Finally, compute the total average and reactive power of the lines

$$P_{\text{tot,line}} = \text{Re}(\mathbf{S}_{\text{tot,line}}) \rightarrow P_{\text{tot,line}} = 13.82 \text{ W}$$
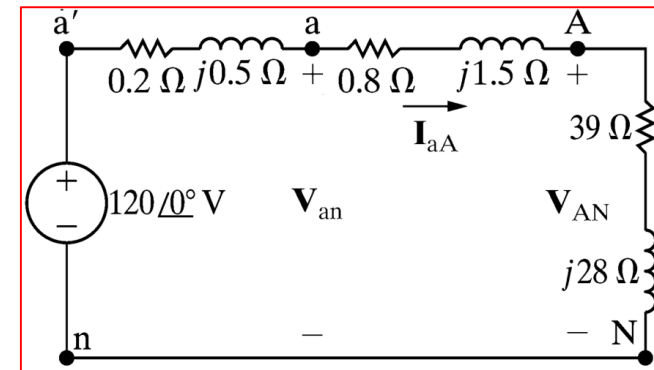
$$Q_{\text{tot,line}} = \text{Im}(\mathbf{S}_{\text{tot,line}}) \rightarrow Q_{\text{tot,line}} = 25.92 \text{ VARs}$$



Example #1 (SOLUTION cont'd)

- ▶ Calculate the total complex power, average power, and reactive power lost in source
 - ▶ First, calculate a-phase line's complex power

$$\mathbf{S}_{a'a} = (\mathbf{V}_{a'n} - \mathbf{V}_{an}) \mathbf{I}_{aA}^* = |\mathbf{I}_{aA}^*|^2 Z_s = \frac{|\mathbf{V}_{a'n} - \mathbf{V}_{an}|^2}{Z_s^*}$$

$$\mathbf{S}_{a'a} = |2.4e^{-j36.89^\circ} \text{A}_{\text{rms}}|^2 (0.2 + j0.5 \Omega)$$

$$\mathbf{S}_{a'a} = 1.15 + j2.88 \text{VA} = 3.10e^{j68.20^\circ} \text{VA}$$

- ▶ Next, compute the total complex power lost in the source


$$\mathbf{S}_{\text{tot,source}} = 3\mathbf{S}_{a'a} = 3(1.15 + j2.88 \text{VA}) = 3(3.10e^{j68.20^\circ} \text{VA})$$

$$\mathbf{S}_{\text{tot,source}} = 3.46 + j8.64 \text{VA} = 9.31e^{j68.20^\circ} \text{VA}$$

- ▶ Finally, compute the total average and reactive power lost in the source

$$P_{\text{tot,source}} = \text{Re}(\mathbf{S}_{\text{tot,source}}) \rightarrow P_{\text{tot,source}} = 3.46 \text{ W}$$
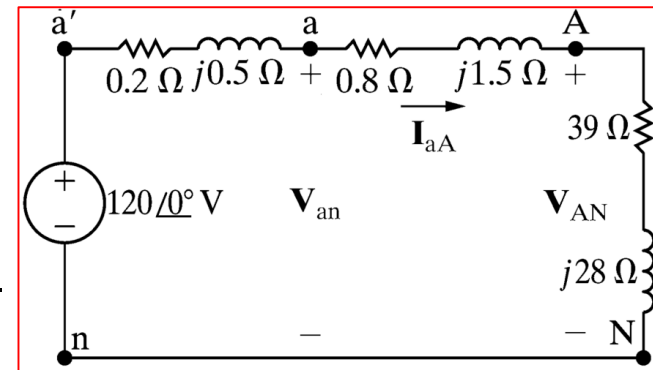
$$Q_{\text{tot,source}} = \text{Im}(\mathbf{S}_{\text{tot,source}}) \rightarrow Q_{\text{tot,source}} = 8.64 \text{ VARs}$$



Example #2

- ▶ A balanced 3-phase Y source with a-b-c sequence has an impedance of $Z_s = 0.2 + j0.5 \Omega/\phi$ and a voltage of $\mathbf{V}_{a'n} = 120e^{j0^\circ} \text{ V (rms)}$. The source drives a balanced 3-phase Δ load with an impedance of $Z_\Delta = 118.5 + j85.8 \Omega/\phi$. The line impedance connecting source to the load is $Z_\ell = 0.3 + j0.9 \Omega/\phi$. Use a-phase internal source voltage as the reference.
 - ▶ Draw the a-phase Y-Y equivalent network of the Y- Δ system
 - ▶ Calculate the line currents for each phase
 - ▶ Calculate the phase voltages at the load terminals
 - ▶ Calculate the phase currents of the load
 - ▶ Calculate the line-to-line voltages at the source's terminals
 - ▶ Calculate the total complex power, average power, and reactive power absorbed by the source
 - ▶ Calculate the total apparent power of the load
 - ▶ Calculate the power factor of the load

Example #2 (SOLUTION)

- ▶ Draw the a-phase Y-Y equivalent network of the Y-Δ system

- ▶ Transform Z_{Δ} load to equivalent Z_Y load
 $Z_Y = Z_{\Delta}/3 = (118.5 + j85.8\Omega)/3$

$$Z_Y = 39.5 + j28.6 \Omega$$

- ▶ Calculate line currents for each phase

- ▶ First compute the a-phase equivalent impedance Z_{ϕ}

$$Z_{\phi} = Z_s + Z_{\ell} + Z_Y$$

$$Z_{\phi} = (0.2 + 0.3 + 39.5) + j(0.5 + 0.9 + 28.6) \rightarrow Z_{\phi} = 40 + j30 \Omega$$


- ▶ Next compute the a-phase transmission line current

$$I_{aA} = V_{a'n}/Z_{\phi} = [120e^{j0^\circ}V(rms)]/(40 + j30\Omega) \rightarrow I_{aA} \approx 2.4e^{-j36.89^\circ}A(rms)$$

- ▶ Finally, compute the b- and c-phase line currents (a-b-c) sequence

$$I_{bB} = (e^{-j120^\circ})I_{aA} \rightarrow I_{bB} \approx 2.4e^{-j156.89^\circ}A(rms)$$
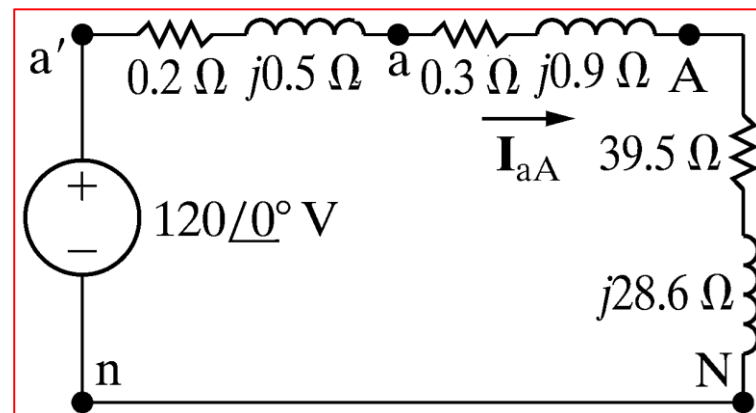
$$I_{cC} = (e^{+j120^\circ})I_{aA} \rightarrow I_{cC} \approx 2.4e^{+j83.11^\circ}A(rms)$$



Example #2 (SOLUTION cont'd)

- ▶ Calculate the phase voltages at the load

- ▶ First, compute the A-phase load voltage

$$\mathbf{V}_{AN} = I_{aA} Z_Y \approx [2.4e^{-j36.89^\circ} \text{A}_{(rms)}](39.5 + j28.6\Omega)$$

$$\mathbf{V}_{AN} \approx 117.04e^{-j0.96^\circ} \text{V}_{(rms)}$$

- ▶ Now, compute B- and C-phase load voltages

$$\mathbf{V}_{BN} = (e^{-j120^\circ})\mathbf{V}_{AN} \rightarrow \mathbf{V}_{BN} \approx 117.04e^{-j120.96^\circ} \text{V}_{(rms)}$$

$$\mathbf{V}_{CN} = (e^{+j120^\circ})\mathbf{V}_{AN} \rightarrow \mathbf{V}_{CN} \approx 117.04e^{+j119.04^\circ} \text{V}_{(rms)}$$

- ▶ Calculate the line-to-line voltages at the load's terminals


- ▶ Use factor $(\sqrt{3}e^{j30^\circ})$ to compute the A-B load voltage (A-B-C sequence)

$$\mathbf{V}_{AB} = (\sqrt{3}e^{j30^\circ})\mathbf{V}_{AN} \rightarrow \mathbf{V}_{AB} \approx 202.72e^{j29.04^\circ} \text{V}_{(rms)}$$

- ▶ Next, compute the B-C and C-A load voltages (A-B-C sequence)

$$\mathbf{V}_{BC} = (e^{-j120^\circ})\mathbf{V}_{AB} \rightarrow \mathbf{V}_{BC} \approx 202.72e^{-j90.96^\circ} \text{V}_{(rms)}$$
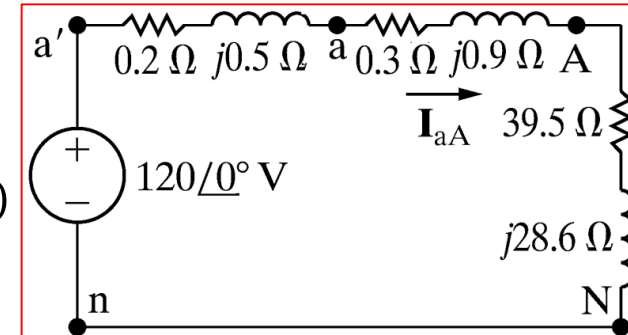
$$\mathbf{V}_{CA} = (e^{+j120^\circ})\mathbf{V}_{AB} \rightarrow \mathbf{V}_{CA} \approx 202.72e^{+j149.04^\circ} \text{V}_{(rms)}$$



Example #2 (SOLUTION cont'd)

- ▶ Calculate phase currents of the load
 - ▶ Compute the a-phase current at load terminals


$$\mathbf{I}_{AB} = \frac{\mathbf{V}_{AB}}{\mathbf{Z}_{\Delta}} = (202.72e^{j29.04^\circ} \text{V}) / (118.5 + j85.8\Omega)$$

$$\mathbf{I}_{AB} \approx 1.39e^{-j6.87^\circ} \text{A}(rms)$$

- ▶ Now, compute B- and C-phase load currents (a-b-c seq.)

$$\mathbf{I}_{BC} = (e^{-j120^\circ})\mathbf{I}_{AB} \rightarrow \mathbf{I}_{BC} \approx 1.39e^{-j126.87^\circ} \text{A}(rms)$$
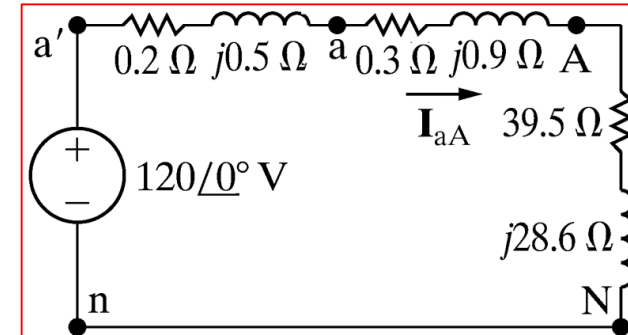
$$\mathbf{I}_{CA} = (e^{-j120^\circ})\mathbf{I}_{CA} \rightarrow \mathbf{I}_{CA} \approx 1.39e^{j113.13^\circ} \text{A}(rms)$$



Example #2 (SOLUTION cont'd)

- ▶ Calculate the line-to-line voltages at the source's terminals

- ▶ First, compute the a-phase voltage at the source's terminals

$$\mathbf{V}_{an} = \mathbf{V}_{a'n} - \mathbf{I}_{aA} Z_S$$

$$\mathbf{V}_{an} \approx 120e^{j0^\circ} \text{V} - [2.4e^{-j36.89^\circ} \text{A}](0.2 + j0.5 \Omega)$$

$$\mathbf{V}_{an} \approx 118.90e^{-j0.32^\circ} \text{V(rms)}$$

- ▶ Next, compute a-b line source terminal voltage


$$\mathbf{V}_{ab} = (\sqrt{3}e^{j30^\circ})\mathbf{V}_{AN} \approx (\sqrt{3}e^{j30^\circ})(118.90e^{-j0.32^\circ} \text{V})$$

$$\mathbf{V}_{ab} \approx 205.94e^{j29.68^\circ} \text{V(rms)}$$

- ▶ Finally, compute the b-c and c-a load voltages (a-b-c sequence)

$$\mathbf{V}_{bc} = (e^{-j120^\circ})\mathbf{V}_{ab} \rightarrow \mathbf{V}_{bc} \approx 205.94e^{-j90.32^\circ} \text{V(rms)}$$
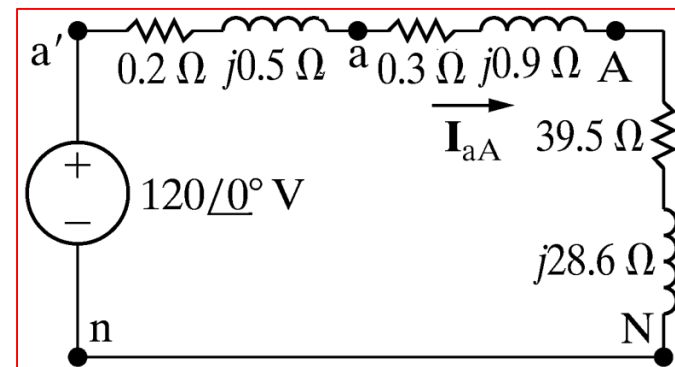
$$\mathbf{V}_{ca} = (e^{+j120^\circ})\mathbf{V}_{ab} \rightarrow \mathbf{V}_{ca} \approx 205.94e^{+j149.68^\circ} \text{V(rms)}$$



Example #2 (SOLUTION cont'd)

- ▶ Calculate total complex power, average power, and reactive power absorbed by the source

- ▶ First, calculate source's a-phase complex power

$$\mathbf{S}_{a'n} = -\mathbf{V}_{a'n} \mathbf{I}_{aA}^* = -|\mathbf{I}_{aA}|^2 Z_\phi = -|\mathbf{V}_{a'n}|^2 / Z_\phi^*$$

$$\mathbf{S}_{a'n} = -(120e^{j0^\circ} \text{V}_{\text{rms}})(2.4e^{-j36.89^\circ} \text{A}_{\text{rms}})^*$$

$$\mathbf{S}_{a'n} = -230.34 - j172.81 \text{ VA} = 288e^{-j143.11^\circ} \text{ VA}$$

- ▶ Next, compute the total complex power absorbed by the source


$$\mathbf{S}_{\text{tot},\text{source}} = 3\mathbf{S}_{a'n} = 3(-230.34 - j172.81 \text{ VA}) = 3(288e^{-j143.11^\circ} \text{ VA})$$

$$\mathbf{S}_{\text{tot},\text{source}} = -691.02 - j518.64 \text{ VA} = 864e^{-j143.11^\circ} \text{ VA}$$

- ▶ Finally, compute the total average and reactive power absorbed by the source

$$P_{\text{tot},\text{source}} = \text{Re}(\mathbf{S}_{\text{tot},\text{source}}) \rightarrow P_{\text{tot},\text{source}} = -691.02 \text{ W absorb}$$
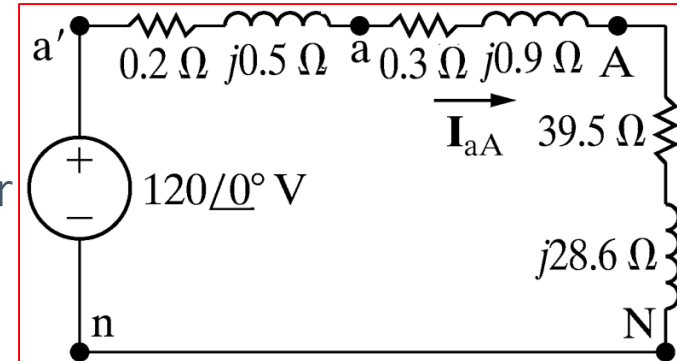
$$Q_{\text{tot},\text{source}} = \text{Im}(\mathbf{S}_{\text{tot},\text{source}}) \rightarrow Q_{\text{tot},\text{source}} = -518.64 \text{ VARs absorb}$$



Example #2 (SOLUTION cont'd)

- ▶ Calculate the total apparent power of the load

- ▶ First, calculate A-phase complex power of load

$$\mathbf{S}_{AB} = \mathbf{V}_{AB} \mathbf{I}_{AB}^* = |\mathbf{V}_{AB}|^2 / Z_{\Delta}^*$$

$$\mathbf{S}_{AB} = |202.72 e^{j29.04^\circ} V_{rms}|^2 / (118.5 + j85.8 \Omega)^*$$

$$\mathbf{S}_{AB} = 227.52 + j164.74 \text{ VA} = 280.90 e^{j35.91^\circ} \text{ VA}$$

- ▶ Next, compute the total complex power absorbed by the load

$$\mathbf{S}_{tot,load} = 3\mathbf{S}_{AB} = 3(227.52 + j164.74 \text{ VA}) = 3(280.90 e^{j35.91^\circ} \text{ VA})$$

$$\mathbf{S}_{tot,load} = 682.56 + j494.21 \text{ VA} = 842.69 e^{j35.91^\circ} \text{ VA}$$


- ▶ Finally, compute the total apparent power of the load

$$S_{tot,load} = |\mathbf{S}_{tot,load}| \rightarrow S_{tot,load} = 842.69 \text{ VA}$$

- ▶ Calculate the power factor of the load

$$pf_{load} = \cos(\theta_s) = \cos(\theta_{Z_{\Delta}}) = \frac{P_{tot,load}}{|\mathbf{S}_{tot,load}|}$$
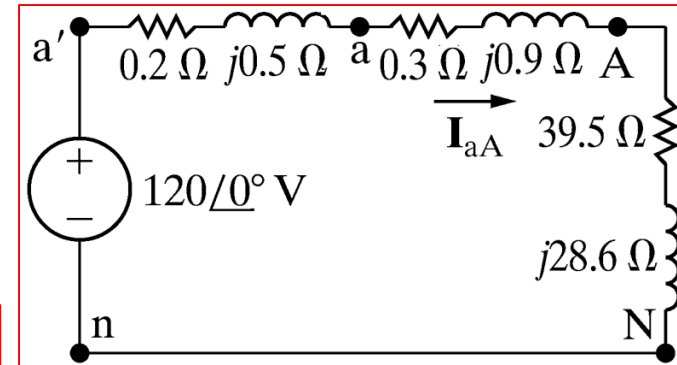
$$pf_{load} = \cos(35.91^\circ) = \frac{682.56 \text{ W}}{842.69 \text{ VA}} \rightarrow pf_{load} = 0.81 \text{ lagging}$$



Example #3

- ▶ A balanced 3-phase Δ source with a-b-c sequence has a negligible internal impedance and an a-phase terminal voltage of $\mathbf{V}_{ab} = 208e^{j0^\circ} \text{ V}$ (rms). The source drives a balanced 3-phase Y load with an impedance of $\mathbf{Z}_Y = 12 + j4 \, \Omega/\phi$. The line impedance connecting source and load is $\mathbf{Z}_\ell = 0.1 + j0.2 \, \Omega/\phi$.
 - ▶ Draw the single-phase equivalent network of the 3-phase network
 - ▶ Calculate the transmission line currents for each phase
 - ▶ Calculate the phase voltages at the load terminals
 - ▶ Calculate the phase currents of the load
 - ▶ Calculate the line-to-line currents for the source
 - ▶ Calculate the total complex power, average power, and reactive power delivered by the source
 - ▶ Calculate the total apparent power absorbed of the load


Example #3 (SOLUTION)

- Draw single-phase equivalent network of the system

- Transform the Δ source of $\mathbf{V}_{ab} = 208e^{j0^\circ}$ V to equivalent Y source

$$\mathbf{V}_{ab} = (\sqrt{3}e^{j30^\circ})\mathbf{V}_{an} \rightarrow \mathbf{V}_{an} = \mathbf{V}_{ab}/(\sqrt{3}e^{j30^\circ})$$
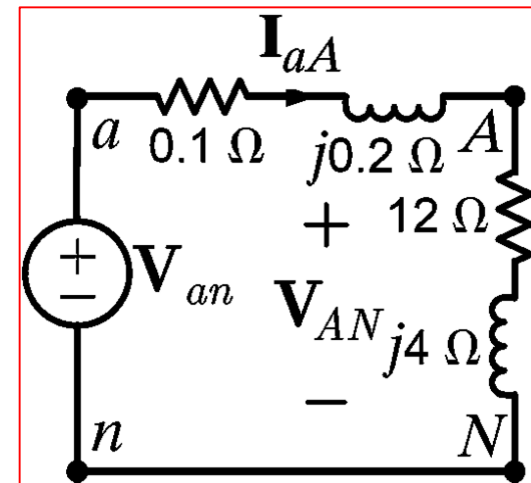
$$\mathbf{V}_{an} = \frac{208e^{j0^\circ} \text{ V}}{(\sqrt{3}e^{j30^\circ})} \rightarrow \boxed{\mathbf{V}_{an} = 120.09e^{-j30^\circ} \text{ V (rms)}}$$



- Calculate the transmission line currents

$$\mathbf{I}_{aA} = \mathbf{V}_{an}/Z_\phi = (120.09e^{-j30^\circ} \text{ V (rms)})/(12.1\Omega + j4.2\Omega)$$

$$\boxed{\mathbf{I}_{aA} = 9.38e^{-j49.14^\circ} \text{ A (rms)}}$$

$$\mathbf{I}_{bB} = (e^{-j120^\circ})\mathbf{I}_{aA} = (e^{-j120^\circ})(9.38e^{-j49.14^\circ} \text{ A (rms)})$$

$$\boxed{\mathbf{I}_{bB} = 9.38e^{-j169.14^\circ} \text{ A (rms)}}$$

$$\mathbf{I}_{cC} = (e^{+j120^\circ})\mathbf{I}_{aA} = (e^{+j120^\circ})(9.38e^{-j49.14^\circ} \text{ A (rms)})$$

$$\boxed{\mathbf{I}_{cC} = 9.38e^{j70.86^\circ} \text{ A (rms)}}$$

Example #3 (SOLUTION cont'd)

- Calculate the phase voltages at the load terminals

$$\mathbf{V}_{AN} = \mathbf{I}_{aA} \mathbf{Z}_Y = (9.38e^{-j49.14^\circ} \text{ A})(12\Omega + j4\Omega)$$

$$\mathbf{V}_{AN} = 118.65e^{-j30.71^\circ} \text{ V (rms)}$$

$$\mathbf{V}_{BN} = (e^{-j120^\circ})\mathbf{V}_{AN} = (e^{-j120^\circ})(118.65e^{-j30.71^\circ} \text{ V})$$

$$\mathbf{V}_{BN} = 118.65e^{-j150.71^\circ} \text{ V (rms)}$$

$$\mathbf{V}_{CN} = (e^{-j120^\circ})\mathbf{V}_{AN} = (e^{j120^\circ})(118.65e^{-j30.71^\circ} \text{ V})$$


$$\mathbf{V}_{CN} = 118.65e^{j89.29^\circ} \text{ V (rms)}$$

- Calculate the phase currents of the load

$$\mathbf{I}_{AN} = \mathbf{I}_{aA} \rightarrow \mathbf{I}_{AN} = 9.38e^{-j49.14^\circ} \text{ A (rms)}$$

$$\mathbf{I}_{BN} = \mathbf{I}_{bB} \rightarrow \mathbf{I}_{BN} = 9.38e^{-j169.14^\circ} \text{ A (rms)}$$
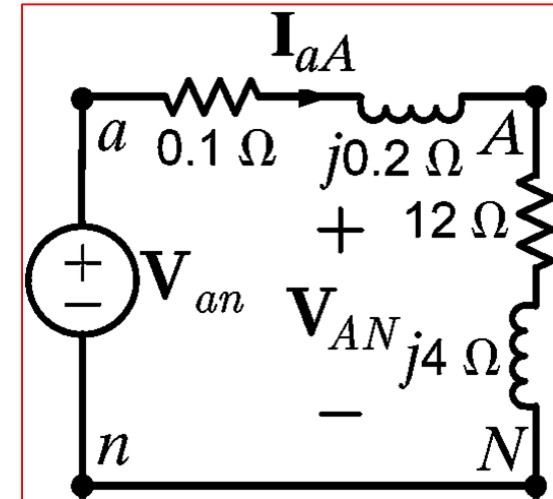
$$\mathbf{I}_{CN} = \mathbf{I}_{cC} \rightarrow \mathbf{I}_{CN} = 9.38e^{j70.86^\circ} \text{ A (rms)}$$



Example #3 (SOLUTION cont'd)

- Calculate the line-to-line voltage at the load

$$\mathbf{V}_{AB} = (\sqrt{3}e^{j30^\circ})\mathbf{V}_{AN} = (\sqrt{3}e^{j30^\circ})(118.65e^{-j30.71^\circ}\text{V})$$

$$\mathbf{V}_{AB} = 205.51e^{-j0.71^\circ} \text{ (rms)}$$

$$\mathbf{V}_{BC} = (e^{-j120^\circ})\mathbf{V}_{AN} \rightarrow \mathbf{V}_{BC} = 205.51e^{-j120.71^\circ} \text{ A (rms)}$$

$$\mathbf{V}_{CA} = (e^{j120^\circ})\mathbf{V}_{AN} \rightarrow \mathbf{V}_{BC} = 205.51e^{j119.25^\circ} \text{ A (rms)}$$

- Calculate the line-to-line (phase) currents for the source


$$\mathbf{I}_{aA} = \mathbf{I}_{ba} - \mathbf{I}_{ac} = (1 - e^{j120^\circ})\mathbf{I}_{ba} \rightarrow \mathbf{I}_{aA} = (\sqrt{3}e^{-j30^\circ})\mathbf{I}_{ba}$$

$$\mathbf{I}_{ba} = \mathbf{I}_{aA} / (\sqrt{3}e^{-j30^\circ}) = (9.38e^{-j49.14^\circ}\text{A}) / (\sqrt{3}e^{-j30^\circ})$$

$$\mathbf{I}_{ba} = 5.42e^{-j19.14^\circ} \text{ A (rms)}$$

$$\mathbf{I}_{cb} = (e^{-j120^\circ})\mathbf{I}_{ba} \Rightarrow \mathbf{I}_{cb} = 5.42e^{-j139.14^\circ} \text{ A (rms)}$$
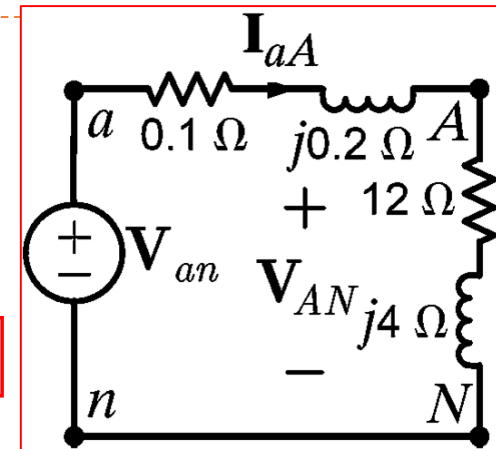
$$\mathbf{I}_{ac} = (e^{-j120^\circ})\mathbf{I}_{ba} \rightarrow \mathbf{I}_{ac} = 5.42e^{j100.86^\circ} \text{ A (rms)}$$



Example #3 (SOLUTION cont'd)

- ▶ Calculate the total complex power, average power, and reactive power delivered by the source
 - ▶ First, compute total complex power supplied by source

$$\mathbf{S}_{tot,src} = 3\mathbf{S}_{ab} = (+)3\mathbf{V}_{ab}\mathbf{I}_{ba}^*$$

$$\mathbf{S}_{tot,src} = 3\mathbf{V}_{ab}\mathbf{I}_{ba}^* = (3)(208e^{j0^\circ}\text{V}_{rms})(5.42e^{-j19.14^\circ}\text{A}_{rms})^*$$

$$\mathbf{S}_{tot,src} = 3382.08e^{j19.14^\circ}\text{VA supplied} = 3195.12 + j1108.91\text{VA supplied}$$

- ▶ Next, compute total average and reactive power delivered by source

$$P_{tot,src} = \text{Re}(\mathbf{S}_{tot,src}) \rightarrow P_{tot,src} = 3195.12 \text{ W}$$


$$Q_{tot,src} = \text{Im}(\mathbf{S}_{tot,src}) \rightarrow Q_{tot,src} = 1108.91 \text{ VARs}$$

- ▶ Calculate the total apparent power absorbed of the load

$$S_{tot,AN} = 3|\mathbf{S}_{AN}| = (+)3|\mathbf{V}_{AN}\mathbf{I}_{AN}^*|$$

$$S_{tot,AN} = (3) \left| (118.65e^{-j30.71^\circ}\text{V}_{rms})(9.38e^{-j49.14^\circ}\text{A}_{rms})^* \right|$$

$$S_{tot,AN} = 3338.82 \text{ VA}$$

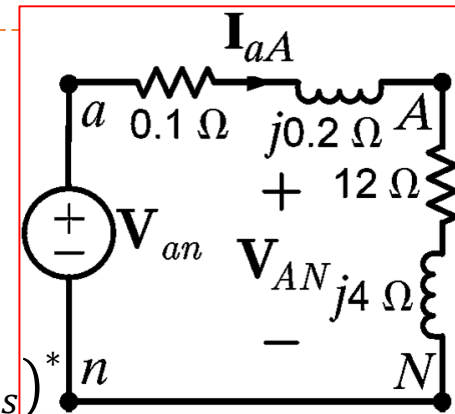

Example #4

- ▶ A balanced 3-phase Δ -source with a-b-c sequence has a source impedance of $Z_S = 0.1 + j0.2 \Omega/\phi$ and an ideal voltage of $\mathbf{V}_{a'b} = 240e^{j10^\circ}$ V (rms). The source drives a balanced Δ -load with impedance $Z_\Delta = 30 - j20 \Omega/\phi$. The line impedance connecting the source and load is $Z_\ell = 0.6 + j0.5 \Omega/\phi$.
 - ▶ Draw the single-phase equivalent network of the system
 - ▶ Calculate the transmission line currents for each phase
 - ▶ Calculate the phase voltages at the load terminals
 - ▶ Calculate the phase currents of the load
 - ▶ Calculate the line-to-line currents through the source
 - ▶ Calculate the line-to-line voltages at the source terminals

Example #4 (SOLUTION)

- ▶ Draw single-phase equivalent network of the system

- ▶ Transform the Δ source of $\mathbf{V}_{a'b} = 240e^{j10^\circ}$ V (rms) to equivalent Y internal source voltage $\mathbf{V}_{a'n}$

$$\mathbf{V}_{a'b} = (\sqrt{3}e^{j30^\circ})\mathbf{V}_{an} \rightarrow \mathbf{V}_{a'n} = \mathbf{V}_{a'b}/(\sqrt{3}e^{j30^\circ})$$

$$\mathbf{V}_{a'n} = \frac{240e^{j10^\circ} \text{ V}}{(\sqrt{3}e^{j30^\circ})} \rightarrow \boxed{\mathbf{V}_{a'n} = 80\sqrt{3}e^{-j20^\circ} \text{ V (rms)}}$$


- ▶ Transform the Δ source impedance of $Z_{s\Delta} = 0.1\Omega + j0.2\Omega$ to an equivalent Y source impedance Z_{sY}

$$Z_{sY} = Z_{s\Delta}/3 = (0.1\Omega + j0.2\Omega)/3 \rightarrow \boxed{Z_{sY} = 33.3 \text{ m}\Omega + j66.7 \text{ m}\Omega}$$

- ▶ Transform the Δ load impedance of $Z_{\Delta} = 30\Omega - j20\Omega$ to an equivalent Y load impedance Z_Y

$$Z_Y = Z_{\Delta}/3 = (30\Omega - j20\Omega)/3 \rightarrow \boxed{Z_Y = 10\Omega - j6.7\Omega}$$

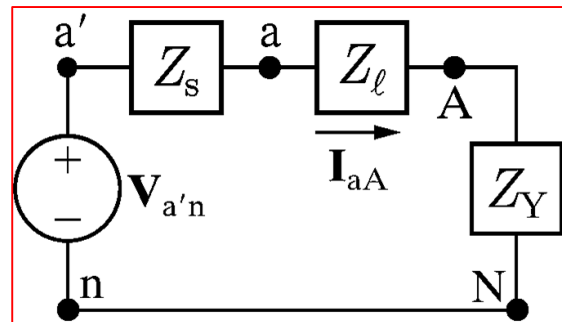- ▶ Note, the line impedance remains unchanged



Example #4 (SOLUTION cont'd)

- Compute the transmission line currents

$$I_{aA} = V_{a'n}/Z_{\phi} = V_{a'n}/(Z_{sY} + Z_l + Z_Y)$$

$$I_{aA} = [80\sqrt{3}e^{-j20^\circ} \text{ V (rms)}] / (10.63\Omega - j6.1\Omega)$$


$$I_{aA} = 11.31e^{j9.85^\circ} \text{ A (rms)}$$

$$I_{bB} = (e^{-j120^\circ})I_{aA} = (e^{-j120^\circ})[11.31e^{j9.85^\circ} \text{ A (rms)}]$$

$$I_{bB} = 11.31e^{-j110.15^\circ} \text{ A (rms)}$$

$$I_{cC} = (e^{+j120^\circ})I_{aA} = (e^{+j120^\circ})[11.31e^{j9.85^\circ} \text{ A (rms)}]$$
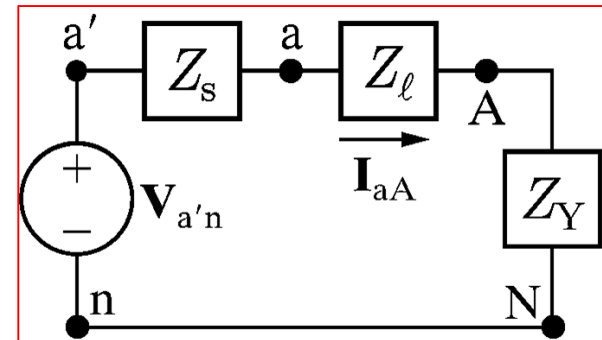
$$I_{cC} = 11.31e^{j29.85^\circ} \text{ A (rms)}$$



Example #4 (SOLUTION cont'd)

- ▶ Calculate the phase voltages at the load terminals

- ▶ First, compute the terminal voltage of the equivalent Y load

$$\mathbf{V}_{AN} = \mathbf{I}_{aA} \mathbf{Z}_Y = [11.31e^{j9.85^\circ} \text{ A}][10\Omega - j6.7\Omega]$$

$$\mathbf{V}_{AN} = 136.14e^{-j23.97^\circ} \text{ V (rms)}$$

$$\mathbf{V}_{BN} = (e^{-j120^\circ})\mathbf{V}_{AN} \rightarrow \mathbf{V}_{BN} = 136.14e^{-j143.97^\circ} \text{ V (rms)}$$

$$\mathbf{V}_{CN} = (e^{+j120^\circ})\mathbf{V}_{AN} \rightarrow \mathbf{V}_{CN} = 136.14e^{j96.03^\circ} \text{ V (rms)}$$


- ▶ Now, compute the terminal voltage of the actual delta load

$$\mathbf{V}_{AB} = (\sqrt{3}e^{j30^\circ})\mathbf{V}_{AN} = (\sqrt{3}e^{j30^\circ})[136.14e^{-j23.97^\circ} \text{ V (rms)}]$$

$$\mathbf{V}_{AB} = 235.80e^{j6.03^\circ} \text{ V (rms)}$$

$$\mathbf{V}_{BC} = (e^{-j120^\circ})\mathbf{V}_{AB} \rightarrow \mathbf{V}_{BC} = 235.80e^{-j113.97^\circ} \text{ V (rms)}$$
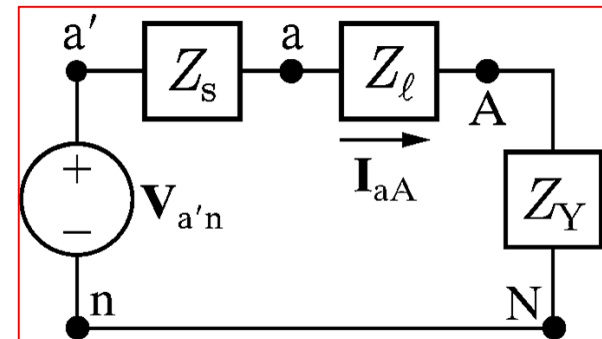
$$\mathbf{V}_{CA} = (e^{+j120^\circ})\mathbf{V}_{AB} \rightarrow \mathbf{V}_{CA} = 235.80e^{j126.03^\circ} \text{ V (rms)}$$



Example #4 (SOLUTION cont'd)

- Calculate the phase currents of the load
 - One way to compute the load's phase currents is to use the load's phase (line-to-line) voltages

$$\mathbf{I}_{AB} = \mathbf{V}_{AB}/Z_{\Delta} = [235.80e^{j6.03^\circ} \text{ V}]/[30\Omega - j20\Omega]$$

$$\mathbf{I}_{AB} = 6.54e^{-j39.72^\circ} \text{ A (rms)}$$

$$\mathbf{I}_{BC} = (e^{-j120^\circ})\mathbf{I}_{AB} \rightarrow \mathbf{I}_{BC} = 6.54e^{-j80.28^\circ} \text{ A (rms)}$$

$$\mathbf{I}_{CA} = (e^{+j120^\circ})\mathbf{I}_{AB} \rightarrow \mathbf{I}_{CA} = 6.54e^{j159.72^\circ} \text{ A (rms)}$$


- One can also compute the load's phase current using \mathbf{I}_{aA}

$$\mathbf{I}_{aA} = \mathbf{I}_{AB} - \mathbf{I}_{CA} = \mathbf{I}_{AB} - \mathbf{I}_{AB}e^{j120^\circ} = (\sqrt{3}e^{-j30^\circ})\mathbf{I}_{AB}$$

$$\mathbf{I}_{AB} = \frac{\mathbf{I}_{aA}}{(\sqrt{3}e^{-j30^\circ})} = \frac{11.31e^{j9.85^\circ} \text{ A rms}}{\sqrt{3}e^{-j30^\circ}} \rightarrow \mathbf{I}_{AB} \approx 6.54e^{-j39.72^\circ} \text{ A (rms)}$$

$$\mathbf{I}_{BC} = (e^{-j120^\circ})\mathbf{I}_{AB} \rightarrow \mathbf{I}_{BC} = 6.54e^{-j80.28^\circ} \text{ A (rms)}$$
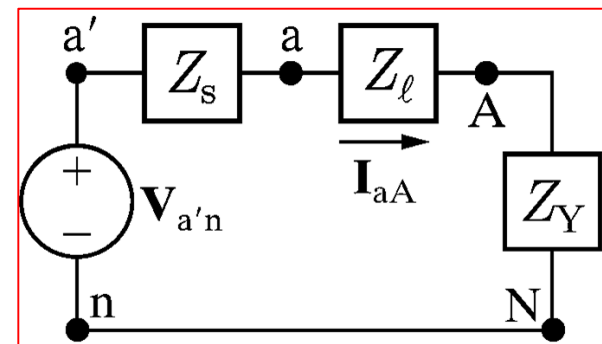
$$\mathbf{I}_{CA} = (e^{+j120^\circ})\mathbf{I}_{AB} \rightarrow \mathbf{I}_{CA} = 6.54e^{j159.72^\circ} \text{ A (rms)}$$



Example #4 (SOLUTION cont'd)

- ▶ Calculate the phase currents through the source
 - ▶ Compute the source's phase currents using the transmission line current

$$\mathbf{I}_{aA} = \mathbf{I}_{ba} - \mathbf{I}_{ac} = (1 - e^{j120^\circ})\mathbf{I}_{ba}$$


$$\mathbf{I}_{aA} = (\sqrt{3}e^{-j30^\circ})\mathbf{I}_{ba} \rightarrow \mathbf{I}_{ba} = \mathbf{I}_{aA}/(\sqrt{3}e^{-j30^\circ})$$

$$\mathbf{I}_{ba} = (11.31e^{j9.85^\circ} \text{ A (rms)})/(\sqrt{3}e^{-j30^\circ})$$

$$\mathbf{I}_{ba} = 6.54e^{-j39.72^\circ} \text{ A (rms)}$$

$$\mathbf{I}_{cb} = (e^{-j120^\circ})\mathbf{I}_{ba} \rightarrow \mathbf{I}_{cb} = 6.54e^{-j80.28^\circ} \text{ A (rms)}$$
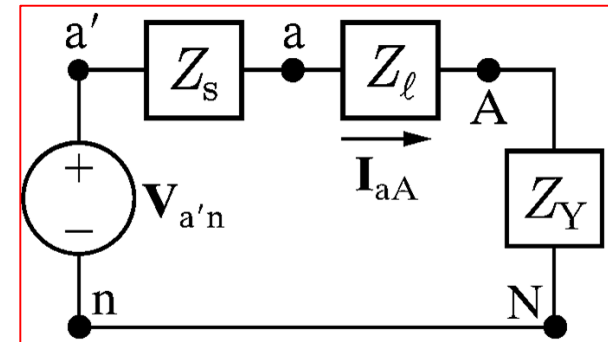
$$\mathbf{I}_{ac} = (e^{+j120^\circ})\mathbf{I}_{ba} \rightarrow \mathbf{I}_{ac} = 6.54e^{j159.72^\circ} \text{ A (rms)}$$



Example #4 (SOLUTION cont'd)

- ▶ Calculate the line-to-line (phase) voltages at the source terminals

- ▶ First, compute \mathbf{V}_{an} of single-phase equivalent network

$$\mathbf{V}_{an} = (Z_l + Z_Y)\mathbf{I}_{aA} = \mathbf{V}_{a'n} - \mathbf{I}_{aA}Z_{sY}$$

$$\mathbf{V}_{an} = (10.6\Omega - j6.2\Omega)(11.31e^{j9.85^\circ} \text{ A rms})$$

$$\mathbf{V}_{an} = 138.88e^{-j20.47^\circ} \text{ V (rms)}$$


- ▶ Now, use \mathbf{V}_{an} to compute the phase voltages at the source terminals

$$\mathbf{V}_{ab} = (\sqrt{3}e^{j30^\circ})\mathbf{V}_{an} = (\sqrt{3}e^{j30^\circ})(138.62e^{-j20.35^\circ} \text{ V (rms)})$$

$$\mathbf{V}_{ab} = 240.6e^{j9.52^\circ} \text{ V rms}$$

$$\mathbf{V}_{bc} = (e^{-j120^\circ})\mathbf{V}_{ab} \rightarrow \mathbf{V}_{bc} = 240.6e^{-j110.47^\circ} \text{ V (rms)}$$
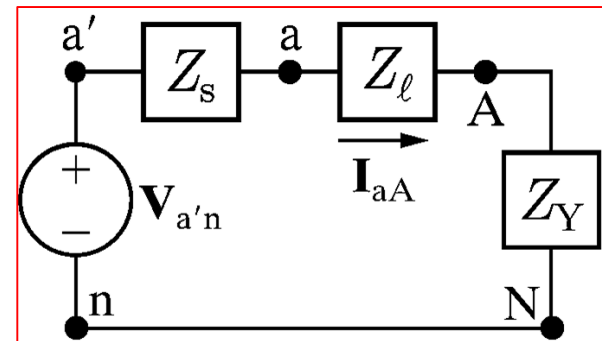
$$\mathbf{V}_{ca} = (e^{+j120^\circ})\mathbf{V}_{ab} \rightarrow \mathbf{V}_{ca} = 240.6e^{j129.53^\circ} \text{ V (rms)}$$



Example #5



- ▶ Two balanced loads are connected to 240 kV (rms) 3-phase lines.

- ▶ Load 1 absorbs 30 kW at a 0.6 lagging pf

- ▶ Load 2 absorbs 45 kVAR at a 0.8 lagging pf

Assume an a - b - c phase sequence for the source:

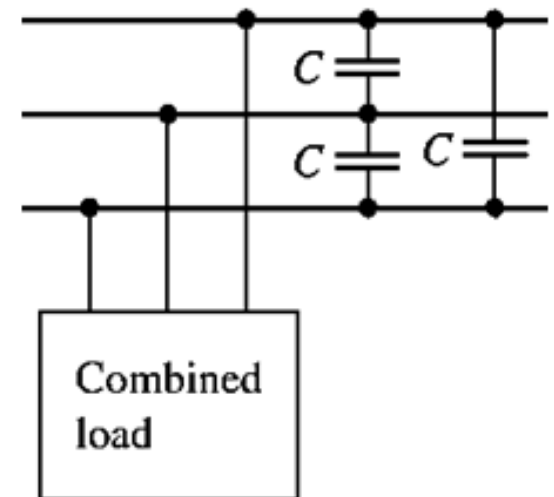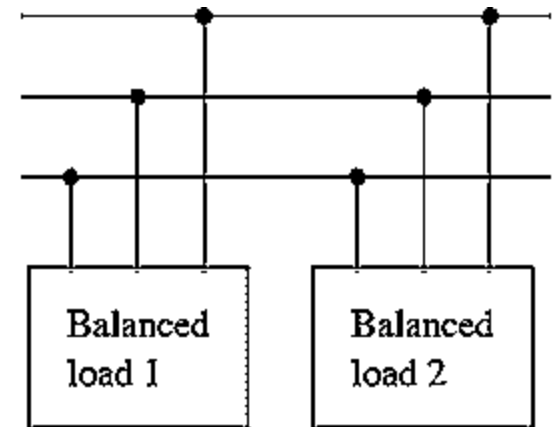- ▶ Compute the total complex, real, and reactive power absorbed by the combined load
- ▶ Compute the combined load's power factor
- ▶ Compute the kVAR rating for 3 capacitors, that when placed in parallel with the combined load, will raise combined load's pf to 0.9 lagging.
- ▶ Compute the capacitance of each capacitor assuming $f = 60\text{Hz}$ 3-phase lines.



Example #5 (SOLUTION)

- ▶ Compute total {complex, real, reactive} power absorbed by combined load

- ▶ First, compute total complex power of Load 1: 30 kW @ $pf = 0.6$ lag

$$P_1 = |\mathbf{S}_1| \cos(\theta_1) = |\mathbf{S}_1| pf_1 \rightarrow \boxed{P_1 = 30\text{kW}}$$

$$Q_1 = |\mathbf{S}_1| \sin(\theta_1) = P_1 \frac{\sin(\theta_1)}{\cos(\theta_1)} = P_1 \tan(\theta_1) = P_1 \tan(\cos^{-1}(pf_1))$$

$$Q_1 = (30\text{kW}) \tan(\cos^{-1}(0.6)) \rightarrow \boxed{Q_1 = 40\text{kVARs}}$$

$$\mathbf{S}_1 = P_1 + jQ_1 \rightarrow \boxed{\mathbf{S}_1 = 30 + j40 \text{ kVA} = 50e^{j53.13^\circ} \text{ kVA}}$$

- ▶ Next, compute total complex power of Load 2: 45 kVAR @ $pf = 0.8$ lag

$$Q_2 = |\mathbf{S}_2| \sin(\theta_2) = |\mathbf{S}_2| rf_1 \rightarrow \boxed{Q_2 = 45\text{kVAR}}$$

$$P_2 = |\mathbf{S}_2| \cos(\theta_2) = Q_2 \frac{\cos(\theta_2)}{\sin(\theta_2)} = Q_2 \cot(\theta_2) = Q_2 \cot(\cos^{-1}(pf_2))$$

$$P_2 = (45\text{kVARs}) \cot(\cos^{-1}(0.8)) \rightarrow \boxed{P_2 = 60\text{kW}}$$

$$\mathbf{S}_2 = P_2 + jQ_2 \rightarrow \boxed{\mathbf{S}_2 = 60 + j45 \text{ kVA} = 75e^{j36.87^\circ} \text{ kVA}}$$

Example #5 (SOLUTION cont'd)

- ▶ Compute total {complex, real, reactive} power absorbed by combined load

- ▶ Next, compute total complex power of combined load

$$\mathbf{S}_{comb} = \mathbf{S}_1 + \mathbf{S}_2 = (30 + j40 \text{ kVA}) + (60 + j45 \text{ kVA})$$

$$\mathbf{S}_{comb} = 90 + j85 \text{ kVA} = 123.79e^{j43.36^\circ} \text{ kVA}$$

- ▶ Finally, compute total real and reactive power of combined load

$$P_{comb} = \mathbf{Re}(\mathbf{S}_{comb}) \rightarrow P_{comb} = 90 \text{ kW absorb}$$

$$Q_{comb} = \mathbf{Im}(\mathbf{S}_{comb}) \rightarrow Q_{comb} = 85 \text{ kVARs absorb}$$

- ▶ Compute the combined load's power factor

$$pf_{comb} = \cos(\theta_{S_{comb}}) = \frac{P_{comb}}{|\mathbf{S}_{comb}|} = \cos(43.36^\circ) = \frac{90 \text{ kW}}{123.79 \text{ kVA}}$$

$$pf_{comb} = 0.747 \text{ lagging}$$

Example #5 (SOLUTION cont'd)

- ▶ Compute the quadrature (kVAR) power rating for 3 capacitors, that when placed in parallel with the combined load, will raise combined load's power factor to 0.9 lagging.

- ▶ First, compute the new power angle (use a + sign for lagging power factor)

$$\theta_{new} = (+) \cos^{-1}(pf_{new}) = (+) \cos^{-1}(0.9) \rightarrow \boxed{\theta_{new} = 25.84^\circ}$$

- ▶ Next, compute the new quadrature power of the combined load while ensuring the average power of the combined load is unchanged!

$$Q_{new} = |S_{new}| \sin(\theta_{new}) = \frac{P_{new}}{\cos(\theta_{new})} \sin(\theta_{new}) = P_{old} \tan(\theta_{new})$$

$$Q_{new} = P_{old} \cos^{-1}(pf_{new}) = (90\text{kW}) \tan(\cos^{-1}(0.9)) \rightarrow \boxed{Q_{new} = 43,489\text{kVAR}}$$

- ▶ Finally, compute the corrective reactive power for the 3 caps as the difference between the new and old reactive powers of the combined load

$$Q_{corr} = Q_{3caps} = Q_{new} - Q_{old}$$

$$Q_{corr} = (43.489 - 85.0)\text{kVARs} \rightarrow \boxed{Q_{corr} = Q_{3caps} = -41.411\text{kVARs}}$$

Example #5 (SOLUTION cont'd)

- ▶ Compute the capacitance of each capacitor assuming $f = 60\text{Hz}$ 3-phase lines.
 - ▶ First, note that $Q_{corr} = Q_{3caps} = -41.411\text{kVARs}$ is for all 3 capacitors. So, the corrective reactive power for one capacitor is computed as:

$$Q_{1cap} = Q_{3caps}/3 = (-41.411\text{kVARs})/3$$

$$Q_{1cap} = -13.804\text{kVARs}$$

- ▶ Next, compute the corresponding corrective reactance of 1 cap:

$$Q_{1cap} = \frac{|V_{line,rms}|^2}{X_{1cap}} \rightarrow X_{1cap} = \frac{|V_{line,rms}|^2}{Q_{1cap}} = \frac{(240\text{kV})^2}{-13.804\text{kVAR}}$$

$$X_{1cap} = -4.173\text{k}\Omega$$

- ▶ Next, compute the corresponding corrective reactance of 1 cap as follows:

$$X_{1cap} = -\frac{1}{\omega C} \rightarrow C = -\frac{1}{\omega X_{1cap}} = -\frac{1}{2\pi f X_{1cap}}$$

$$C = -\frac{1}{2\pi(60\text{Hz})(-4.173\text{k}\Omega)} \rightarrow C = 635.65\text{pF}$$